

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

EE 202

EXAM I

DATE: Thursday 27/2/2014


TIME: 6:00 PM-7:30 PM *

SER #	
ID#	
Name	KEY
Section#	

	Maximum Score	Score
Problem No 1	40	
Problem No 2	30	
Problem No 3	20	
Problem No 4	10	
Total	100	

Problem No 1 (40)

(a)

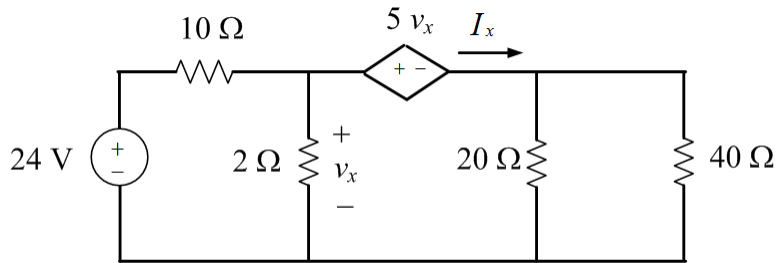


If $v_x = 8\text{ V}$, then the current I_x is

(i) 1.6 A (ii) -1.6 A (iii) 2.4 A (iv) -2.4 A

(v) 3.6 A (vi) -3.6 A (vii) 5.6 A (viii) -5.6 A

(b)

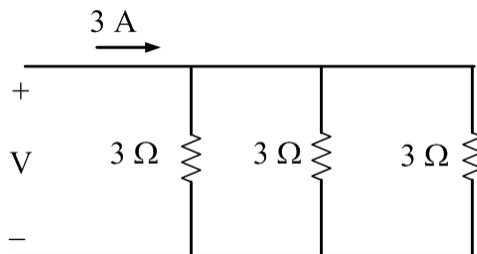


For the circuit shown above, the voltage V is

(i) 3 V (ii) -3 V (iii) 9 V (iv) -9 V

(v) 27 V (vi) -27 V (vii) 1 V (viii) -1 V


(c)

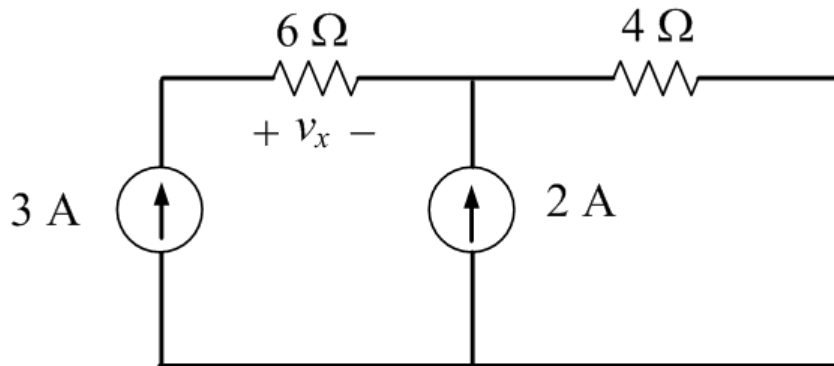

For the circuit shown above, the voltage v_x is

- (i) 30 V (ii) -30 V (iii) 6 V (iv) -6 V
(v) 12 V (vi) -12 V **(vii) 18 V** (viii) -18 V


(d)

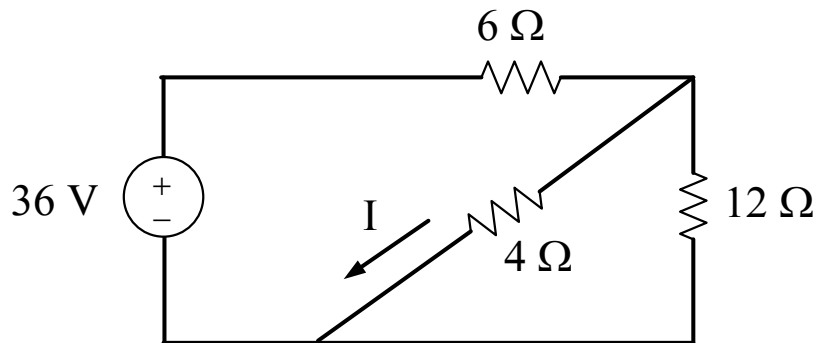

For the circuit shown above, the current I is

- (i) 1 A (ii) -1 A (iii) 4 A (iv) -4 A
(v) 3 A (vi) -3 A (vii) 2 A (viii) -2 A

(e)

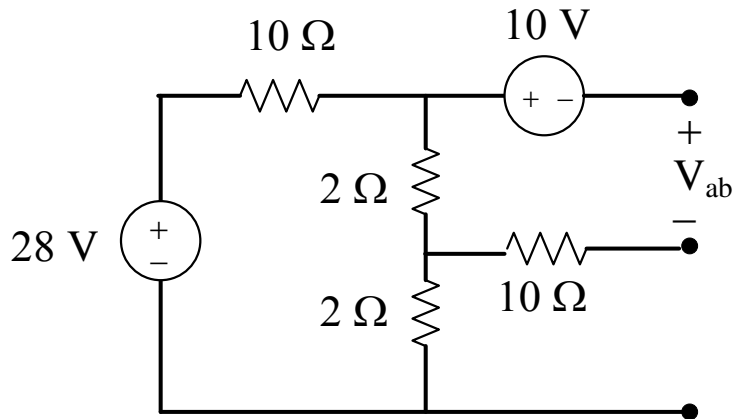


For the circuit shown above, the voltage V_{ab} is

(i) 4 V (ii) -4 V (iii) 10 V (iv) -10 V

(v) 6 V (vi) -6 V (vii) 5 V (viii) -5 V

(f)

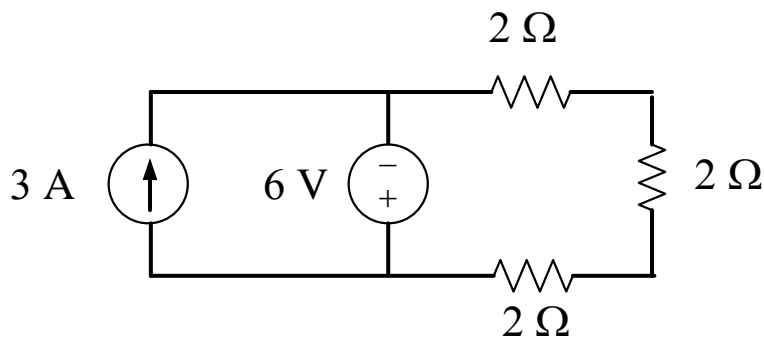


For the circuit shown above, the power delivered by the independent voltage source is

(i) 6 W (ii) -6 W (iii) 12 W (iv) -12 W

(v) 18 W (vi) -18 W (vii) 24 W (viii) -24 W

(g)

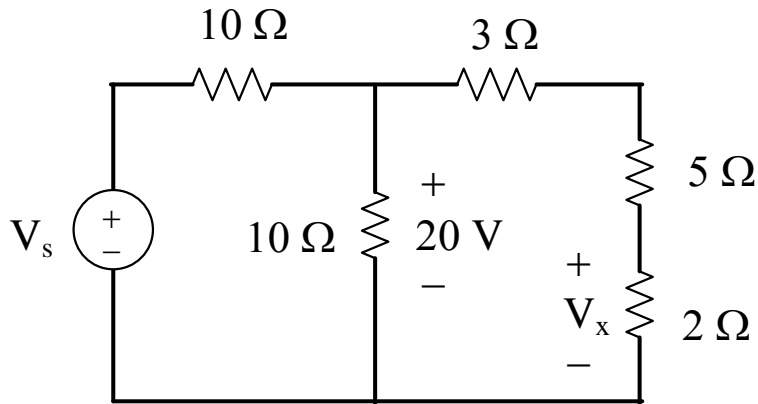


For the circuit shown above, the voltage V_x is

(i) 4 V (ii) -4 V (iii) 2 V (iv) -2 V

(v) 10 V (vi) -10 V (vii) 5 V (viii) -5 V

(h)

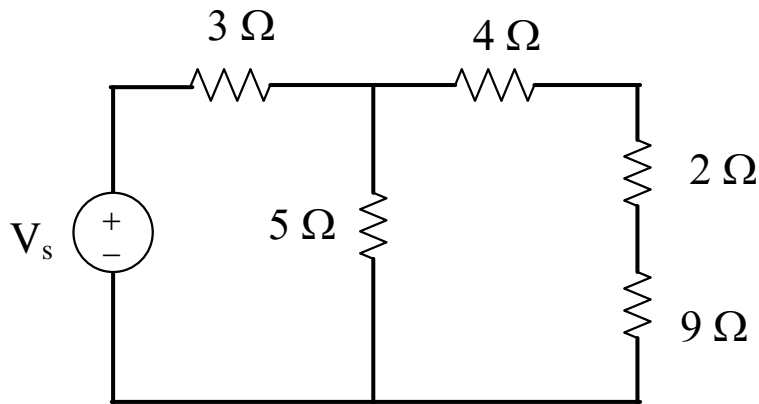


For the circuit shown above, if the $3\ \Omega$ absorbs 1200 W, then the $9\ \Omega$ absorbs

(i) 625 W (ii) 150 W (iii) 75 W (iv) 225 W

(v) 900 W (vi) 750 W (vii) 100 W (viii) 350 W


(k)

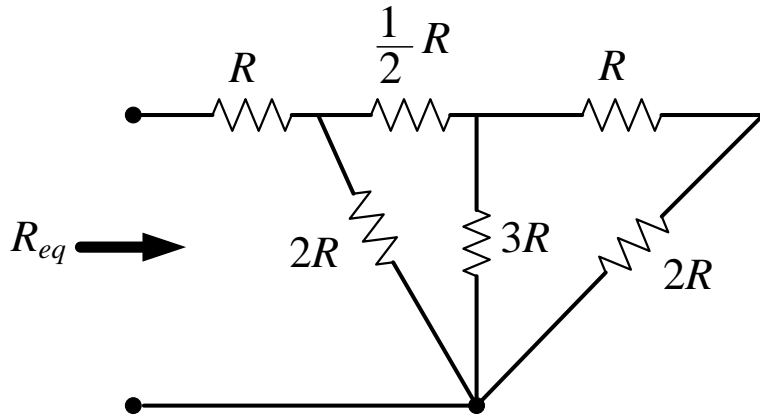

For the circuit shown above, the equivalent resistant R_{eq} is

- (i) R **(ii) $2R$** (iii) $3R$ (iv) $0.5R$
(v) $1.5R$ (vi) $2.5R$ (vii) $4R$ (viii) $3.5R$


(l)

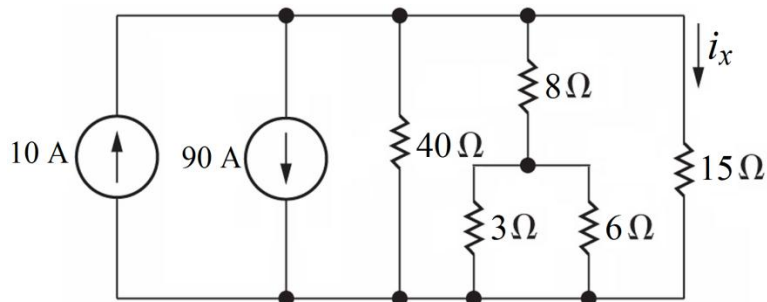

For the circuit shown above, the current i_x

- i) 16.67 A, ii) -16.67 A, iii) 18.46 A, iv) -18.46 A,
v) 27.83 A, **vi) -27.83 A,** vii) 35.44 A, viii) -35.44 A.

Problem No 2 (30)

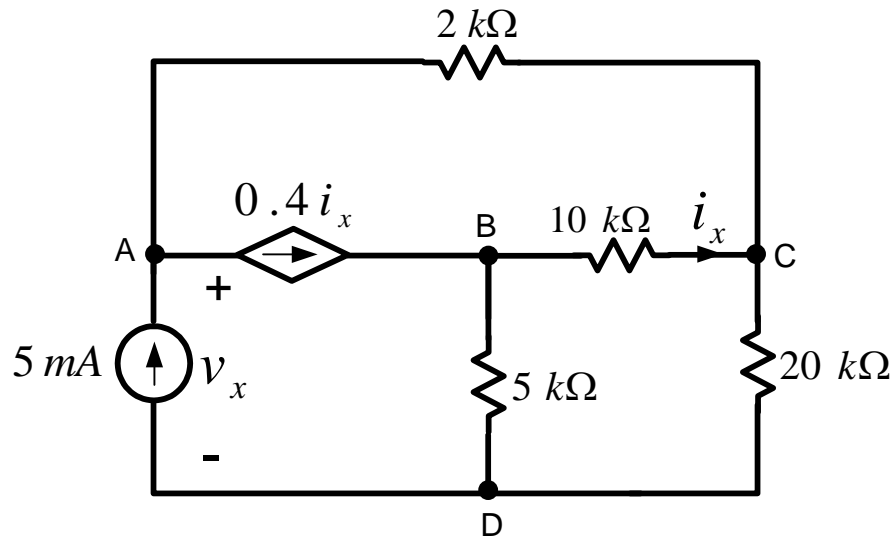

For the circuit shown above Using KCL and KVL and ohm's law ,find i_x and v_x ?

(Do Not Use Node Voltage Method or Mesh Method)

Taking KCL at A

$$i_{2k\Omega} = 5 - 0.4i_x$$

Taking KCL at B

$$i_{5k\Omega} = 0.6i_x$$

Taking KCL at C

$$i_{20k\Omega} = i_x + i_{2k\Omega} = 5 + 0.6i_x$$

Taking KVL for the path "BCDB"

$$10i_x + 20(5 + 0.6i_x) + 5 \times 0.6i_x = 0$$

$$25i_x = -100$$

$$i_x = -4 \text{ mA}$$

Taking KVL for the path "ACBA"

$$2(5 - 0.4i_x) - 10i_x = v_{AB}$$


$$v_{AB} = 53.2 \text{ V}$$

Taking KVL for the path "ABDA"

$$v_{AB} - 5 \times 0.6i_x = v_x$$

$$v_x = 65.2 \text{ V}$$

Problem No 3 (20)

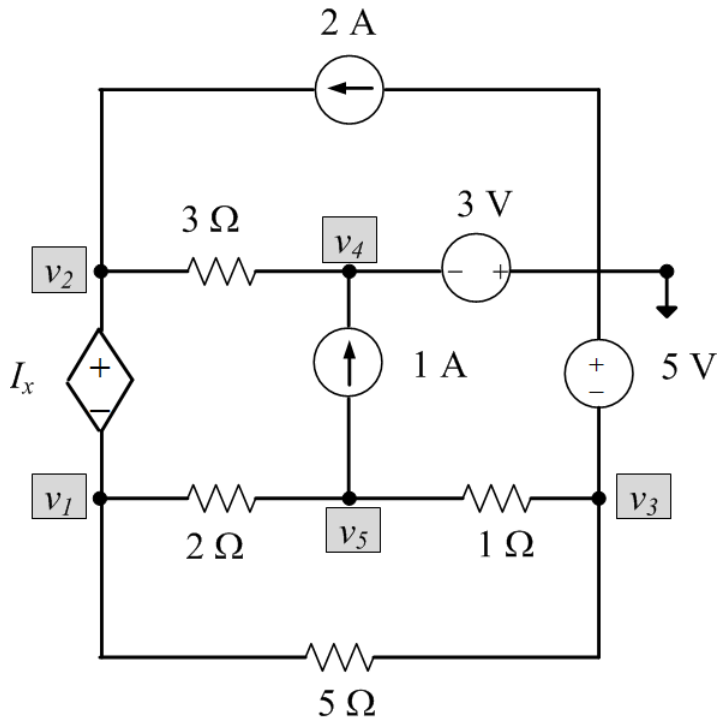

For the circuit shown above find the nodal equations necessary to solve for the node voltages v_1, v_2, v_3 **DO NOT SOLVE ANY SYSTEM OF EQUATIONS**


$$v_4 = -3 \text{ V} \quad v_5 = -5 \text{ V}$$

$$\begin{aligned} \text{KCL SN} &\Rightarrow \frac{v_2 + 3}{3} + \frac{v_1 - v_3}{2} + \frac{v_1 + 5}{5} - 2 = 0 \\ &\Rightarrow 21v_1 + 10v_2 - 15v_3 = 0 \text{ ----- (1)} \end{aligned}$$

$$\begin{aligned} \text{KCL at } v_3 &\Rightarrow \frac{v_3 - v_1}{2} + \frac{v_3 + 5}{4} + 1 = 0 \\ &\Rightarrow -2v_1 + 3v_3 = -9 \text{ ----- (2)} \end{aligned}$$

$$\begin{aligned} \text{Voltage Restriction} \quad v_2 - v_1 &= I_x = \frac{v_2 + 3}{3} \\ &\Rightarrow -3v_1 + 2v_2 = 3 \text{ ----- (3)} \end{aligned}$$

Problem No 4 (10)

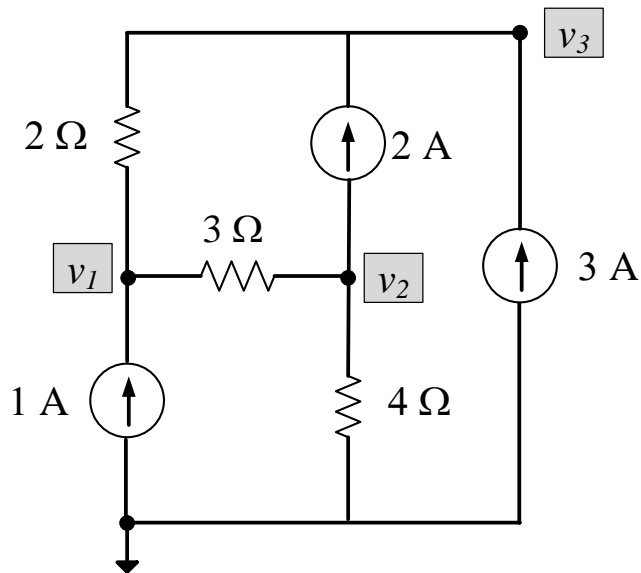

For the circuit shown above if the nod voltages are given as :

$$v_1 = 34 \text{ V} \quad v_2 = 16 \text{ V} \quad v_3 = 44 \text{ V}$$

Find the power delivered by the independent current sources ?

$$P_{1A}^{\text{delivered}} = v_1 (1) = 34(1) = 34 \text{ W}$$

$$P_{2A}^{\text{delivered}} = (v_3 - v_2)(2) = (44 - 16)(2) = 56 \text{ W}$$

$$P_{3A}^{\text{delivered}} = v_3 (3) = 44(3) = 132 \text{ W}$$