


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**ELECTRICAL ENGINEERING DEPARTMENT****EE 202****EXAM II****DATE: Sunday 13 April 2014****TIME: 6:30 PM - 8:00 PM ***

SER #	
ID#	Solution - Updated
Name	
Section#	

	Maximum Score	Score
Problem No 1	24	
Problem No 2	26	
Problem No 3	20	
Problem No 4	30	
Total	100	

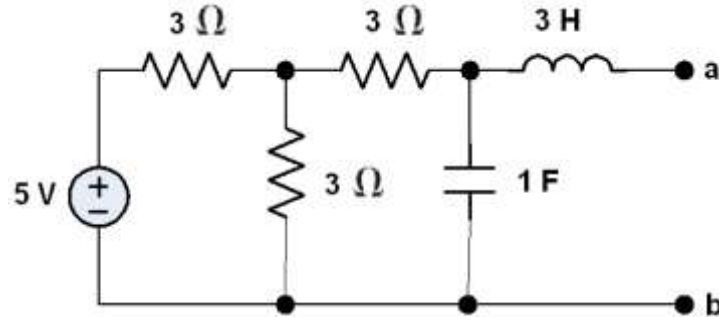Problem No 1:**Part (a):**


For the circuit shown below, under DC conditions, the voltage between terminals a-b is:



- (i) 0 V, (ii) 5 V, (iii) 1.667 V, (iv) 2.5 V,
 (v) 0.833 V, (vi) 7.5 V, (vii) 2 V, (viii) 0.556 V.

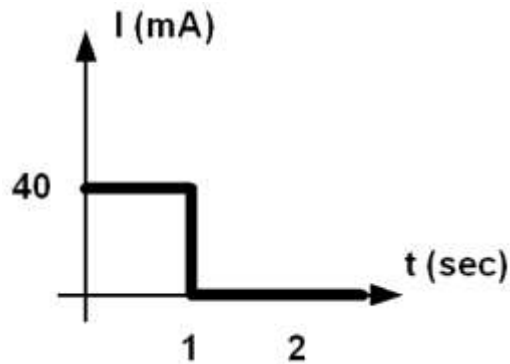Part (b):


The current through an initially uncharged $4 \mu\text{F}$ capacitor is shown in Figure 3. The voltage across the capacitor terminals at $t=1.5$ seconds is:



- (i) 10 V, (ii) 0 V, (iii) 10 mV, (iv) 15 KV,
 (v) 10 KV, (vi) 15 mV, (vii) 15 V, (viii) 30 V.

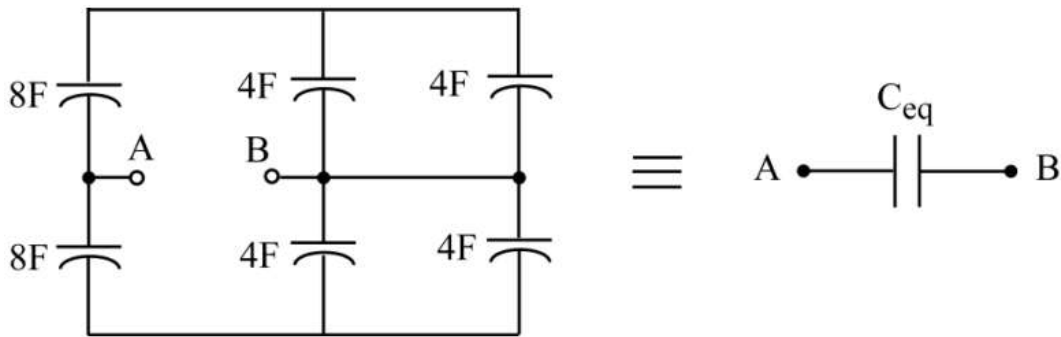Part (c):


Compute the equivalent capacitance (C_{eq}) of the capacitor network shown below.



- (i) 2 F, (ii) 4 F, (iii) 6 F, **(iv) 8 F,**
 (v) 10 F, (vi) 12 F, (vii) 14 F, (viii) 16 F.

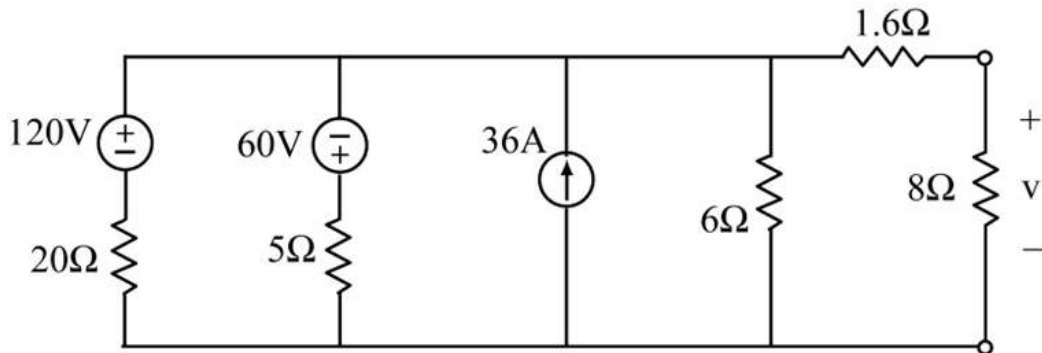Part (d):


Using source transformations, find the voltage “v” (in V):



- (i) 12, (ii) 24, (iii) 36, **(iv) 48,**
 (v) 56, (vi) 60, (vii) 72, (viii) 84.

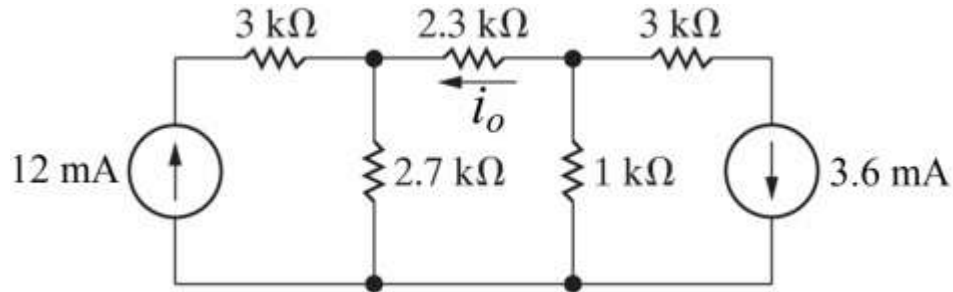Part (e):


For the circuit shown below, find the current i_o :



- (i) 6 mA, (ii) -6 mA, (iii) 4.8 mA, (iv) -4.8 mA,
 (v) 3 mA, (vi) -3 mA, (vii) 2.4 mA, (viii) -2.4 mA.

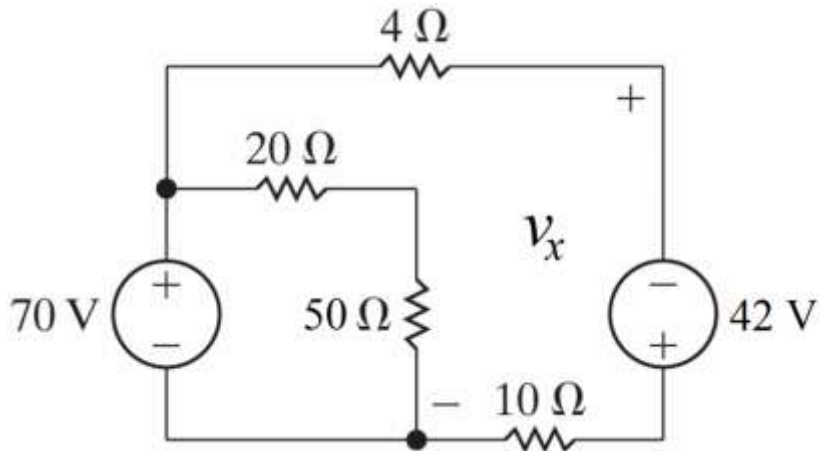Part (f):


Find the voltage v_x in the following circuit (Hint: Use the principle of superposition)



- (i) 80 V, (ii) -80 V, (iii) 62 V, (iv) -62 V,
 (v) 13 V, (vi) -13 V, (vii) 38 V, (viii) -38 V.

Problem No 2:

Given the following circuit:

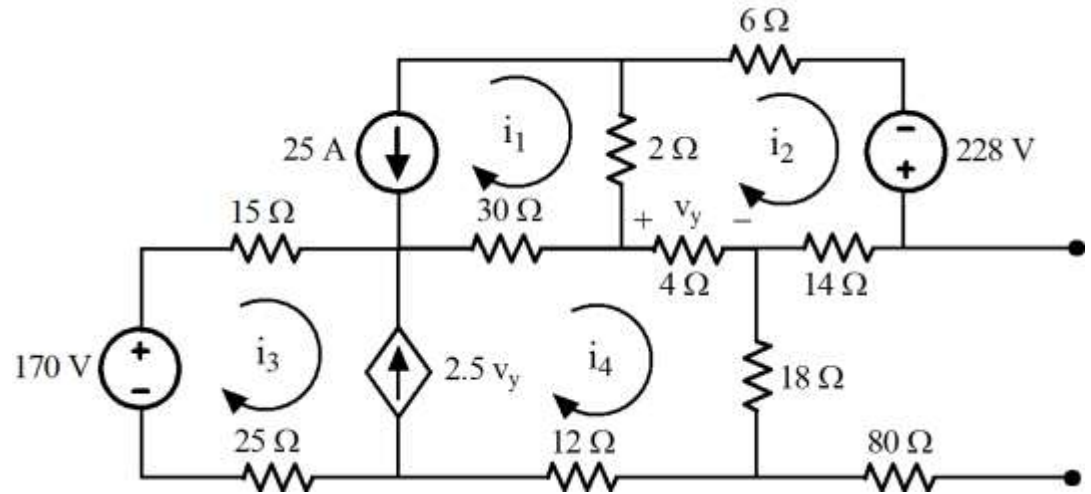

- a) Find all the necessary equations to solve for the mesh currents i_1 , i_2 , i_3 , and i_4 . [**Note: In this part do not simplify or solve any system of equations**]

Solution:

Current Source 25A:

$$i_1 = -25$$

Current Source $2.5v_y$:

$$i_4 - i_3 = 2.5 v_y$$

KVL in mesh 2:

$$2(i_2 + 25) + 6i_2 - 228 + 14i_2 + 4(i_2 - i_4) = 0$$

Super Mesh m3+m4:

$$-170 + 15i_3 + 30(i_4 + 25) + 4(i_4 - i_2) + 18i_4 + 12i_4 + 25i_3 = 0$$

Help Equation for dependent source:

$$v_y = 4(i_4 - i_2)$$

- b) Simplify the equations in part(a) and calculate the values of the mesh currents i_1 , i_2 , i_3 , and i_4 .

Solution:

Simplify the above equation into a matrix form, then solve for the mesh currents

$$\begin{bmatrix} 26 & 0 & -4 \\ -10 & 1 & 9 \\ -4 & 40 & 64 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 178 \\ 0 \\ -580 \end{bmatrix}$$

$$\begin{aligned} i_1 &= -25 \text{ A}, & i_2 &= 9 \text{ A}, \\ i_3 &= -36 \text{ A}, & i_4 &= 14 \text{ A}. \end{aligned}$$

- c) Find the expressions and the values of the power delivered by the two current sources. The expressions will be as functions of the mesh currents (i_1 , i_2 , i_3 , and i_4).

Solution:


$$\begin{aligned} P_{\text{delivered by the 25 A Current Source}} &= [v][i] \\ &= -[2(i_2 - i_1) + 30(i_4 - i_1)][i_1] \\ &= -[-32i_1 + 2i_2 + 30i_4][i_1] \\ &= [2(i_2 + 25) + 30(i_4 + 25)][25] \\ &= 30.95 \text{ kW} \end{aligned}$$

$$\begin{aligned} P_{\text{delivered by the 2.5 v}_y \text{ Current Source}} &= [v][i] \\ &= [30(i_4 - i_1) + 4(i_4 - i_2) + 30i_4][2.5(4)(i_4 - i_2)] \\ &= [-30i_1 - 4i_2 + 64i_4][10i_4 - 10i_2] \\ &= [30(i_4 + 25) + 4(i_4 - i_2) + 30i_4][2.5(4)(i_4 - i_2)] \\ &= 80.5 \text{ kW} \end{aligned}$$


Problem No 3:

For the circuit shown below:

- Find the value of the resistor R so that maximum power is transferred to it.
- Find the value of maximum power that is transferred to the resistance R .

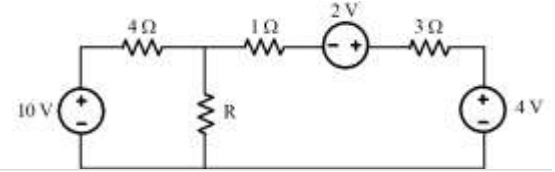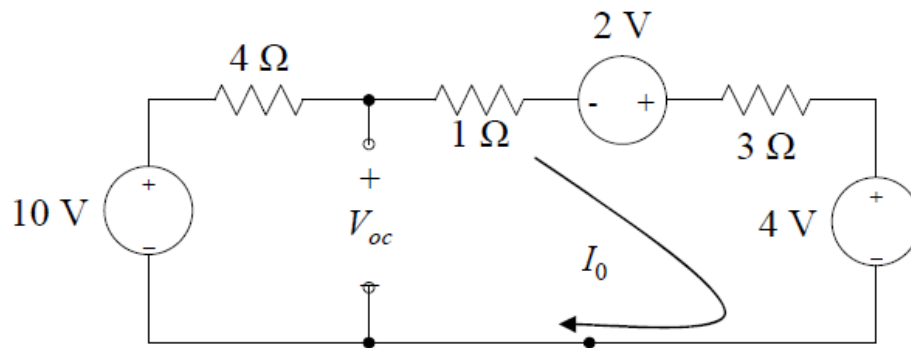**Solution**

- Thevenin's equivalent at the terminals of R must be found.




KVL:

$$-10 - 2 + 4 + 8I_0 = 0$$

$$\Rightarrow I_0 = 1 \text{ A}$$

$$\Rightarrow V_{oc} = 10 - 4I_0 = 6 \text{ V}$$

R_{Th} :

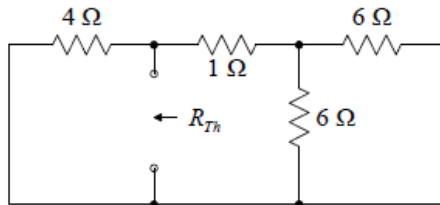


$$R_{Th} = 4\Omega \parallel (1 + 6 \parallel 6)\Omega = 4\Omega \parallel 4\Omega = 2\Omega$$

\therefore For maximum power transfer $R = R_{Th} = 2\Omega$

(b) Maximum power transferred: $P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = 4.5 \text{ W}$

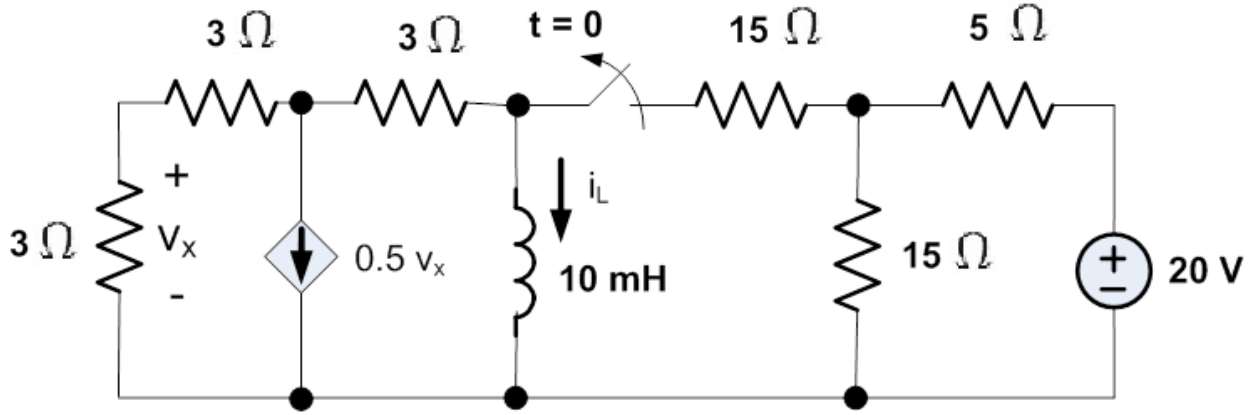Problem No 4:

In the circuit shown in the Figure, the switch was closed for a long time. At time $t=0$, the switch was open. Find an expression for the current $i_L(t)$ inside the inductor for $t \geq 0$.



Sol.



before opening the switch,

$$z_1 = \frac{20}{5+7.5} = 1.6 \text{ A}$$

$$z_L(0) = \frac{z_1}{2} = 0.8 \text{ A}$$

after opening the switch

$$E = \frac{L}{R_{eq}}$$

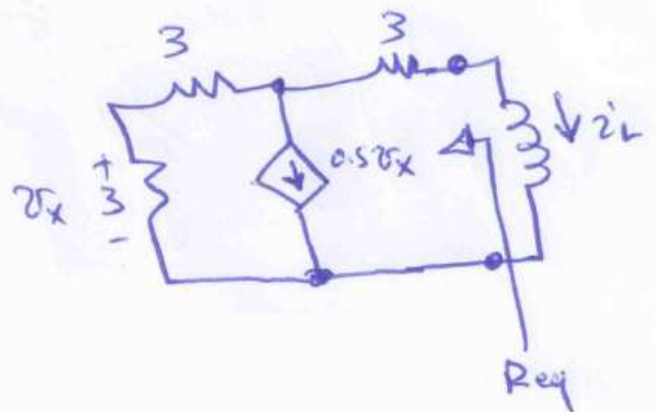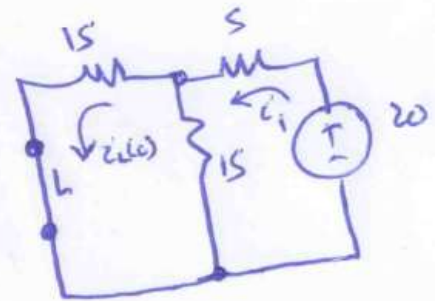

to find Req;

$$1 = 3i_x + 6i_2$$


$$i_x = 0.5v_x + i_2$$

$$v_x = 3i_2$$

$$\Rightarrow i_x = 1.5i_2 + i_2 = 2.5i_2$$

$$\Rightarrow 1 = 7.5i_2 + 6i_2 \Rightarrow i_2 = \frac{2}{27} \text{ A}$$

$$i_x = \frac{5}{27} \text{ A}$$

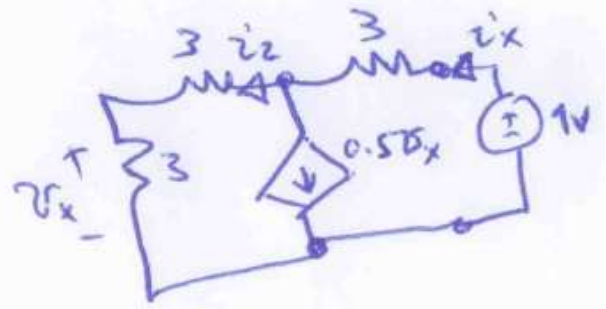

$$R_{eq} = \frac{1}{i_x} = \frac{27}{5} = \underline{\underline{5.4 \Omega}}$$

$$\Rightarrow \tau = \frac{L}{R_{eq}} = \frac{10\text{m}}{5.4} = \underline{\underline{1.852 \text{ m Sec.}}}$$

$$\Rightarrow i_L(t) = i_L(0) e^{-\frac{t}{\tau}} \text{ A, } t \geq 0$$

$$i_L(t) = 0.8 e^{-539.96t} \text{ A, } t \geq 0$$

