

EE 202-Winter 2013-2014 (132)

HW5

Prepared by: Dr. Mohammad S. Sharawi

Due 13/4/2014

**Q1** A voltage of  $60 \cos 4\pi t$  V appears across the terminals of a 3-mF capacitor. Calculate the current through the capacitor and the energy stored in it from  $t = 0$  to

$t = 0.125$  s.

**Q2** Find the equivalent capacitance between terminals  $a$  and  $b$  in the circuit of Fig. 1. All capacitances are in  $\mu\text{F}$ .

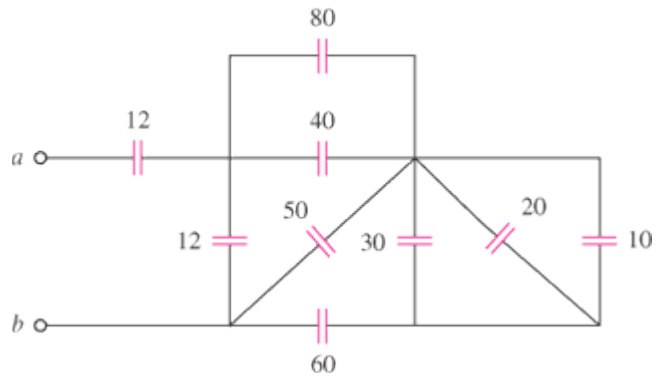


Figure 1

**Q3** In the circuit in Fig. 2, let  $i_s = 30e^{-2t}$  mA and  $v_1(0) = 50$  V,  $v_2(0) = 20$  V. Determine: (a)  $v_1(t)$  and  $v_2(t)$ , (b) the energy in each capacitor at  $t = 0.5$  s.


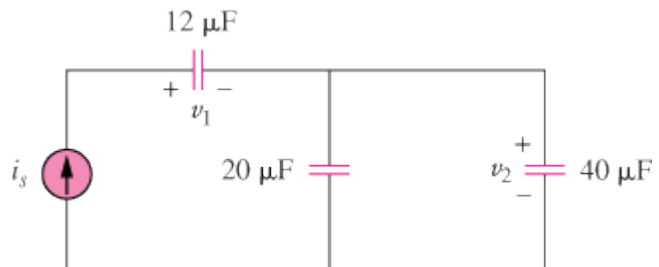



Figure 2

**Q4** Determine  $L_{eq}$  at terminals  $a$ - $b$  of the circuit in Fig. 3.

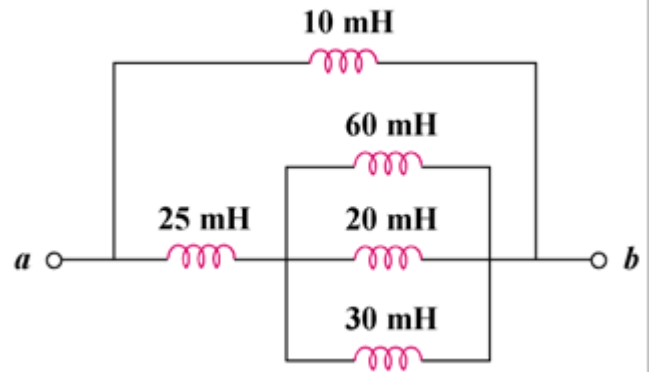


**Figure 3**

**Q5** Determine  $L_{eq}$  that may be used to represent the inductive network of Fig. 4 at the terminals.

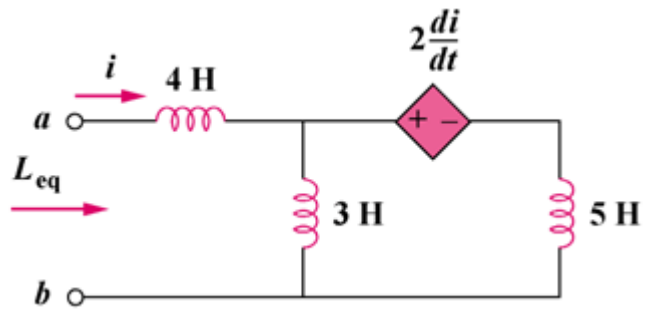


**Figure 4**

**Q6** Find the time constant of each of the circuits in Fig. 5.

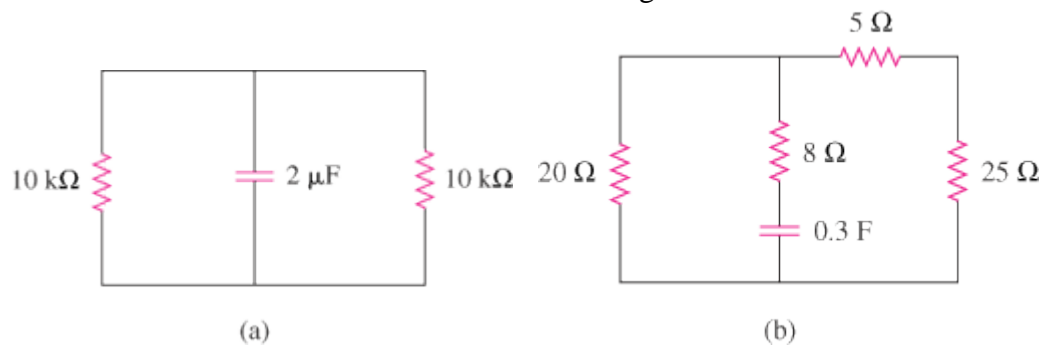


**Figure 5**

**Q7** In the circuit of Fig. 6,  $v(0) = 20$  V. Find  $v(t)$  for  $t > 0$ .

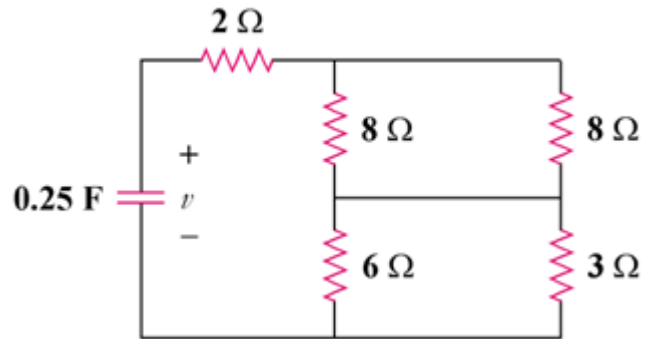

**Figure 6**

**Q8** Consider the circuit of Fig. 7. Find  $v_0(t)$  if  $i(0) = 2$  A and  $v(t) = 0$ .

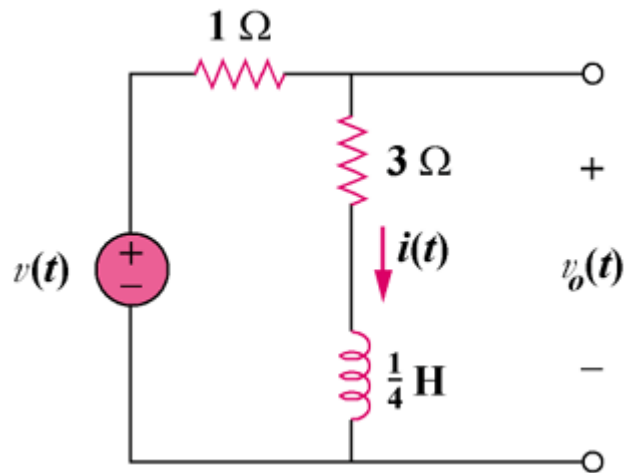

**Figure 7**