# KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS Electrical Engineering Department

## EE 208 ELECTRICAL SYSTEMS

## Experiment # 3 SERIES & PARALLEL CONNECTIONS, CDR & VDR

#### **OBJECTIVE:**

- 1 To **study** series and parallel connections of electrical elements experimentally.
- 2 To experimentally **verify** the current divider rule (**CDR**) for parallel circuits and the voltage divider rule (**VDR**) for series circuits.

**APPARATUS:** DC Power Supply

Ohmmeter, DC Voltmeter and DC Ammeter

Carbon Resistors:  $100 \Omega$ ,  $150 \Omega$ ,  $220 \Omega$  and  $330 \Omega$ .

#### THEORY:

#### > Series Conditions:

By definition, a series connection between any two electrical elements is such that the **same current passes through both elements**. For example element e1, e2, and e3 in Figure 1 are in series since the same current I1 passes through them.

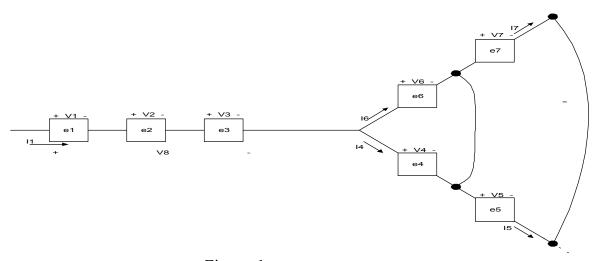


Figure 1

#### Parallel Connections:

By definition, a parallel connection between any two electrical elements is such that **the voltage is the same across both the elements**. For example, elements e4 and e6 in Figure 1 are in parallel, since the same voltage ( $V_4 = V_6$ ) is across both of them. Also, element e5 and e7 are in parallel for a similar reason.

#### • Voltage Divider Rule (VDR):

For a discussion of VDR, refer to your textbook. As an example of VDR, in Figure 1, if  $e1 = R_1$ ,  $e2 = R_2$ , and  $e3 = R_3$ , then:

$$V_1 = \frac{R_1}{R_1 + R_2 + R_3} V_8 \tag{1}$$

$$V_2 = \frac{R_2}{R_1 + R_2 + R_3} V_8 \tag{2}$$

#### • Current Divider Rule (CDR):

For a discussion of CDR, refer to your textbook. As an example of CDR in Figure 1, If  $e4=R_4$  and  $e6=R_6$ , then:

$$I_4 = \frac{R_6}{R_4 + R_6} I_1 \tag{3}$$

For I<sub>5</sub> and I<sub>7</sub>, CDR can be applied as


$$I_5 = \frac{R_7}{R_5 + R_7} (I_4 + I_6) \tag{4}$$

$$I_7 = \frac{R_5}{R_5 + R_7} (I_4 + I_6) \tag{5}$$

This is valid, since  $I_4$  +  $I_6$  is the total current passing though the parallel combination in this case.
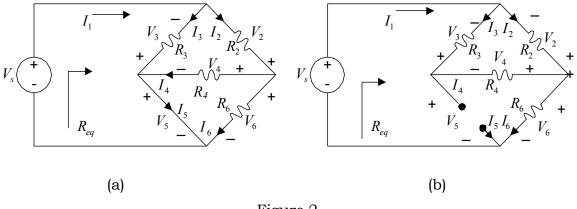
#### PROCEDURE:

1- **Check the values** of resistors used in the circuit of Figure 2, using the Ohmmeter. Record the values in Table 1.



- Figure 2
- 2- **Connect** the circuit of **Figure 2a** and adjust the supply **voltage Vs to 10** V, using the DC voltmeter.
- 3- Measure the entire unknown voltages and currents shown. Record their values in Table 2.

- 4- Measure Req using an Ohmmeter and record its values in Table 2.
- 5- **Connect** the circuit of **Figure 2b** and adjust the supply voltage **Vs to 10 V**, using the DC voltmeter.
- 6- **Measure the entire unknown voltages and currents shown**. Record their values in Table3 (recall that when measuring current by an ammeter, <u>the ammeter should be placed in series with the element in which the current passes</u>. Keep this fact in mind when measuring I<sub>5</sub>.)
- 7- **Measure Req.** and record its value in Table 3.

#### **REPORT:**

- 1- For the circuit shown in Figure 2a and Figure 2b, calculate: the unknown voltages and currents shown and the equivalent resistance seen by  $V_s$ . Record your results in Table 1 and Table 2.
- 2- Compare the theoretical and experimental values of voltages and currents and the equivalent resistance of both circuits. Calculate the percent errors.

#### **QUESTIONS:**

- > Referring to the circuit of **Figure 2a**:
  - 1. Are  $R_4$  and  $R_6$  in parallel or in series?
  - 2. Are  $R_3$  and  $R_4$  in parallel or in series?
  - 3. Are Vs and  $R_3$  in parallel or in series?
  - 4. Are Vs and  $R_6$  in series or in parallel?
  - 5. Are Vs and R<sub>eq</sub> in parallel or in series?
  - 6. Is VDR applicable for applicable for R<sub>3</sub> and R<sub>4</sub>?
  - 7. Is CDR applicable for  $R_4$  and  $R_6$ ?
  - 8. Is the parallel combination of  $R_4$  and  $R_6$  in series or in parallel with  $R_2$ ?

Justify your answer in each case by referring to the experimental results.

> Referring to circuit of **Figure 2b**:

**Questions 9-15: Answer** questions 1-7 respectively for the circuit of Figure 2b.

16. Is the series combination of  $R_3$  and  $R_4$  in series or in parallel with  $R_2$ ?

Justify your answer in each case by referring to the experimental results.

## **EXPERIMENT # 3 Laboratory Report**

Name:	I.D. I	Lab.	Section:	

## TABLE 1

## **Resistor Values:**

Resistor	$R_2$	R <sub>3</sub>	R <sub>4</sub>	R <sub>6</sub>	
Nominal Value (Ohm)	100	220	150	330	
Ohmmeter reading					

## TABLE 2

## Circuit of Figure 2a:

Unknown	$I_1$	$I_2$	$I_3$	<b>I</b> 4	$I_5$	I <sub>6</sub>	$V_2$	V <sub>3</sub>	$V_4$	V <sub>5</sub>	V <sub>6</sub>	$R_{\rm eq}$
Theory												
Experiment												
% Error												

## TABLE 3

## Circuit of Figure 2b

Unknown	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$V_2$	$V_3$	V <sub>4</sub>	$V_5$	$V_6$	$R_{\rm eq}$
Theoretical												
Experimental												
% Error												