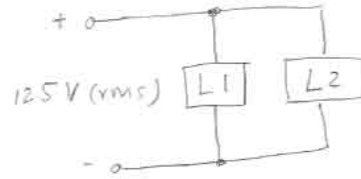


HW #14

①

10.20

$$P_t = 4500 \text{ W}, (Pf)_t = 0.96 \text{ (leading)}$$



$$\frac{P_t}{S_t} = (Pf)_t \Rightarrow S_t = \frac{P_t}{(Pf)_t} = \frac{4500}{0.96}$$

$$= 4687.5 \text{ VA}$$

$$\theta_t = -\cos^{-1}(0.96) = -16.26^\circ$$

$$\therefore \bar{S}_t = 4687.5 \angle -16.26^\circ \text{ VA} = 4500 - j1312.48 \text{ VA}$$

$$P_1 = 2700 \text{ W}, (Pf)_1 = 0.80 \text{ (lagging)}$$

$$\therefore S_1 = \frac{P_1}{(Pf)_1} = \frac{2700}{0.80} = 3375 \text{ VA}$$


$$\theta_1 = +\cos^{-1}(0.80) = 36.87^\circ$$

$$\therefore \bar{S}_1 = 3375 \angle 36.87^\circ = 2700 + j2025 \text{ VA}$$

$$\begin{aligned} \bar{S}_2 &= \bar{S}_t - \bar{S}_1 = 4500 - j1312.48 - (2700 + j2025) \\ &= 1800 - j3337.48 = 3791.94 \angle -61.66^\circ \end{aligned}$$

$$\therefore (Pf)_2 = \cos 61.66^\circ = 0.4747 \text{ (leading)}$$

10.29

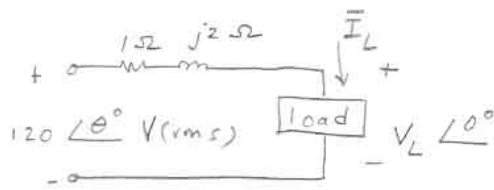

a)  $S_L = 600 \text{ VA}$

$$\theta_L = + \cos^{-1} 0.8 = 36.87^\circ$$

$$\therefore \bar{S}_L = 600 \angle 36.87^\circ \text{ VA}$$

$$\text{since } \bar{V}_L = V_L \angle 0^\circ \Rightarrow \theta_{L_V} = 0^\circ, \theta_{L_I} = -36.87^\circ$$

$$\therefore \bar{I}_L = I_L \angle -36.87^\circ \text{ A (rms)}$$

$$\begin{aligned} \bar{S}_L &= \bar{I}_L^* \bar{V}_L = (I_L \angle 36.87^\circ)(V_L \angle 0^\circ) \\ &= 600 \angle 36.87^\circ \end{aligned}$$

$$\therefore I_L V_L = 600 \quad (1)$$

$$\text{But } \bar{I}_L = \frac{120 \angle \theta^\circ - V_L \angle 0^\circ}{(1 + j2)}$$

$$(1 + j2) \bar{I}_L = 120 \angle \theta^\circ - V_L \angle 0^\circ, \text{ using eqn. (1)}$$

$$(1 + j2) \frac{600}{V_L} \angle -36.87^\circ = 120 \angle \theta^\circ - V_L \angle 0^\circ$$

$$(1 + j2) \frac{600}{V_L} (0.8 - j0.6) = 120 \cos \theta^\circ + j120 \sin \theta^\circ - V_L$$

$$\frac{600}{V_L} (0.8) + \frac{2(600)(0.6)}{V_L} + j \left( \frac{2(600)(0.8)}{V_L} - \frac{600(0.6)}{V_L} \right)$$

$$= (120 \cos \theta^\circ - V_L) + j120 \sin \theta^\circ$$

equating the real & imaginary parts of the previous eqn.  $\Rightarrow$

$$\frac{480}{V_L} + \frac{720}{V_L} = 120 \cos \theta^\circ - V_L \quad (2)$$

$$\frac{960}{V_L} - \frac{360}{V_L} = 120 \sin \theta^\circ \quad (3)$$

$\Downarrow$

$$\frac{1200}{V_L} + V_L = 120 \cos \theta^\circ \quad (4)$$

$$\frac{600}{V_L} = 120 \sin \theta^\circ \quad (5)$$

$$\text{From (5)} \Rightarrow \sin \theta^\circ = \frac{5}{V_L} \Rightarrow \cos \theta^\circ = \sqrt{1 - \frac{25}{V_L^2}} \quad (6)$$

Substituting (6) into (4)  $\Rightarrow$

$$\frac{1200}{V_L} + V_L = 120 \sqrt{1 - \frac{25}{V_L^2}}$$

$\Downarrow$

$$\frac{1440000}{V_L^2} + 2400 + V_L^2 = 14400 \left(1 - \frac{25}{V_L^2}\right)$$

$$\therefore 1440000 + 2400V_L^2 + V_L^4 = 14400V_L^2 - 360000$$

$$\therefore V_L^4 - 12000V_L^2 + 18 \times 10^5 = 0 \quad (7)$$

solving ⑦  $\Rightarrow V_L = 108.85 \text{ V (rms)}$

or  $V_L = 12.326 \text{ V (rms)}$


if  $V_L = 108.85 \text{ V (rms)} \Rightarrow \sin \theta^\circ = \frac{5}{V_L} = 0.0459$

$\therefore \theta = 2.63^\circ$  ,  $I_L = \frac{600}{V_L} = 5.51 \text{ A (rms)}$

if  $V_L = 12.326 \text{ V (rms)} \Rightarrow \sin \theta^\circ = \frac{5}{V_L} = 0.406$


$\therefore \theta = 23.95^\circ$  ,  $I_L = \frac{600}{V_L} = \frac{600}{12.326} = 48.68 \text{ A rms}$

b)

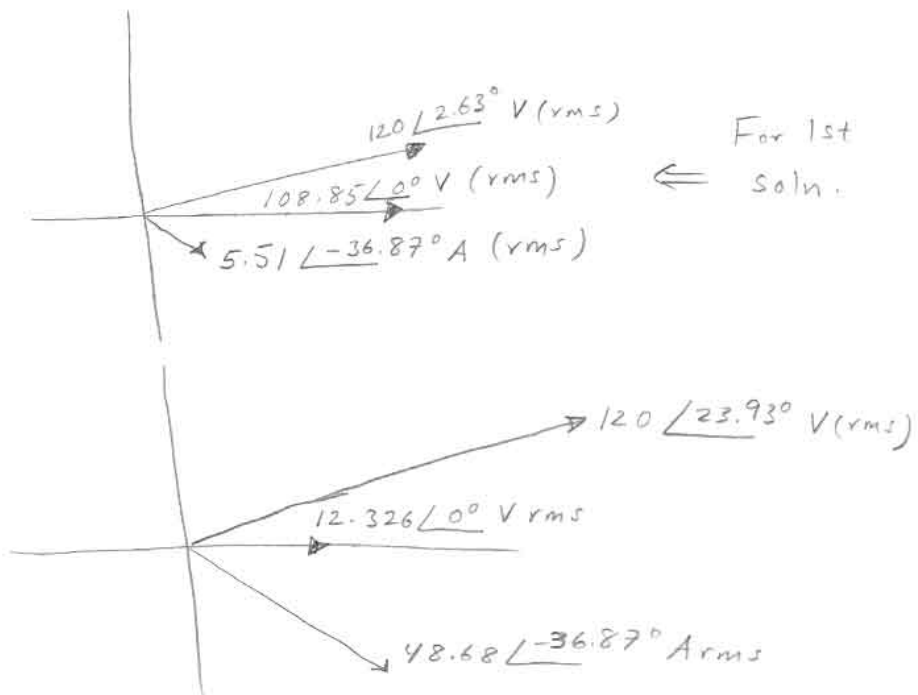

10.31

(5)

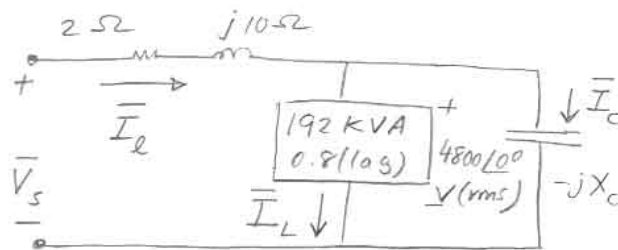

$$S_L = 192000 = I_L V_L = I_L (4800) \Rightarrow I_L = 40 \text{ A rms}$$

$$\theta_L = + \cos^{-1}(0.8) = 36.87^\circ$$

$$\therefore \bar{I}_L = 40 \angle -36.87^\circ = 32 - j24 \text{ A (rms)}$$

$$\bar{I}_c = \frac{4800 \angle 0^\circ}{-jX_c} = \frac{4800}{X_c} \angle 90^\circ = I_c \angle 90^\circ = jI_c$$

$$\bar{I}_l = \bar{I}_L + \bar{I}_c = 32 - j24 + jI_c = 32 + j(I_c - 24)$$

$$\bar{V}_s = (2 + j10) \bar{I}_l + 4800$$

$$= (2 + j10) [32 + j(I_c - 24)] + 4800$$

$$= \left( \begin{array}{l} 64 - 10I_c + 240 \\ + 4800 \end{array} \right) + j(320 + 2I_c - 48)$$

$$= (5104 - 10I_c) + j(272 + 2I_c)$$

$$\therefore V_s^2 = (4800)^2 = (5104 - 10I_c)^2 + (272 + 2I_c)^2$$

Solving  $\Rightarrow I_c = 31.57 \text{ A (rms)}$  or

(6)

$$I_c = 939.51 \text{ A (rms)}$$

We choose  $I_c = 31.57 \text{ A (rms)}$  to reduce the line current.

$$\therefore I_c = \frac{4800}{X_c} = 31.57 \Rightarrow X_c = 152.04 \Omega$$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi(60)C} = 152.04$$



$\Downarrow$

$$C = 17.45 \mu\text{F}$$

10.33

(7)

a)

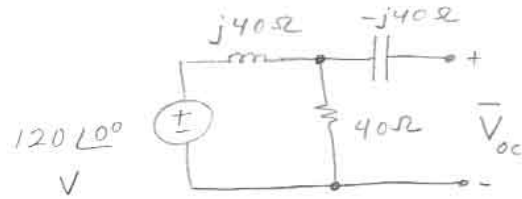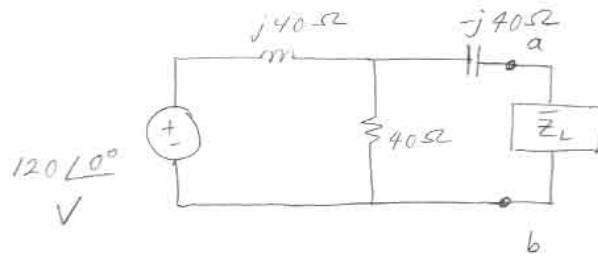

$$\bar{V}_{oc} = \left( \frac{40}{40 + j40} \right) (120 \angle 0^\circ) = 84.85 \angle -45^\circ \text{ V}$$


$$\bar{Z}_{th} = -j40 + (40 \parallel j40)$$

$$= 20 - j20 \Omega$$

$$\therefore \bar{Z}_L = \bar{Z}_{th}^* = 20 + j20 \Omega$$

$$b) P_{max} = \frac{V_{th}^2}{8R_{th}} = \frac{(84.85)^2}{8(20)} = 45 \text{ W}$$

10.35

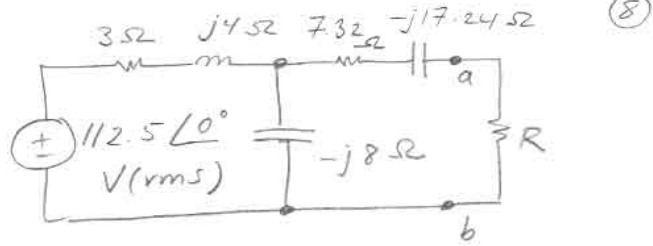


$$\begin{aligned}\bar{V}_{th} = \bar{V}_{oc} &= \left( \frac{-j8}{3+j4-j8} \right) (112.5 \angle 0^\circ) \\ &= \frac{(8 \angle -90^\circ)(112.5 \angle 0^\circ)}{5 \angle -53.13^\circ} = 180 \angle 36.87^\circ\end{aligned}$$

$$\begin{aligned}\bar{Z}_{th} &= 7.32 - j17.24 + (-j8 \parallel 3 + j4) \\ &= 15 - j15 \Omega = 21.21 \angle -45^\circ \Omega\end{aligned}$$

$$\therefore R = Z_{th} = 21.21 \Omega$$

b)

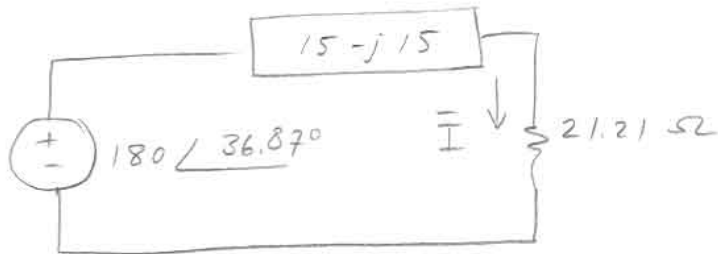

$$\bar{I} = \frac{180 \angle 36.87^\circ}{15 - j15 + 21.21} = \frac{180 \angle 36.87^\circ}{39.19 \angle -22.50^\circ}$$

$$\begin{aligned}I &= \frac{180}{39.19} = 4.59 \text{ A (rms)} \Rightarrow P_R = I^2 R \\ &= (4.59)^2 (21.21) = 447.4 \text{ W}\end{aligned}$$