
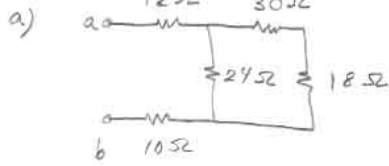


3.7

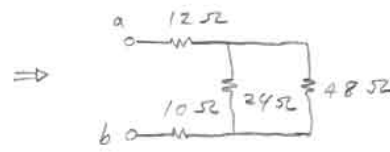

HW #3




1/9

$$\frac{24 \times 48}{24 + 48} = 16 \Omega \Rightarrow$$



$$\therefore R_{eq} = 38 \Omega$$

3.8

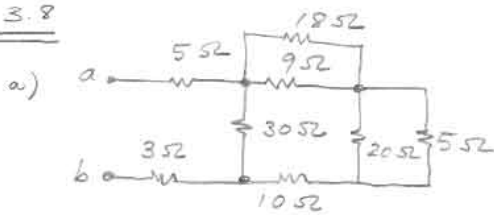



$$18 // 9 \neq 20 // 5$$

$$\downarrow$$



$$\frac{18 \times 9}{18 + 9} = 6 \Omega$$

$$\downarrow$$
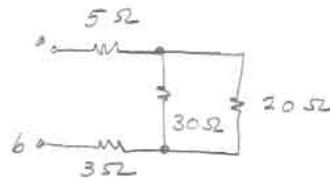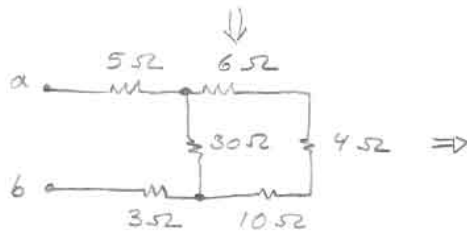
$$\frac{20 \times 5}{20 + 5} = 4 \Omega$$




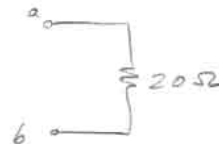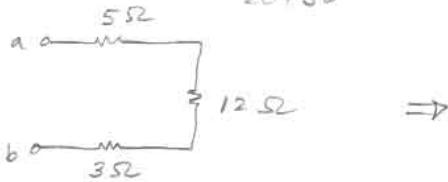
$$20 // 30 \Rightarrow \frac{20 \times 30}{20 + 30} = 12 \Omega \Rightarrow$$





$$\therefore R_{eq} = 20 \Omega$$


3.8 C

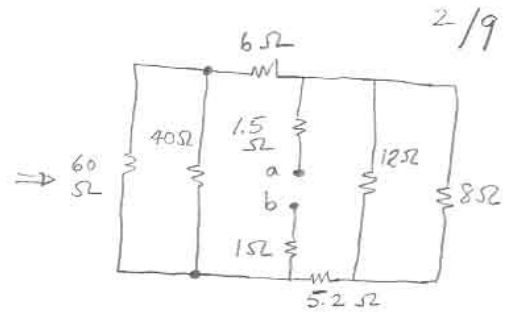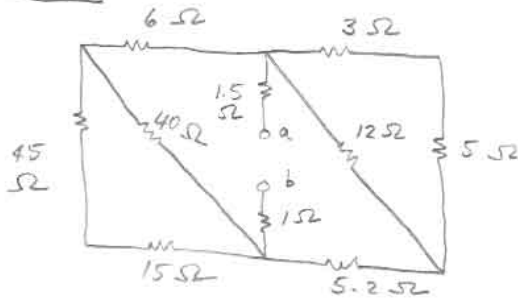
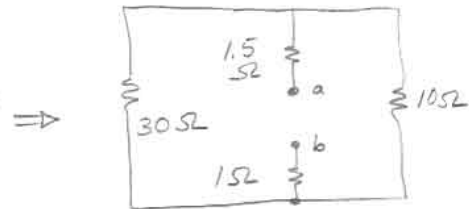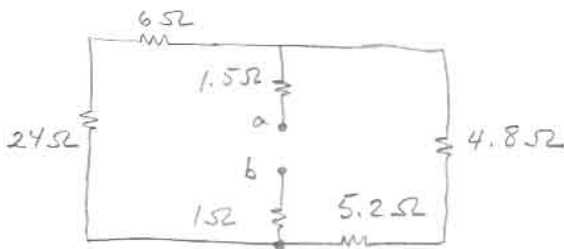
$$60 // 40 \Rightarrow \frac{60 \times 40}{60 + 40} = 24 \Omega, \quad 12 // 8 \Rightarrow \frac{12 \times 8}{12 + 8} = 4.8 \Omega$$


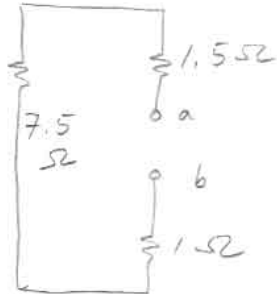
$$10 // 30 \Rightarrow \frac{10 \times 30}{10 + 30} = \frac{300}{40} = 7.5 \Omega$$





$\Rightarrow$




$\therefore R_{eq} = 10 \Omega$

3.9 a)


3/9

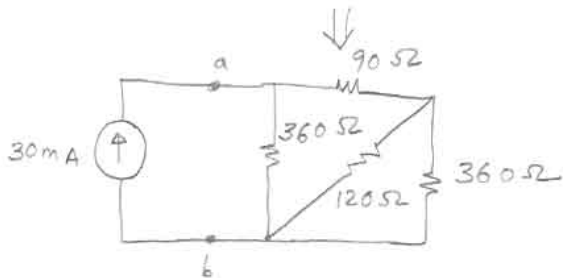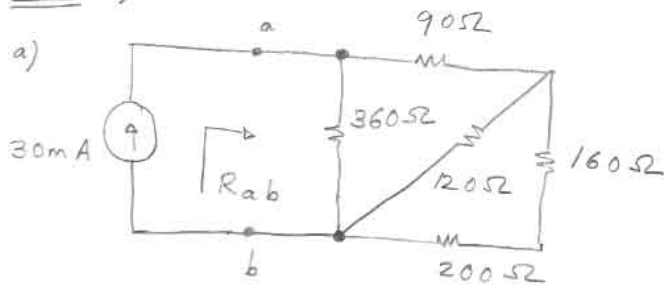

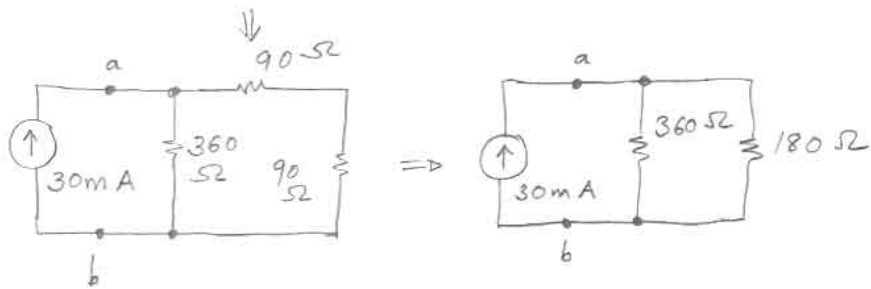
$$120 \parallel 160 \Rightarrow \frac{120 \times 160}{120 + 160} = 90 \Omega$$


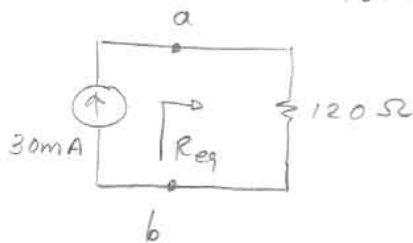
$$180 \parallel 360 \Rightarrow \frac{180 \times 360}{180 + 360} = 120 \Omega$$



$$\therefore R_{eq} = 120 \Omega$$

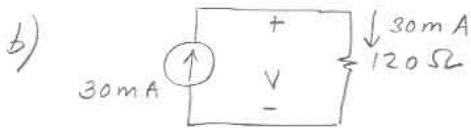





$$V = 30 \text{mA} \times 120 = 3.6 \text{V}$$

$$\therefore P_{30\text{mA}} = -iV = -(30 \times 10^{-3}) \times 3.6 = -0.108 \text{W}$$

$$\therefore \text{Power delivered by the source} = 0.108 \text{W}$$

3.25

4)

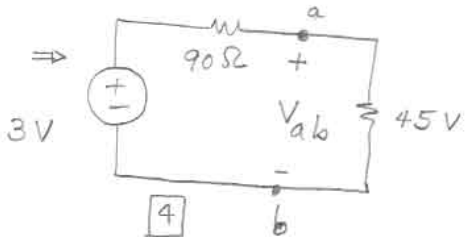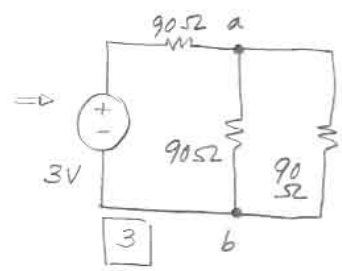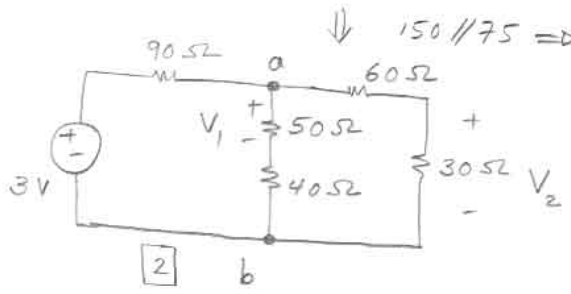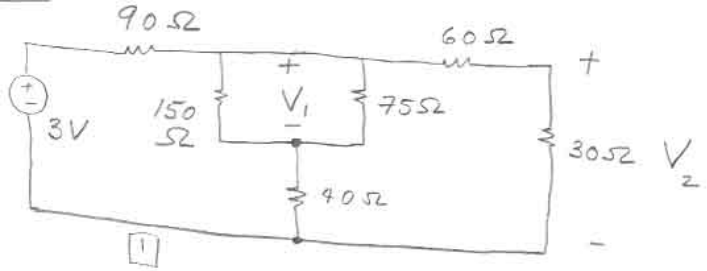


$90 \parallel 90 = \frac{1}{2} \times 90 = 45 \Omega$

VDR in circuit [4]  $\Rightarrow V_{ab} = \frac{45}{45+90} \times 3 = 1V$

" " " [2]  $\Rightarrow V_1 = \frac{50}{50+40} \times V_{ab}$   
 $= \frac{50}{90} \times 1 = \frac{5}{9} V$


" " " "  $\Rightarrow V_2 = \frac{30}{30+60} \times V_{ab} = \frac{30}{90} \times 1 = \frac{1}{3} V$

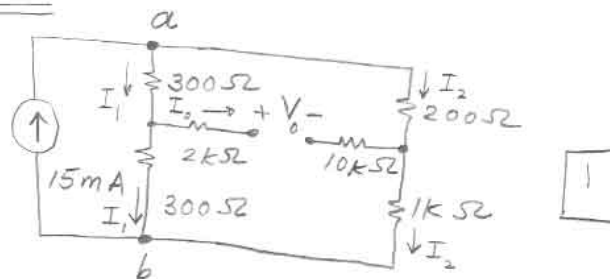$V_1 = \frac{5}{9} V \neq V_2 = \frac{1}{3} V$



$I_0 = 0 \text{ A}$  because no current passes through the "open circuit".

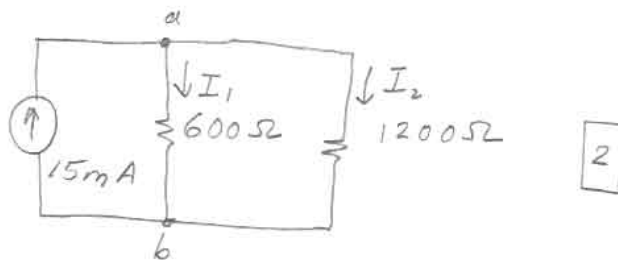- ∴ The current  $I_1$  passes through the two  $300\Omega$  resistors (i.e. they are in series).
- ∴ The current  $I_2$  passes through  $200\Omega$  &  $1k\Omega$  (i.e.  $200\Omega$  &  $1k\Omega$  are in series).



$$\text{CDR in circuit [2]} \Rightarrow I_1 = \frac{1200}{1200+600} \times 15\text{mA}$$

$$= 10\text{mA}$$

$$\text{" " " " } \Rightarrow I_2 = \frac{600}{1200+600} \times 15\text{mA}$$

$$= 5\text{mA}$$

3.26 (continued)

6/9

KVL in upper right circuit  $\square 1 \Rightarrow$

$$-V_o - 2000 I_o - 300 I_1 + 200 I_2 + 10000 I_o = 0$$

$$(I_o = 0, I_1 = 10 \text{ mA}, I_2 = 5 \text{ mA})$$

$$\therefore -V_o - 300(10 \times 10^{-3}) + 200(5 \times 10^{-3}) = 0$$

$$\boxed{\therefore V_o = -3 + 1 = -2 \text{ V}}$$

We can also apply KVL in the lower right circuit  $\square 1 \Rightarrow$

$$-300 I_1 + V_o + 1000 I_2 = 0$$

$$-300 \times (10 \times 10^{-3}) + V_o + 1000 \times (5 \times 10^{-3}) = 0$$







$$-3 + V_o + 5 = 0$$

$$\Rightarrow \boxed{V_o = -2 \text{ V}} \text{ (same answer).}$$

(again because  $I_o = 0$ , the voltage drops across  $2 \text{ k}\Omega$  &  $10 \text{ k}\Omega$  are both zero)

3.27

7/9

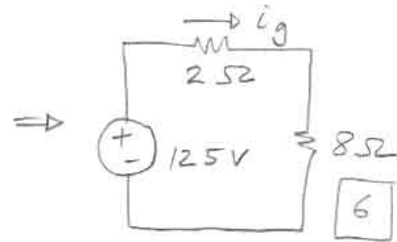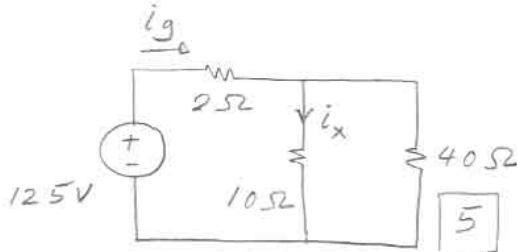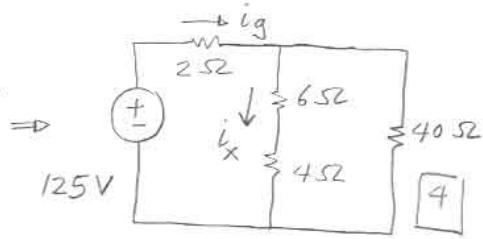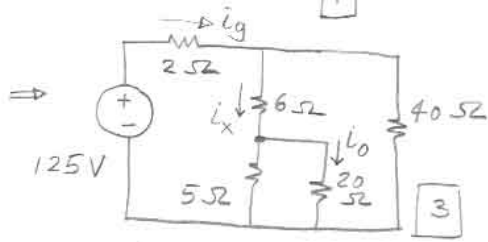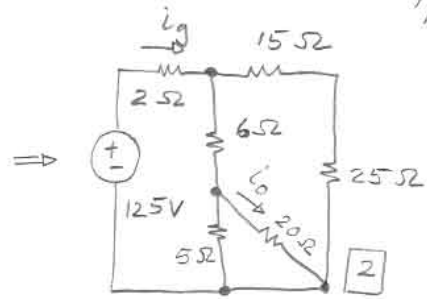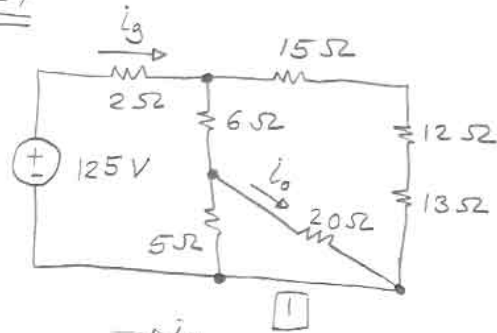

Using circuit [6]  $\Rightarrow i_g = \frac{125}{10} = 12.5 \text{ A}$


CDR in circuit [5]  $\Rightarrow i_x = \frac{40}{10+40} \times i_g$   
 $= \frac{40}{50} \times 12.5 = 10 \text{ A}$

CDR in circuit [3]  $\Rightarrow i_o = \frac{5}{5+20} \times i_x$   
 $= \frac{5}{25} (10) = 2 \text{ A}$


$\therefore i_o = 2 \text{ A}$

3.29

8/9

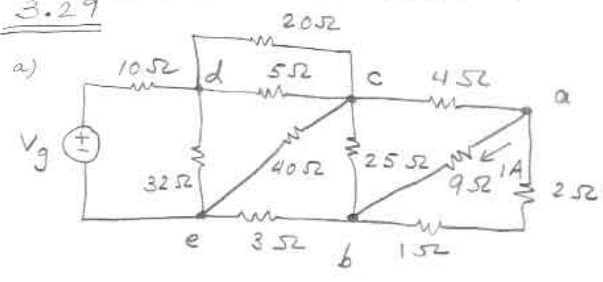

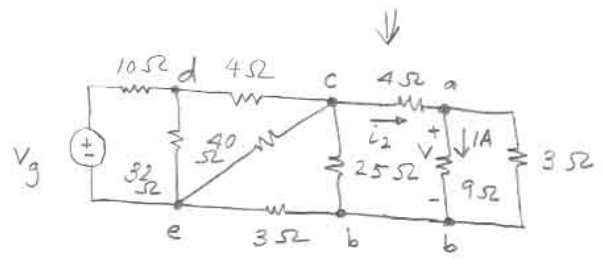
$$5 \parallel 20 = \frac{5 \times 20}{20 + 5} = 4.5 \Omega$$




$$V = 1 \times 9 = 9V$$
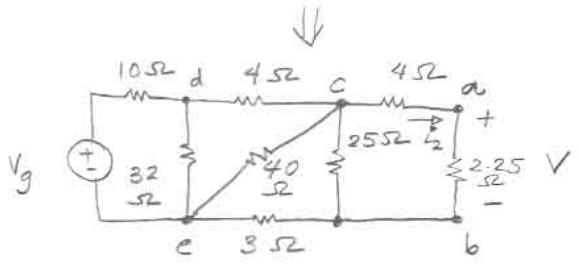
$$9 \parallel 3 = \frac{9 \times 3}{9 + 3} = 2.25 \Omega$$


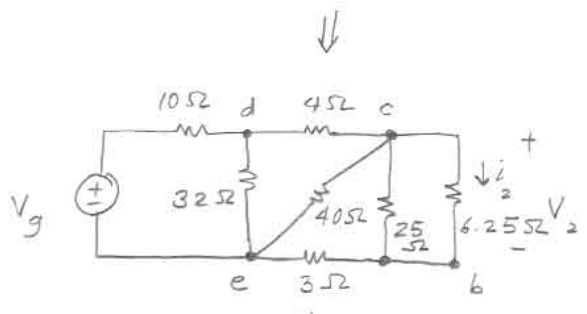
$$i_2 = \frac{V}{R} = \frac{9}{2.25} = 4A$$




$$V_2 = 6.25 \times i_2$$

$$= 6.25 \times 4 = 25V$$


$$25 \parallel 6.25 = \frac{25 \times 6.25}{25 + 6.25}$$

$$= 5 \Omega$$

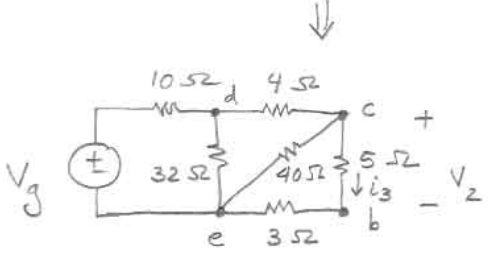

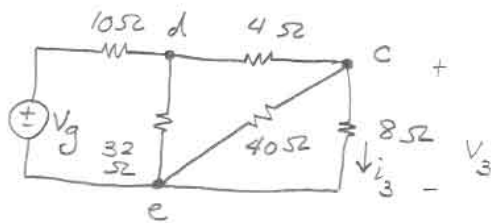
$$i_3 = \frac{V_2}{R} = \frac{25}{5} = 5A$$






$$V_3 = 8 i_3 = 8 \times 5 = 40 \text{ V} \quad 9/9$$
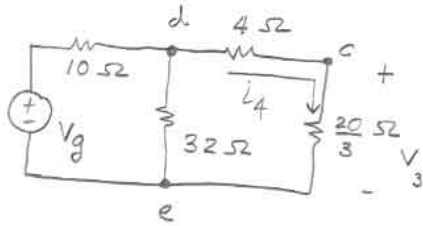
$$40 // 8 = \frac{40 \times 8}{40 + 8} = \frac{20}{3} \Omega$$




$$i_4 = \frac{V_3}{(20/3)} = 40 \times \frac{3}{20}$$

$$= 6 \text{ A}$$

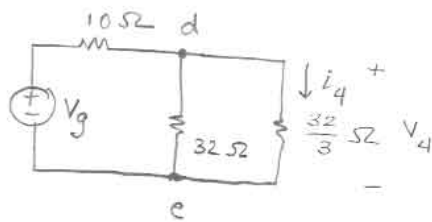

$$V_4 = \frac{32}{3} i_4 = \frac{32}{3} \times 6$$

$$= 64 \text{ V}$$

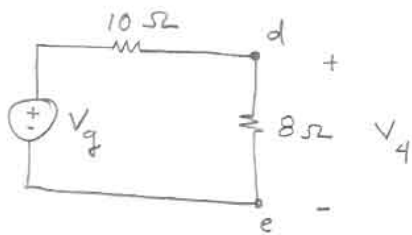

$$32 // \frac{32}{3} = \frac{32 \times \frac{32}{3}}{32 + \frac{32}{3}} = 8 \Omega$$

$$\text{KVL} \quad V_4 = \frac{8}{18} \times V_g \Rightarrow V_g = \frac{18}{8} V_4 = \frac{18}{8} \times 64$$

$$V_g = 144 \text{ V}$$