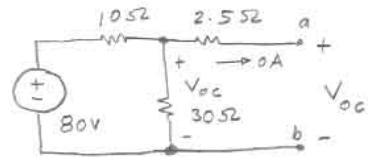



Q. 59



VDR \Rightarrow

$$V_{oc} = \frac{30}{10+30} \times 80 = 60V = V_{th}$$

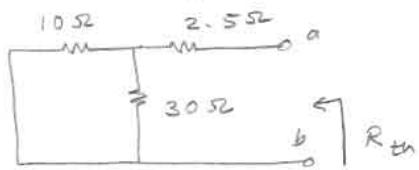Set all independent sources to zero \Rightarrow




$$R_{th} = 10 // 30 + 2.5$$


$$= \frac{300}{40} + 2.5$$

$$= 7.5 + 2.5 = 10 \Omega$$

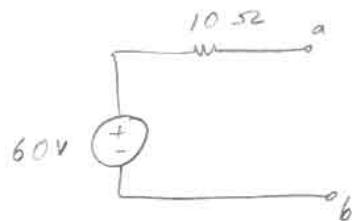\therefore Thévenin's Equivalent Circuit:



Q. 60

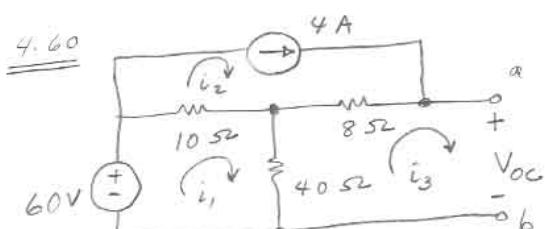

$$V_{oc} = ?$$


Use mesh analysis: $i_3 = 0$ A (because of the open circuit).
 $i_2 = 4$ A

KVL around mesh 1 $\Rightarrow -60 + 10(i_1 - 4) + 40i_1 = 0$

$$\therefore i_1 = 2 \text{ A}$$


$$V_{OC} = 4 \times 8 + 40i_1 = 32 + 40 \times 2 = 112 \text{ V} = V_{Th}$$

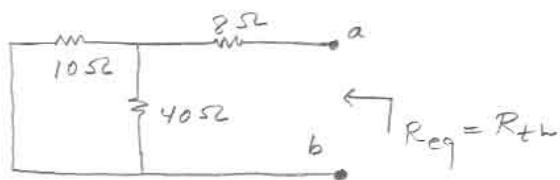To find R_{Th} , set all independent sources to zero:




$$R_{Th} = 10 \parallel 40 + 8 = \frac{400}{50} + 8 = 8 + 8 = 16 \text{ ohms}$$

Ans:

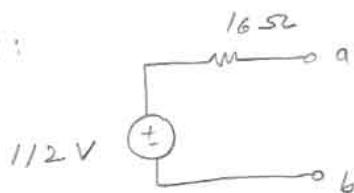

Q.61

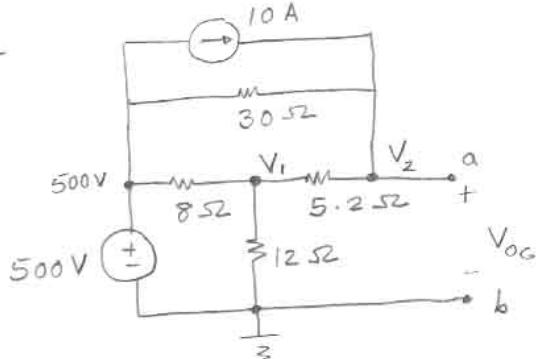

$$\text{KCL at node 1} \Rightarrow \frac{V_1 - 500}{8} + \frac{V_1}{12} + \frac{V_1 - V_2}{5.2} = 0$$

$$15.6(V_1 - 500) + 10.4V_1 + 24(V_1 - V_2) = 0$$

$$50V_1 - 24V_2 = 7800$$

$$25V_1 - 12V_2 = 3900 \quad (1)$$

KCL at node 2 =>

$$\frac{V_2 - V_1}{5.2} + \frac{V_2 - 500}{30} - 10 = 0$$


$$30(V_2 - V_1) + 5.2(V_2 - 500) - 1560 = 0$$

$$-30V_1 + 35.2V_2 = 4160$$

$$150V_1 - 176V_2 = -20800 \quad (2)$$

Solving for $V_2 = 425 = V_{th}$

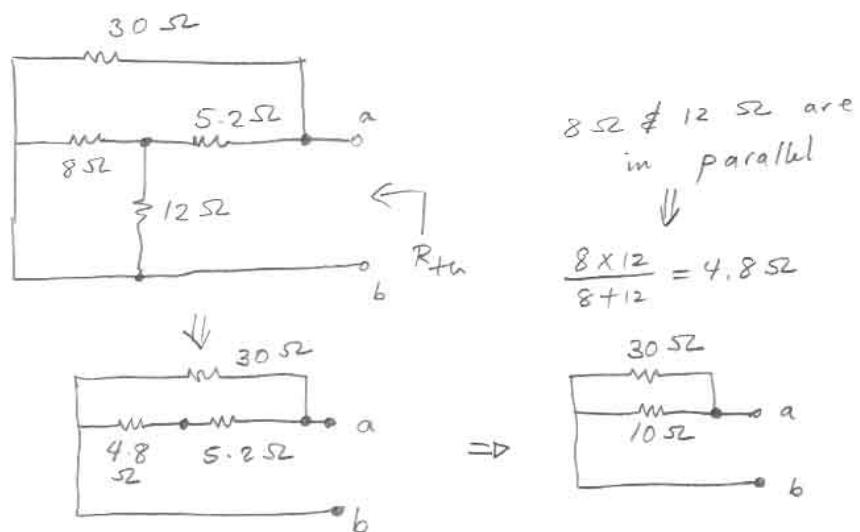
Set all independent sources to zero \Rightarrow



$$\therefore R_{th} = 30 \parallel 10 = \frac{30 \cdot 10}{40} = 7.5 \Omega$$


4

Ans:

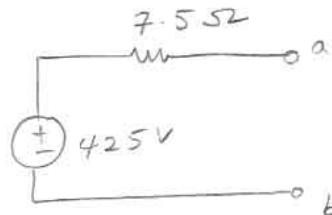

4.64

a)


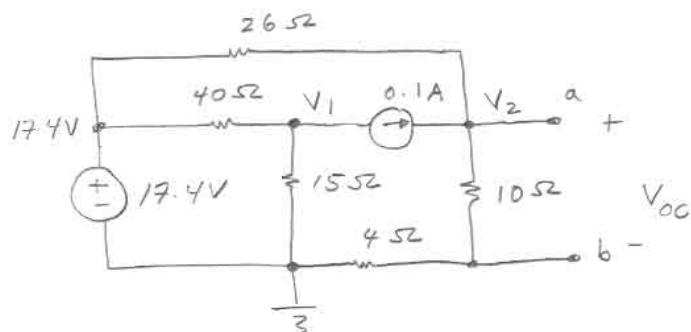


$$KCL \text{ at node } 2 \Rightarrow -0.1 + \frac{V_2}{14} + \frac{V_2 - 17.4}{26} = 0$$

(Decoupled equation)

$$\Rightarrow V_2 = 7V, \text{ Use VDR} \Rightarrow$$
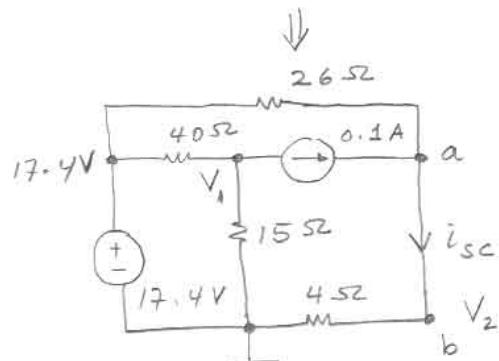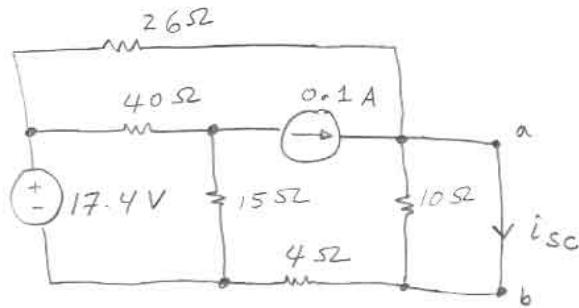
$$V_{oc} = \frac{10}{9+10} \times V_2 = \frac{10}{19} \times 7 = 5V = V_{th}$$




$$\text{KCL at node 2} \Rightarrow \frac{V_2}{4} + \frac{V_2 - 17.4}{26} - 0.1 = 0$$

$$(\text{Decoupled eqn.}) \Rightarrow V_2 = \frac{8}{3} \text{ V}$$


$$\therefore i_{sc} = \frac{V_2}{4} = \frac{8/3}{4} = \frac{8}{12} = \frac{2}{3} \text{ A.}$$

$$\therefore R_{th} = \frac{V_{oc}}{i_{sc}} = \frac{5}{2/3} = \frac{15}{2} = 7.5 \text{ ohms}$$

Ans.

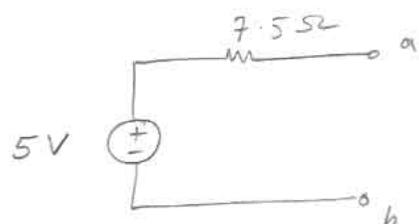


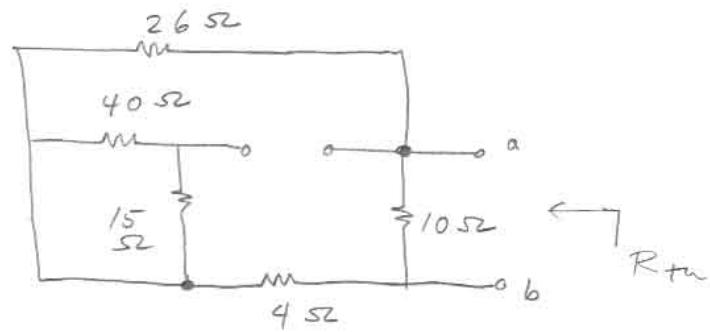b) To find R_{th} by removing the independent sources \Rightarrow




\downarrow
40 ohms & 15 ohms are in parallel
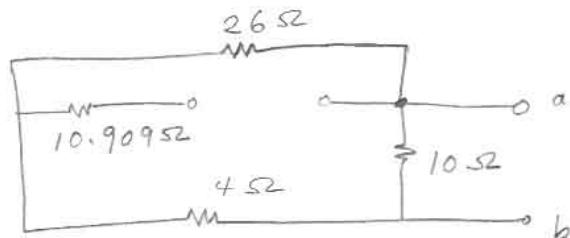
$$\frac{40 \times 15}{40 + 15} = 10.909 \text{ ohms}$$



\downarrow

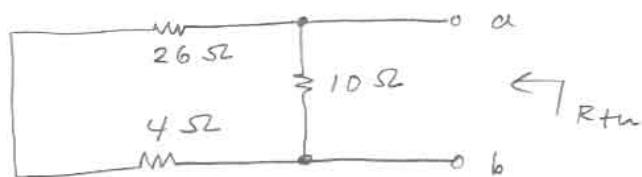

\downarrow


$$R_{th} = 30 \parallel 10 = 7.5 \text{ ohms}$$

(Same answer)

4.66


7

Model the battery using a Thvenin model:

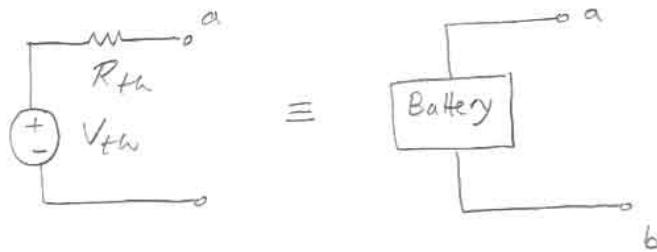


Then use the given information to find

V_{th} & R_{th} .

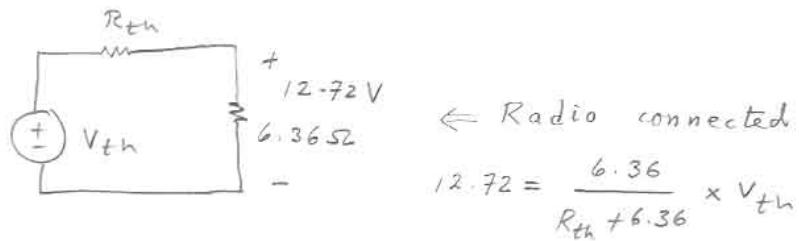
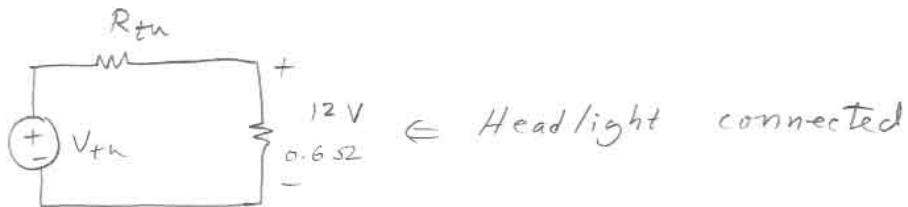
$$\therefore 12.72 R_{th} + 80.899 = 6.36 V_{th} \quad (1)$$




$$12 = \frac{0.6}{R_{th} + 0.6} \times V_{th} \Rightarrow 12 R_{th} + 7.2 = 0.6 V_{th} \quad (2)$$

$$\text{Solve } (1) \neq (2) \Rightarrow V_a = 12.8 \text{ V} \neq R_{th} = 40 \text{ m}\Omega$$

Use source transformation to find Norton
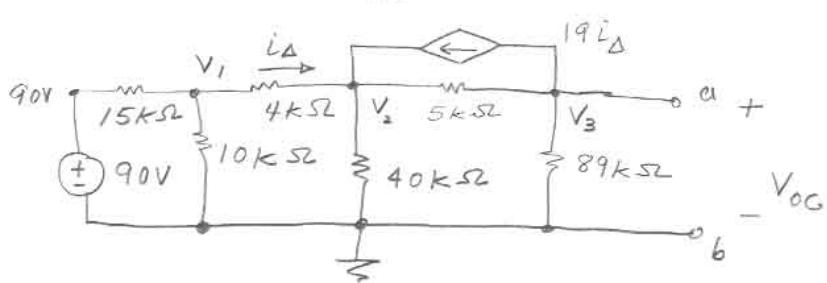
$$\text{Equivalent } \Rightarrow I_N = \frac{V_{th}}{R_{th}} = \frac{12.8}{40 \times 10^{-3}} = 320 \text{ A}, R_N = 40 \text{ m}\Omega.$$



KCL at nodes 1, 2, and 3 \Rightarrow

$$\frac{V_1 - 90}{15k} + \frac{V_1}{10k} + \frac{V_1 - V_2}{4k} = 0 \quad (1)$$

$$\frac{V_2 - V_1}{4k} + \frac{V_2}{40k} + \frac{V_2 - V_3}{5k} - 19i_\Delta = 0 \quad (2)$$



$$19i_\Delta + \frac{V_3 - V_2}{5k} + \frac{V_3}{89k} = 0 \quad (3)$$

Substitute $i_\Delta = \frac{V_1 - V_2}{4k}$ into eqns. (2) & (3),
then solve.




$$V_1 = 32.75V, V_2 = 30.58V, V_3 = V_{DC} = V_{th} = -19.8V$$

To find R_{th} , you can use the short circuit method and solve for I_{SC} using mesh analysis.

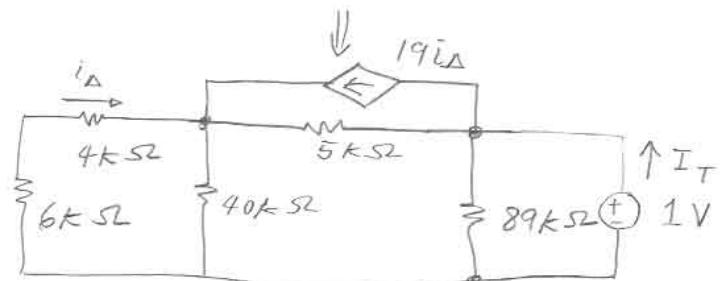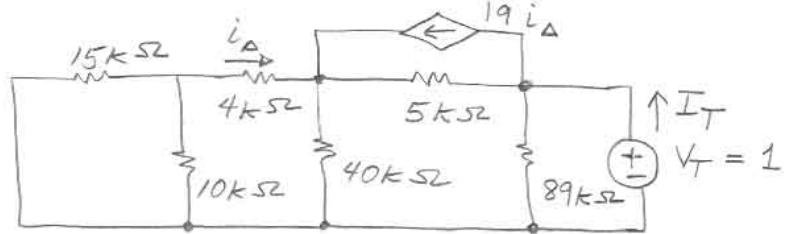Alternatively, you can set all independent sources to zero and use a test voltage source \Rightarrow



↓

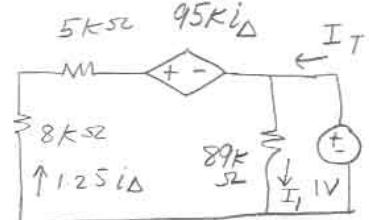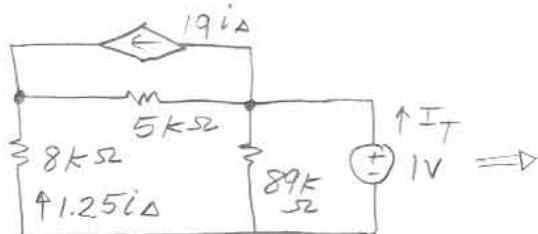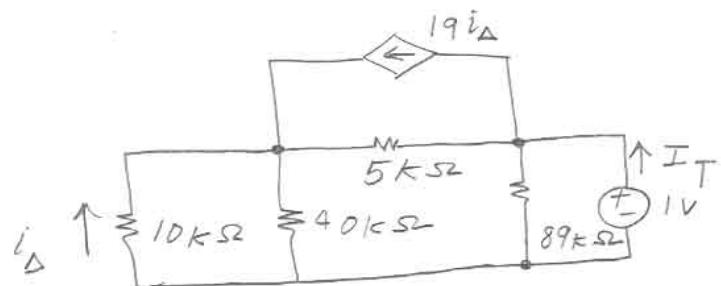

$$KVL \Rightarrow -1 - 95k i_{\Delta} - 13k(1.25i_{\Delta}) = 0$$

$$i_{\Delta} = -8.989 \mu A, \quad i_1 = \frac{1}{89k} = 11.24 \mu A$$

$$\therefore I_T = -1.25i_{\Delta} + I_1 = 22.476 \mu A, \quad R_{ex} = \frac{1}{22.476 \mu A} = 44.49 k\Omega$$