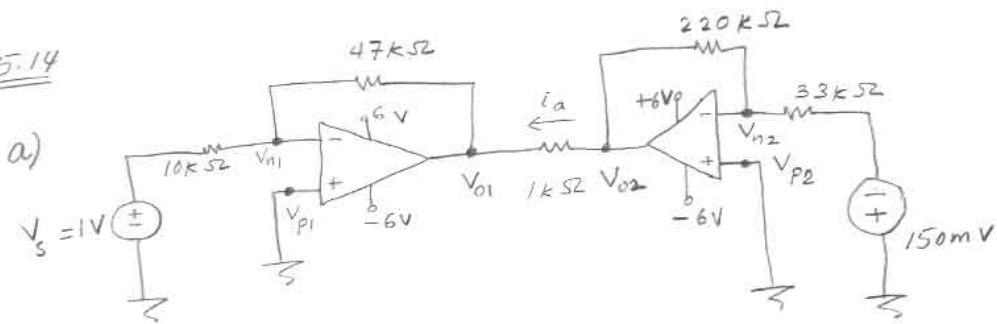


HW #8

①

5.14



a)

$$V_{p1} = 0 \Rightarrow V_{n1} = 0$$

$$\text{KCL at } V_{n1} \Rightarrow \frac{0 - 1}{10^4} + \frac{0 - V_{01}}{47 \times 10^3} = 0 \Rightarrow V_{01} = -4.7 \text{ V}$$

$$V_{p2} = 0 \Rightarrow V_{n2} = 0$$

$$\text{KCL at } V_{n2} \Rightarrow \frac{0 + 150 \times 10^{-3}}{33 \times 10^3} + \frac{0 - V_{02}}{220 \times 10^3} = 0 \Rightarrow V_{02} = 1 \text{ V}$$


$$i_a = \frac{V_{02} - V_{01}}{1\text{k}} = \frac{1 + 4.7}{1000} = 5.7 \text{ mA}$$

b) For  $i_a = 0 \Rightarrow V_{01} = V_{02} = 1$ , thus we need to adjust  $V_s$  until  $V_{01} = 1 \text{ V}$ .

$$\frac{0 - V_s}{10000} + \frac{0 - 1}{47000} = 0 \quad (\text{KCL at } V_{n1})$$

$$\Downarrow \\ V_s = -0.213 \text{ V}$$

(2)

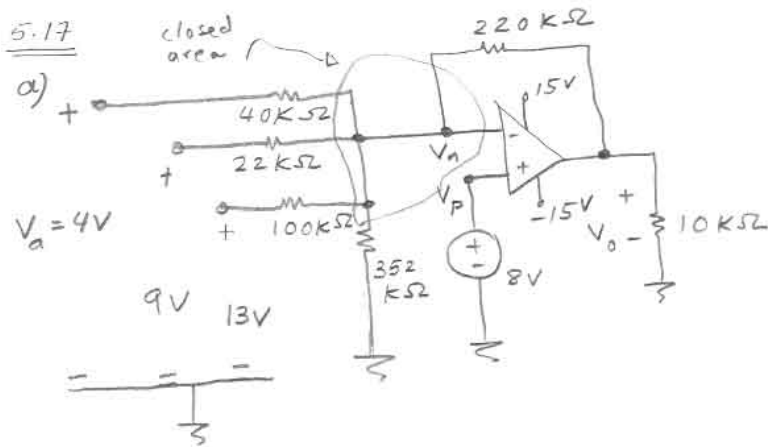

$$V_p = 8V \Rightarrow V_n = 8V$$

KCL around closed area  $\Rightarrow$

$$\frac{8 - V_o}{220K} + \frac{8 - 0}{352K} + \frac{8 - 13}{100K} + \frac{8 - 9}{22K} + \frac{8 - 4}{40K} = 0$$

$$\frac{8 - V_o}{220} + \frac{8}{352} - \frac{5}{100} - \frac{1}{22} + \frac{4}{40} = 0$$

$$\frac{V_o - 8}{220} = 2.7273 \times 10^{-2} \Rightarrow V_o = 14V$$

$$b) \frac{8 - V_o}{220K} + \frac{8 - 0}{352K} + \frac{8 - 13}{100K} + \frac{8 - 9}{22K} + \frac{8 - V_a}{40K} = 0$$

$$\frac{8 - V_o}{220} + \frac{8}{352} - \frac{5}{100} - \frac{1}{22} + \frac{8 - V_a}{40} = 0$$

$$\frac{8 - V_o}{220} - 7.2727 \times 10^{-2} + \frac{8 - V_a}{40} = 0$$

$$V_o = 220 \left( -7.2727 \times 10^{-2} + \frac{8 - V_a}{40} \right) + 8$$

$$V_o = -16 + 44 - 5.5V_a + 8 = 36 - 5.5V_a$$

$$-15 \leq V_o \leq 15 \quad \left( \begin{array}{l} \text{condition for the Op} \\ \text{Amp. to operate in} \\ \text{the linear region.} \end{array} \right)$$

$$\therefore -15 \leq 36 - 5.5V_a \leq 15$$

$$-51 \leq -5.5V_a \leq -21$$

$$\frac{-51}{-5.5} \geq V_a \geq \frac{-21}{-5.5}$$

$$\therefore 9.273 \geq V_a \geq 3.818$$

6.3

$$v_L(t) = \begin{cases} 3e^{-4t} \text{ mV}, & 0 \leq t \leq 2 \\ -3e^{-4(t-2)} \text{ mV}, & 2 < t < \infty \end{cases}$$

$$i_L(t) = \frac{1}{L} \int_{t_0}^t v_L(t) dt + i_L(t_0) \quad (1)$$

we know that  $i_L(0) = 0$  (given).

$$\therefore i_L(t) = \frac{1}{L} \int_0^t v_L(t) dt + i_L(0) = \frac{1}{L} \int_0^t v_L(t) dt \quad (2)$$

For  $0 \leq t \leq 2 \Rightarrow$

$$i_L(t) = \frac{1}{2.5 \times 10^{-3}} \int_0^t 3e^{-4t} \times 10^{-3} dt$$

$$= 400(3)(10^{-3}) \frac{e^{-4t}}{-4} \Big|_0^t = -0.3 e^{-4t} \Big|_0^t \quad (4)$$

$$= -0.3 [e^{-4t} - 1] = 0.3 - 0.3 e^{-4t} \text{ A} \quad (3)$$

From (3)  $\Rightarrow i_L(2) = 0.3 - 0.3 e^{-8} = 0.3 \text{ A}$

Using (1)  $\Rightarrow$

$$i_L(t) = \frac{1}{L} \int_2^t v_L(t) dt + i_L(2) \quad , \text{ for } t > 2$$

$$= \frac{1}{2.5 \times 10^{-3}} \int_2^t (-3 e^{-4(t-2)}) \times 10^{-3} dt + 0.3$$

$$= 400(-3 \times 10^{-3}) \int_2^t e^{-4(t-2)} dt + 0.3$$



$$= -1.2 \frac{e^{-4(t-2)}}{-4} \Big|_2^t + 0.3$$

$$= \frac{1.2}{4} [e^{-4(t-2)} - e^{-4(0)}] + 0.3$$

$$= 0.3 [e^{-4(t-2)} - 1] + 0.3 = 0.3 e^{-4(t-2)} \quad (\text{for } t > 2)$$


$$\therefore i_L(t) = \begin{cases} 0.3 - 0.3 e^{-4t} & , 0 \leq t \leq 2 \\ 0.3 e^{-4(t-2)} & , t > 2 \end{cases}$$

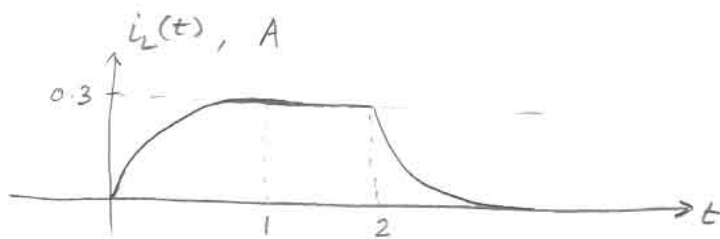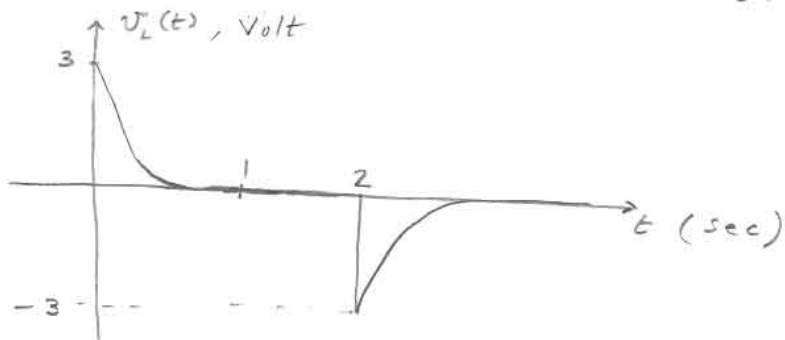The sketches of  $v_L(t)$  &  $i_L(t)$  are shown below:



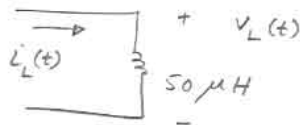6.4

$$i_L(t) = 18t e^{-10t}, \quad t \geq 0$$



$$\begin{aligned} \text{a) } v_L(t) &= L \frac{di_L(t)}{dt} = 50 \times 10^{-6} \frac{d}{dt} [18t e^{-10t}] \\ &= 50 \times 10^{-6} [18 e^{-10t} - 180t e^{-10t}] \\ &= 900 \times 10^{-6} e^{-10t} [1 - 10t], \quad t > 0 \end{aligned}$$

$$\text{b) } P_L = i_L v_L = (18t e^{-10t})(0.9 \times 10^{-3} e^{-10t})(1 - 10t)$$

$$\begin{aligned} P_L(200 \times 10^{-3}) &= 18(200 \times 10^{-3}) e^{-2} (0.9 \times 10^{-3})(e^{-2})(1 - 2) \\ &= -59.34 \mu\text{W} \end{aligned}$$

(6)

c) Actually delivering power at  $t = 200 \text{ ms}$ .

$$d) i_L(200 \text{ ms}) = 18(0.2) e^{-2} = 0.48721 \text{ A}$$

$$W(t) = \frac{1}{2} L i_L^2(t)$$

$$W(200 \text{ ms}) = \frac{1}{2} (50 \times 10^{-6}) (0.48721)^2 = 5.93 \mu\text{J}$$

$$e) W(t) = \frac{1}{2} L i_L^2(t)$$

$$= \frac{1}{2} (50 \times 10^{-6}) (18t e^{-10t})^2$$

$$= 25 \times 10^{-6} (18)^2 t^2 e^{-20t}$$

$$= 8.1 \times 10^{-3} t^2 e^{-20t} \quad (1)$$

Maximum energy occurs when  $W'(t) = 0$

$$\therefore \frac{dW}{dt} = 0 \Rightarrow 8.1 \times 10^{-3} 2t e^{-20t} + 8.1 \times 10^{-3} t^2 (-20) e^{-20t} = 0$$

$$\therefore 2t - 20t^2 = 0 \Rightarrow t = 0 \text{ or } t = \frac{1}{10}$$

$t = 0$  (rejected because the energy is minimum at  $t = 0$ ).

$\therefore t = \frac{1}{10} = 100 \text{ ms}$  is the time instant at which the energy stored in  $L$  is maximum.


$$\begin{aligned} \text{Substituting in (1)} \Rightarrow W(0.1) &= W_{\text{max}} \\ &= 8.1 \times 10^{-3} (0.1)^2 e^{-2} \\ &= 10.962 \mu\text{J} \end{aligned}$$

6.14

$$i_c(t) = c \frac{d v_c(t)}{dt} = 20 \times 10^{-6} \frac{d}{dt} \begin{cases} 30 t^2 \\ 30 (t-1)^2 \\ 0 \end{cases}$$

$$= 20 \times 10^{-6} \begin{cases} 60 t \\ 60 (t-1) \\ 0 \end{cases}$$
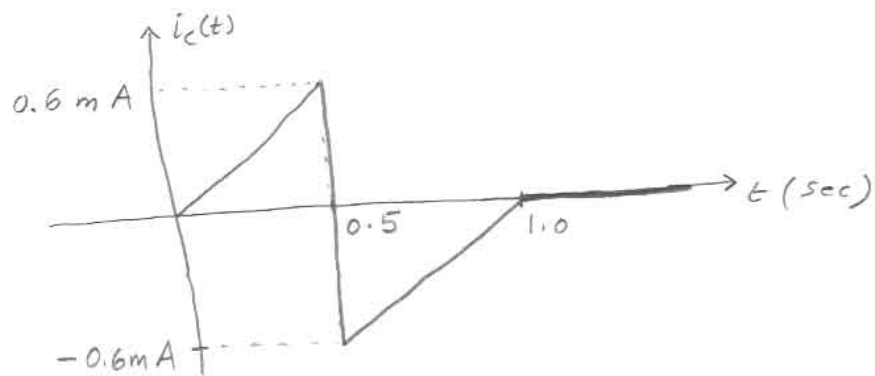
$$i_c(t) = \begin{cases} 1200 \times 10^{-6} t & , 0 \leq t \leq 0.5 \\ 1200 \times 10^{-6} (t-1) & , 0.5 \leq t \leq 1.0 \\ 0 & , \text{elsewhere} \end{cases}$$



6.18

$$a) v_c(t) = \frac{1}{C} \int_{t_0}^t i_c(t) dt + v_c(t_0), \text{ for } t \geq t_0$$

$$\text{since } v_c(0) = -20 \Rightarrow$$

$$v_c(t) = \frac{1}{C} \int_0^t i_c(t) dt + v_c(0) = \frac{1}{C} \int_0^t i_c(t) dt - 20$$

$$= \frac{1}{0.5 \times 10^{-6}} \int_0^t 50 e^{-2000t} \times 10^{-3} dt - 20, t \geq 0$$

$$= 2 \times 10^6 \times 10^{-3} \times 50 \frac{e^{-2000t}}{-2000} \Big|_0^t - 20$$

$$= -50(e^{-2000t} - 1) - 20 = -50e^{-2000t} + 30$$

$$\therefore v_c(t) = 30 - 50e^{-2000t}, t \geq 0.$$

$$v_c(500 \times 10^{-6}) = 30 - 50e^{-2000 \times 500 \times 10^{-6}} = 11.606 \text{ V}$$

$$w_c(t) = \frac{1}{2} C v_c^2(t) \Rightarrow$$

$$\therefore w_c(500 \times 10^{-6}) = \frac{1}{2} (0.5 \times 10^{-6}) (11.606)^2$$

$$= 33.68 \mu \text{ J}$$

$$b) v_c(\infty) = 30 - 50e^{-\infty} = 30 \text{ V}$$

$$w_c(\infty) = \frac{1}{2} C v_c^2(\infty) = \frac{1}{2} (0.5 \times 10^{-6}) (30)^2$$

$$= 225 \mu \text{ J}$$