
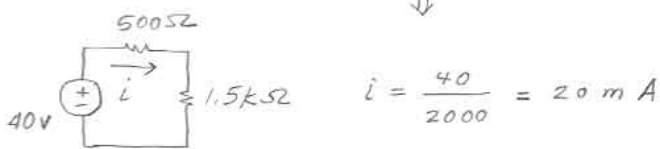


7.1

①

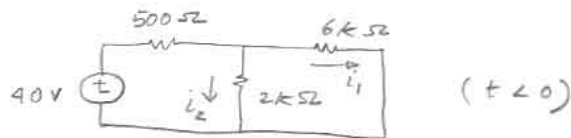a) The switch remains closed for a long time before it was opened at  $t=0$ . Therefore, the circuit is D.C. for  $t < 0$ .

∴ Inductor is replaced by a short circuit:




Using CDR in the 1st circuit:

$$i_1 = \frac{2}{8} \times i = \frac{1}{4} \times 20 \text{ mA} = 5 \text{ mA}, t < 0$$

$$i_2 = \frac{6}{8} \times i = \frac{3}{4} \times 20 \text{ mA} = 15 \text{ mA}, t < 0$$

$$\therefore i_1(0^-) = 5 \text{ mA} \neq i_2(0^-) = 15 \text{ mA}$$

b) For  $t > 0 \Rightarrow$

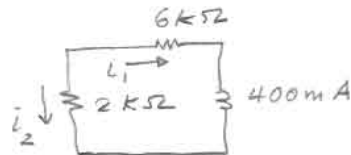

$$i_1(0^-) = i_1(0^+) = 5 \text{ mA} \quad (\text{because current through an inductor is continuous})$$

$$\therefore i_2(0^+) = -i_1(0^+) = -5 \text{ mA}$$

$$c) i_1(t) = i_1(0) e^{-t/\tau}, \quad t \geq 0 \quad (2)$$

$$i_1(0) = 5 \text{ mA}, \quad \tau = \frac{L}{R} = \frac{0.4}{8000} = 0.05 \times 10^{-3} \text{ s}$$

$$\therefore i_1(t) = 5 e^{-t/5 \times 10^{-5}} \text{ mA} = 5 e^{-20000t} \text{ mA}, \quad t \geq 0$$

$$d) i_2(t) = -i_1(t) = -5 e^{-20000t} \text{ mA}, \quad t > 0$$


e) The current through a resistor can be discontinuous (i.e. it can change instantaneously). But the current through the inductor cannot change instantaneously (i.e. it is always continuous).

The switching results in  $i_1(t^-) = i_1(t^+)$ ,  
and  $i_2(t^+) = -i_1(t^+) \Rightarrow i_2(t^+) = -i_1(t^-)$   
 $\neq i_2(t^-)$

73

(3)

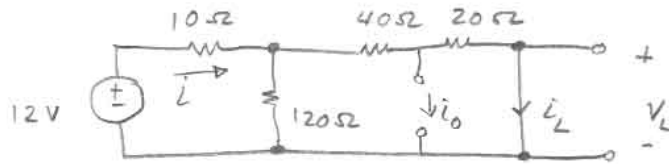
a) For  $t < 0$ , the circuit is D.C. because the switch remains open for a long time. Thus,



$$i_0(t) = 0 \text{ for } t < 0.$$

$$\therefore i_0(0^-) = 0$$

b)

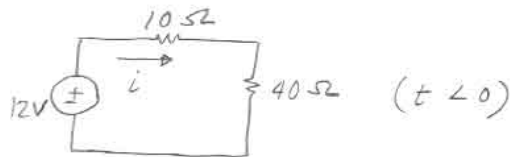


$$i(t) = \frac{12}{50} = 240 \text{ mA}, t < 0$$

$$\therefore i_L(t) = \frac{120}{180} \times 240 \text{ mA (CDR is used)}$$

$$= 160 \text{ mA}, t < 0$$

$$\therefore i_L(0^-) = 160 \text{ mA}$$

c) For  $t > 0$

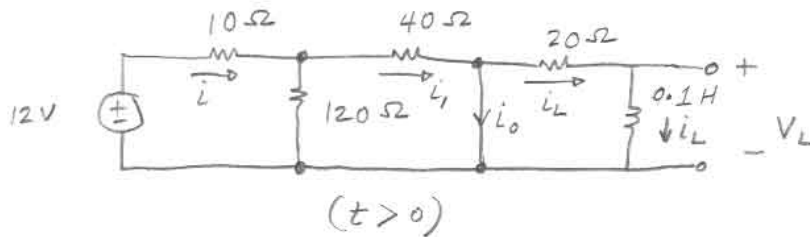

$$40 // 120 \Omega \Rightarrow 30 \Omega$$

(4)

$$\therefore i(t) = \frac{12}{10+30} = \frac{12}{40} = 0.3 \text{ A}, t > 0$$

$$\text{CDR} \Rightarrow i_1(t) = \frac{120}{160} \times 0.3 = \frac{3}{4} \times 0.3 = 0.225 \text{ A}, t > 0.$$

$$\therefore i_1(0^+) = 0.225 \text{ A}$$

$$i_0(0^+) = i_1(0^+) - i_L(0^+)$$

$$= i_1(0^+) - i_L(0^-)$$

$$= 225 \text{ mA} - 160 \text{ mA} = 65 \text{ mA}$$

$$d) i_L(0^+) = i_L(0^-) = 160 \text{ mA}$$

$$e) i_L(t) = i_L(0) e^{-t/\tau}, \quad \tau = \frac{L}{R} = \frac{0.1}{20} = 5 \text{ ms}$$

$$i_L(0) = 160 \text{ mA}$$

$$\therefore i_L(t) = 160 e^{-t/5 \times 10^{-3}} \text{ mA} = 160 e^{-200t} \text{ mA}, t \geq 0$$

$$i_0(t) = i_1(t) - i_L(t) = (225 - 160 e^{-200t}) \text{ mA}, t > 0.$$

$$\therefore i_0(\infty) = 225 \text{ mA}$$

$$\left[ \text{or since } i_L(\infty) = 0 \right.$$

$$\left. \therefore i_0(\infty) = i_1(\infty) - i_L(\infty) = 225 \text{ mA} - 0 = 225 \text{ mA} \right]$$

(5)

$$f) i_L(\infty) = 0$$

$$g) i_L(t) = 160 e^{-200t} \text{ mA}, t \geq 0$$

$$h) v_L(0^-) = 0.$$

$$\begin{aligned} i) v_L(t) &= L \frac{di_L}{dt} = 0.1 \frac{d}{dt} [160 e^{-200t} \text{ mA}], t > 0 \\ &= 0.1(-200)(160) e^{-200t} \text{ mV} \\ &= -3200 e^{-200t} \text{ mV} \\ &= -3.2 e^{-200t} \text{ V}, t > 0 \end{aligned}$$

$$\therefore v_L(0^+) = -3.2 \text{ V}$$

$$\left[ \begin{aligned} \text{or: } v_L(0^+) &= -20 i_L(0^+) \\ &= -20(160 \text{ mA}) = -3.2 \text{ V} \end{aligned} \right]$$

j)  $v_L(\infty) = 0$ , because  $i_L(t)$  becomes zero (i.e. constant current) as  $t \rightarrow \infty$ .

You can also make the same conclusion from the voltage expression in part i).

$$k) v_L(t) = -3.2 e^{-200t} \text{ V}, t > 0. \text{ (see part i).}$$


$$l) i_0(t) = (225 - 160 e^{-200t}) \text{ mA}, t \geq 0 \text{ (see part e).}$$

7.18

(6)

a) The two switches remain closed for a long time before they are opened at  $t=0$ .


∴ The circuit is D.C. for  $t < 0$

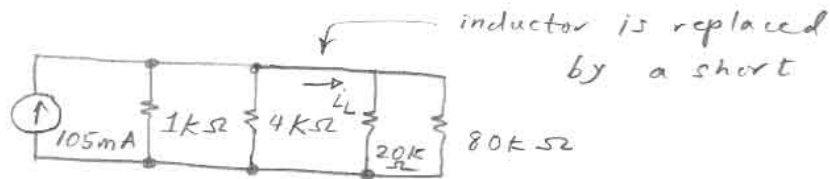

$t < 0$

$$1 \text{ k}\Omega // 4 \text{ k}\Omega \Rightarrow 0.8 \text{ k}\Omega$$

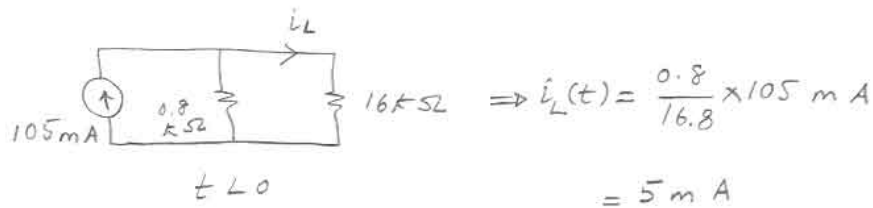
$$20 \text{ k}\Omega // 80 \text{ k}\Omega \Rightarrow 16 \text{ k}\Omega$$




$$\therefore i_L(0^-) = 5 \text{ mA}$$

The initial energy stored in the 6 H inductor
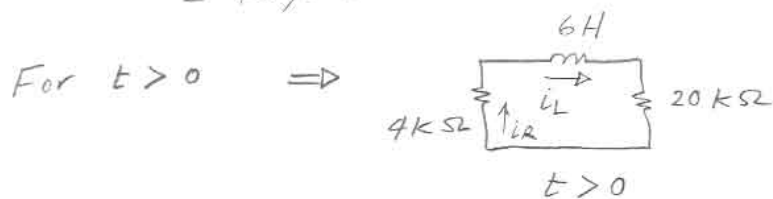
$$\text{is } W_L(0^-) = \frac{1}{2} L i_L^2(0^-) = \frac{1}{2} \times 6 \times (5 \times 10^{-3})^2$$
$$= 75 \mu\text{J}$$



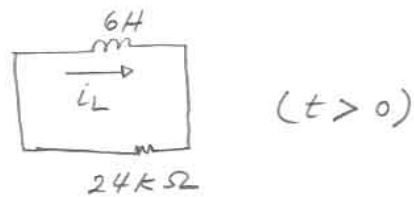

$$i_L(t) = i_L(0) e^{-t/\tau}, \quad \tau = \frac{L}{R} = \frac{6}{24000} = 0.25 \text{ ms}$$

$$\therefore \frac{1}{\tau} = 4000 \text{ s}^{-1}$$

$$i_L(0) = 5 \text{ mA}$$

$$\therefore i_L(t) = 5 e^{-4000t} \text{ mA}, \quad t \geq 0$$

The current through the  $4 \text{ k}\Omega$  resistor is

$$i_R(t) = i_L(t) = 5 e^{-4000t} \text{ mA}, \quad t \geq 0.$$

$$P_{4\text{k}\Omega}(t) = i_R^2(t) R = (5 \times 10^{-3} e^{-4000t})^2 \times 4000$$

$$= 25 \times 10^{-6} \times 4000 e^{-8000t}$$

$$= 100 e^{-8000t} \text{ mW}, \quad t \geq 0$$

$\therefore$  Energy dissipated in the  $4 \text{ k}\Omega$  resistor after  $t = 0$  is:

$$\begin{aligned} W_{4\text{k}\Omega}(t) &= \int_0^t P_{4\text{k}\Omega}(t) dt = \int_0^t 0.1 e^{-8000t} dt \\ &= \frac{0.1 e^{-8000t}}{-8000} \Big|_0^t = \frac{0.1}{8000} (1 - e^{-8000t}) \end{aligned}$$

$$= 12.5(1 - e^{-8000t}) \mu\text{J}$$

②

To find the instant of time  $t$  at which

$$W_{4\text{k}\Omega} = 0.1 \times W_{20\text{k}\Omega} \Rightarrow$$

$$12.5(1 - e^{-8000t}) = 0.1 \times 75$$

$$1 - e^{-8000t} = 0.6 \Rightarrow e^{-8000t} = 0.4$$

$$-8000t = \ln 0.4 \Rightarrow t = \frac{\ln 0.4}{-8000} = 114.54 \mu\text{s}$$

- b) At  $t = 114.54 \mu\text{s}$ , the energy dissipated by the  $4\text{k}\Omega$  &  $20\text{k}\Omega$  resistors is 6 times larger than the energy dissipated by the  $4\text{k}\Omega$  resistor.  
 $\therefore$  % of energy is 60%.


This conclusion is valid because the same current passes through the  $4\text{k}\Omega$  &  $20\text{k}\Omega$  resistors.



7.22

9



a)

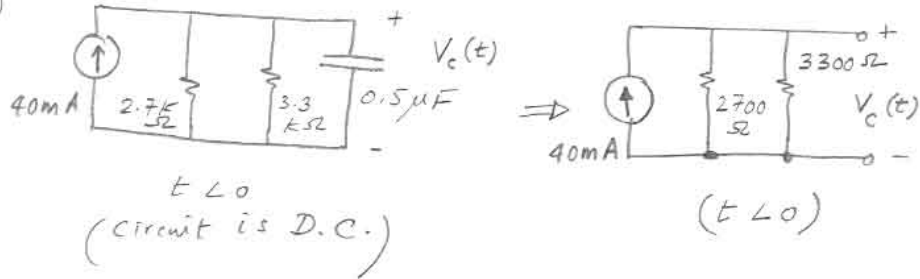

$$V_c(t) = (40 \text{ m}) \times (2700 // 3300)$$

$$= 40 \text{ m} \times 1485 = 59.4 \text{ V}, \quad t < 0$$

For  $t > 0$

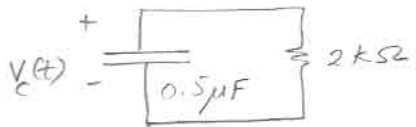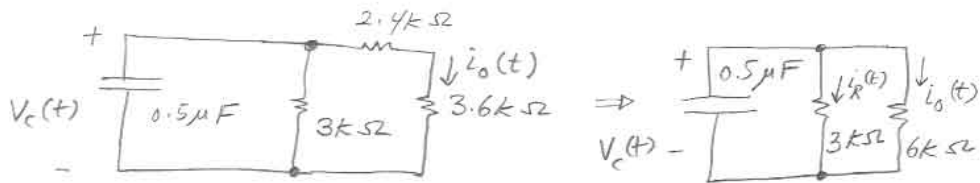

$$\therefore V_c(t) = V_c(0) e^{-t/\tau}$$

$$\tau = RC = 0.5 \times 10^{-6} (2000)$$

$$= 10^{-3} \text{ s}$$

$$V_c(0) = 59.4 = V_c(0)$$

$$\therefore V_c(t) = 59.4 e^{-1000t}, \quad t \geq 0$$

$$\therefore i_o(t) = \frac{V_c(t)}{6000} = \frac{59.4 e^{-1000t}}{6000} = 9.9 e^{-1000t} \text{ mA}, \quad t \geq 0$$

$$b) i_R(t) = \frac{v_c(t)}{3000} = \frac{59.4 e^{-1000t}}{3000}$$

(10)

$$= 19.8 e^{-1000t} \text{ mA}, t \geq 0.$$

$$\therefore P_{3k}(t) = i_R^2(t) R = (19.8 \times 10^{-3} e^{-1000t})^2 \times 3000$$

$$= 1.176 e^{-2000t} \text{ W}$$

$$w_{3k\Omega}(t) = \int_0^t p_{3k\Omega}(t) dt = \int_0^t 1.176 e^{-2000t} dt$$

$$= \frac{1.176 e^{-2000t}}{-2000} \Big|_0^t = \frac{1.176}{2000} (1 - e^{-2000t})$$

$$\therefore w_{3k\Omega}(500\mu s) = \frac{1.176}{2000} (1 - e^{-2000 \times 500 \times 10^{-6}})$$

$$= 371.7 \mu\text{J}$$

Initial energy stored in the capacitor:

$$w_c(0) = \frac{1}{2} C v_c^2(0) = \frac{1}{2} (500 \times 10^{-6}) (59.4)^2$$

$$= 882.1 \mu\text{J}$$

% of energy dissipated after  $500\mu s =$




$$\frac{371.7 \mu\text{J}}{882.1 \mu\text{J}} \times 100\% = 42.1\%$$

7.53

(11)

For  $t < 0$ , the voltage across  $C$  is zero (why?).

For  $t > 0$

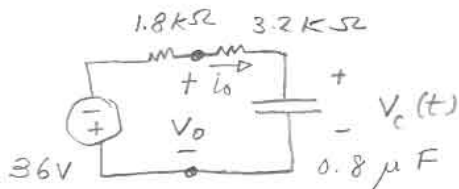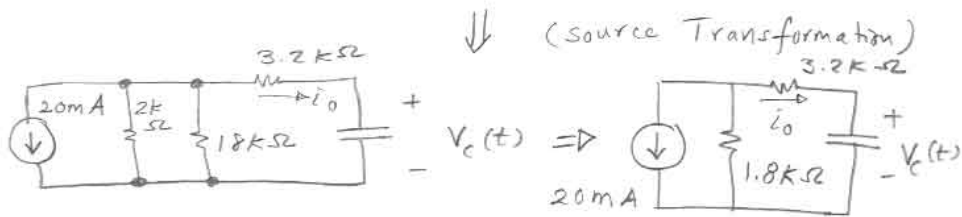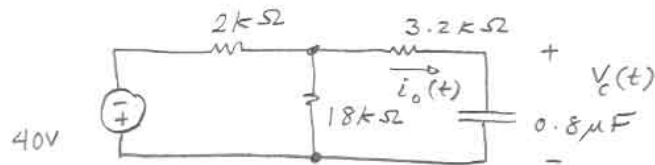

$$\therefore i_o(0^+) = \frac{-36 - V_c(0^+)}{5K} = \frac{-36 - 0}{5000} = -7.2 \text{ mA}$$

b)  $i_o(\infty) = 0$ . (Capacitor behaves as an open circuit as  $t \rightarrow \infty$ ).

$$c) \tau = RC = 5000 \times 0.8 \times 10^{-6} = 4 \text{ ms}$$

$$d) V_c(t) = (-36)(1 - e^{-t/\tau}) = -36(1 - e^{-250t}), t \geq 0$$

$$\therefore i_o(t) = \frac{-36 - V_c(t)}{5000} = \frac{-36 e^{-250t}}{5000}$$

$$= -7.2 e^{-250t} \text{ mA}, t \geq 0$$

$$e) 36 + 1800 i_o + V_o = 0 \Rightarrow V_o(t) = -36 + 12.96 e^{-250t}, t \geq 0$$