

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

SECOND SEMESTER 2007/2008

EE 201 MAJOR EXAM I

DATE: WEDNESDAY 19-3-2008

TIME: 10:00-10:55 AM

LOCATION: IN CLASS

Student's Name:..... **KEY** .....


Student's I.D. Number:.....

	Maximum Score	Score
<b>Problem 1</b>	<b>40</b>	
<b>Problem 2</b>	<b>20</b>	
<b>Problem 3</b>	<b>40</b>	
<b>Total</b>	<b>100</b>	

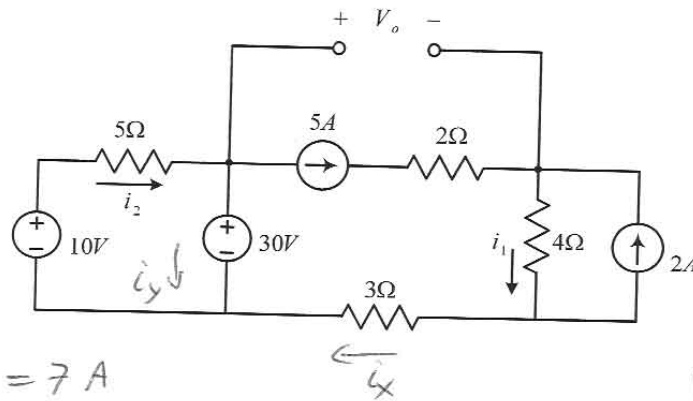Problem 1 [40 pts]

In the circuit shown below, find:

- $i_1$
- $i_2$
- $V_o$
- Power absorbed by the  $30V$  source.



$$a) i_1 = 5 + 2 = 7 A$$

$$b) i_2 = \frac{10 - 30}{5} = -4 A$$

$$c) i_x = i_1 - 2 = 7 - 2 = 5 A$$

$$V_o = 30 - 5 \times 3 - 4 \times 7 = -13 V$$

$$d) i_y = i_2 - 5 = -4 - 5 = -9 A$$

$$P_{30V} = 30 i_y = -270 W$$

Answers:

$$i_1 = 7 A$$



$$i_2 = -4 A$$

$$V_o = -13 A$$






$$P_{30V} = -270 W$$

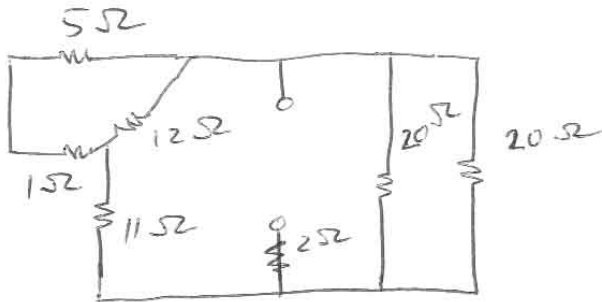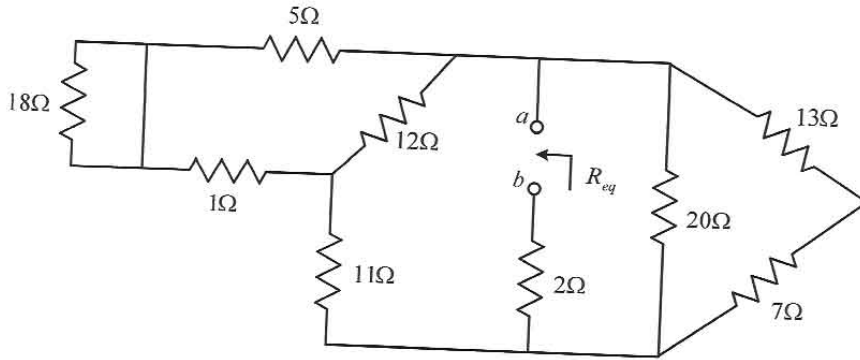Problem 2 [20 pts]

In the given circuit, calculate the equivalent resistance seen between the terminals  $a$  &  $b$ .




**Answer:**  
 $R_{eq} =$

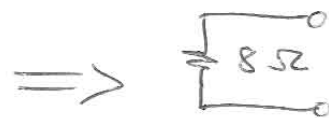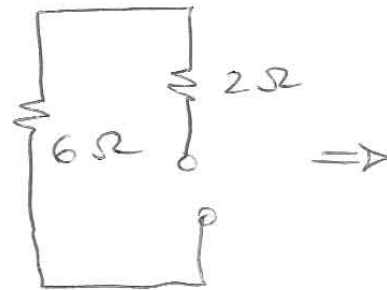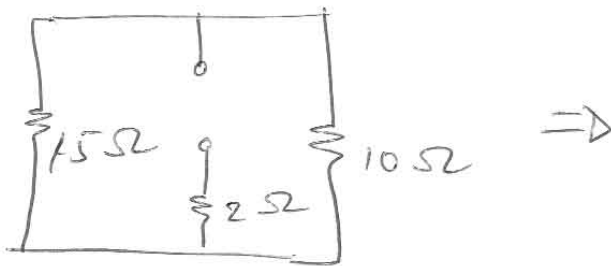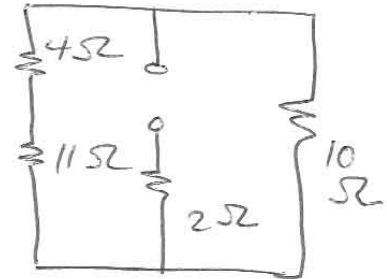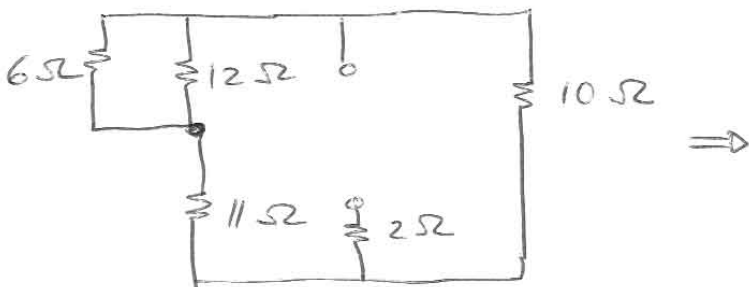

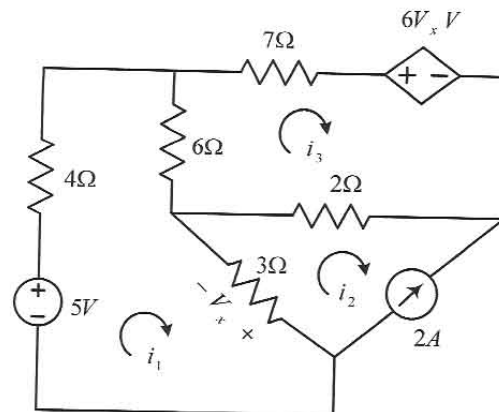Problem 3 [40 pts]

Calculate the mesh currents  $i_1, i_2, i_3$  in the given circuit.



$$i_2 = -2 \text{ A}$$

$$-5 + 4i_1 + 6(i_1 - i_3) + 3(i_1 - i_2) = 0$$

$$\therefore 13i_1 - 6i_3 = -1 \quad (1)$$

$$7i_3 + 6V_x + 2(i_3 - i_2) + 6(i_3 - i_1) = 0$$

$$V_x = 3(i_2 - i_1)$$

$$\therefore -24i_1 + 15i_3 = 32 \quad (2)$$

solving

$$i_1 = 3.47 \text{ A}, \quad i_3 = 7.69 \text{ A}$$

Answers:

$$i_1 = 3.47 \text{ A}$$

$$i_2 = -2 \text{ A}$$

$$i_3 = 7.69 \text{ A}$$