

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
SECOND SEMESTER 2007/2008

EE 201 MAJOR EXAM II
DATE: SATURDAY 3-5-2008
TIME: 10:00-10:55 AM
LOCATION: IN CLASS

Student's Name:.....
Student's I.D. Number:.....


KEY

	Maximum Score	Score
Problem 1	40	
Problem 2	20	
Problem 3	40	
Total	100	

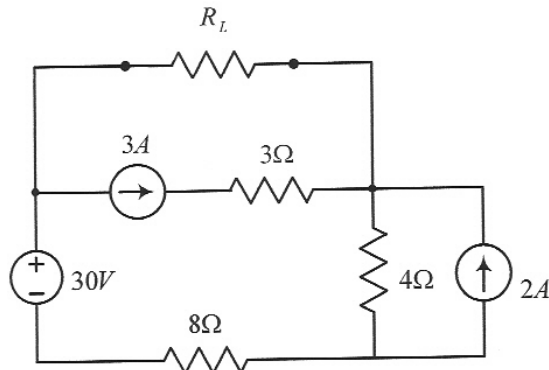
Problem 1 [40 pts]

In the circuit shown below, find:

- R_L for maximum power transfer.
- The maximum power transferred to R_L .



a)

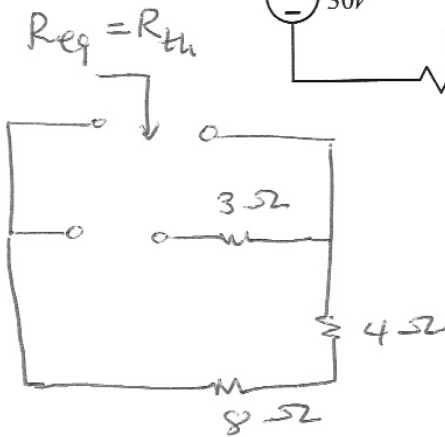


$$\Rightarrow R_{eq} = 4 + 8 = 12 \Omega$$

Answers:

a) $R_L = 12 \Omega$

b) $P_{max} = 4.08 \text{ W}$

b)

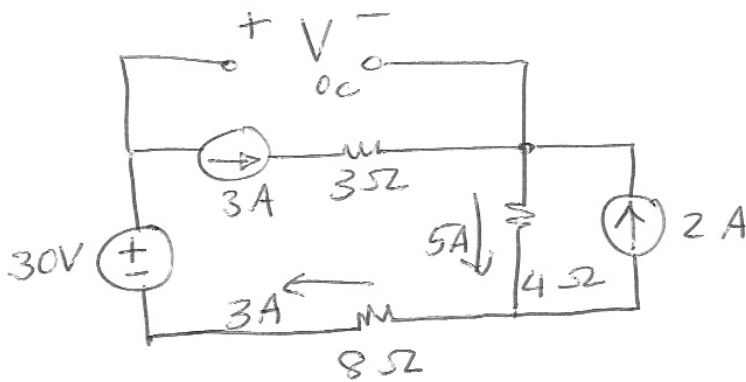


$$V_{OC} = V_{th} = 30 - 3 \times 8 - 5 \times 4 = -14 \text{ V}$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(14)^2}{4 \times 12} = 4.08 \text{ W}$$

Problem 2 [20 pts]

In the ideal Op Amp circuit shown below, calculate the current i_L through the $1k\ \Omega$ load resistor.

[Show your work clearly]

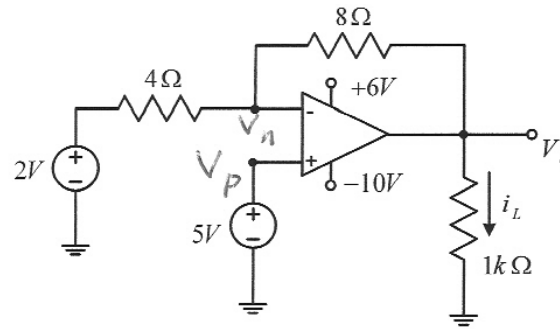

$$V_p = V_n = 5V$$

KCL at node n \Rightarrow

$$\frac{5-2}{4} + \frac{5-V_o}{8} = 0$$

$$\therefore V_o = 11V > 6V = V_{cc}^+ \Rightarrow$$

$$V_o = 6V$$

$$\therefore i_L = \frac{V_o}{1k} = \frac{6}{1000} = 6mA$$





Answer:

$$i_L = 6mA$$

Problem 3 [40 pts]

In the circuit shown below, switch S_1 has been closed and switch S_2 has been open for a long time. At $t = 0$, switch S_1 is opened and switch S_2 is closed suddenly. Find:

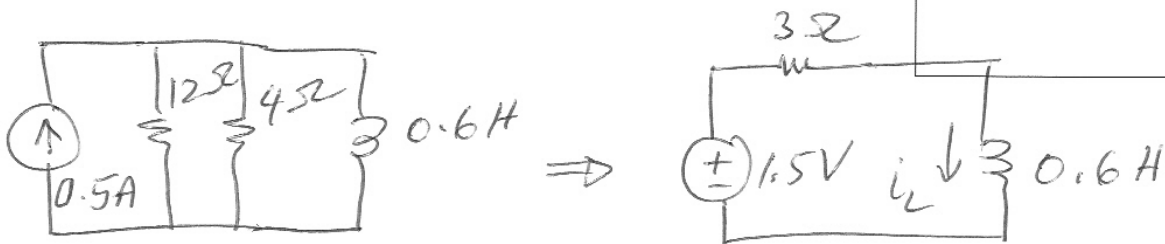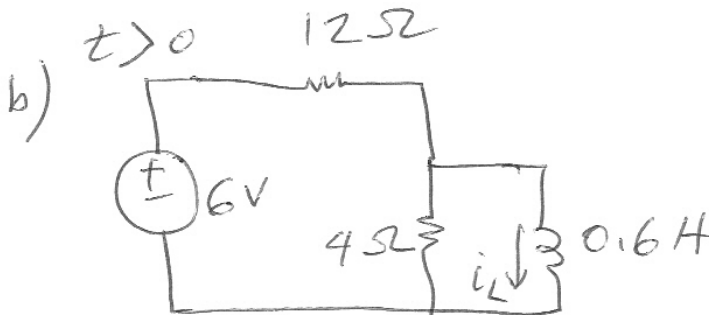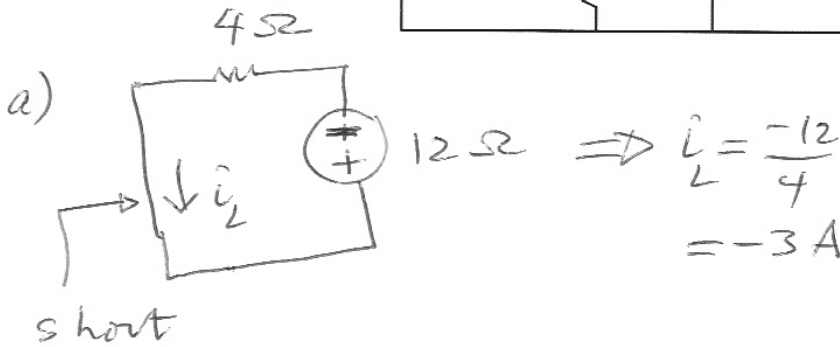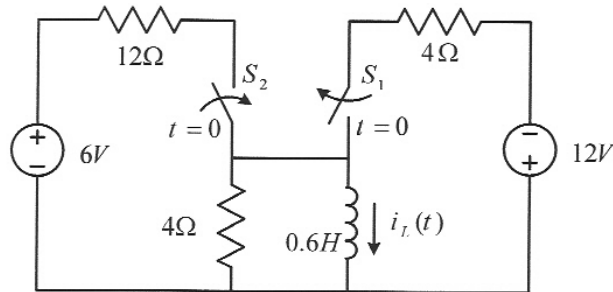- a) $i_L(t)$ for $t < 0$.
 b) $i_L(t)$ for $t \geq 0$.



$$-1.5 + 3i_L + 0.6 \frac{di_L}{dt} = 0 \Rightarrow \frac{di_L}{dt} + 5i_L = 2.5$$

$$\therefore i_L(t) = \frac{b}{a} + A e^{-at} = 0.5 + A e^{-5t}$$

$$i_L(0) = -3 = 0.5 + A \Rightarrow A = -3.5$$

$$\therefore i_L(t) = 0.5 - 3.5 e^{-5t}$$

Answers:

a) For $t < 0$,

$$i_L(t) = -3A$$

b) For $t \geq 0$,

$$i_L(t) = 0.5 - 3.5 e^{-5t}$$