

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

SECOND SEMESTER 2005/2006

EE 201 MAJOR EXAM I

LOCATION: IN CLASS

DATE: MONDAY 20-3-2006

DURATION: 50 MINUTES

Student's Name:.....

Student's I.D. Number:.....


<b>Problem 1</b>	
<b>Problem 2</b>	
<b>Problem 3</b>	
<b>Total</b>	

Problem 1 [33 points]

In the circuit shown, the current through the  $4\Omega$  resistor is  $4\text{A}$ .  
Use KVL, KCL and Ohm's law **only** to calculate:

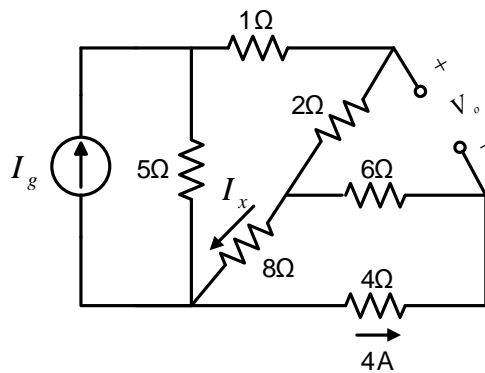- a)  $V_o$
- b)  $I_x$
- c)  $I_g$


[Do not use Node Analysis, Mesh Analysis or Source Transformation]



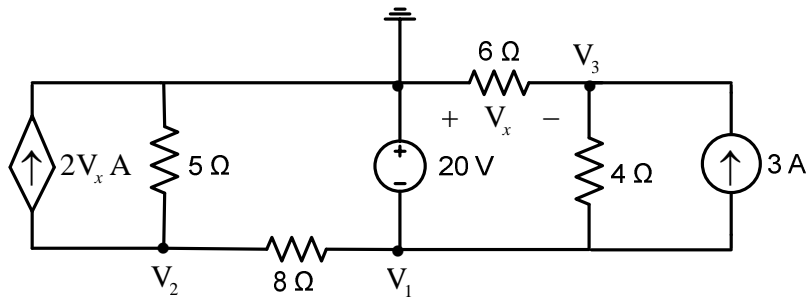Problem 2 [34 points]

In the given circuit:

- Calculate the node voltages  $V_1$ ,  $V_2$ , and  $V_3$ .
- The power absorbed by the independent current source.



Problem 3 [33 points]

In the given circuit, use source transformation to calculate the currents:

a)  $I_1$ .

b)  $I_2$ .

