

EE 201 Assignment - 2

Dr. H. M. Masoudi

Use Multisim Software to calculate the current i in the circuit shown below. Use the assignment guidelines to submit your answer electronically using WebCT.

