

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-360


Key Solution

Quiz # 8 Serial #

Name:

I.D.#

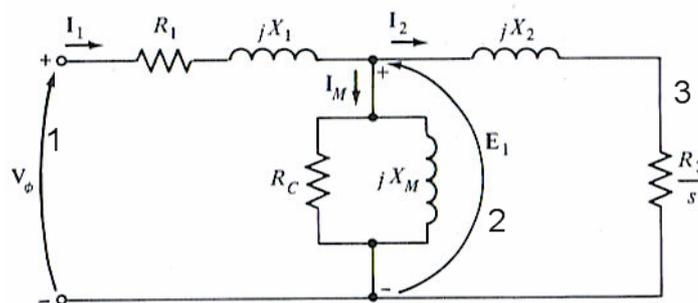1) In the per-phase equivalent circuit of a polyphase induction motor shown below, number "1" is the (...) power, number "2" is the (...), and number "3" is the (...) power.



- a) electrical input ; converted ; mechanical output
- b) electrical input; air-gap; mechanical output
- c) **electrical input; air-gap; converted**
- d) mechanical input; converted; electrical output

2) A three-phase, 60-Hz, induction motor has a full-load speed of 1100 rpm. The number of poles and the slip of the motor are:

- a) 4-pole; 0.39
- b) 4-pole; 0.64
- c) **6-pole; 0.083**
- d) 6-pole; 0.091