

**KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS**  
**ELECTRICAL ENGINEERING DEPARTMENT**

**EE 201 Major Exam II**

**TIME: 06:30P.M. – 08:00 P.M.**

**DATE: Monday December 18, 2006**

**Key Solution**

**Student's Name:** \_\_\_\_\_

**Student's I.D. Number:** \_\_\_\_\_

**Section Number:** \_\_\_\_\_

**Serial Number:** \_\_\_\_\_

	Grade	Max. Grade
Problem 1		5
Problem 2		5
Problem 3		5
Total		15


**Problem 1 (5 Points)**


In the circuit shown, Find:

- a) The value of the load resistor  $R_L$  that results in maximum power transfer.
- b) The maximum power absorbed by  $R_L$ .


**Answer:**

(a) $R_L =$	
(b) $P_{\max} =$	

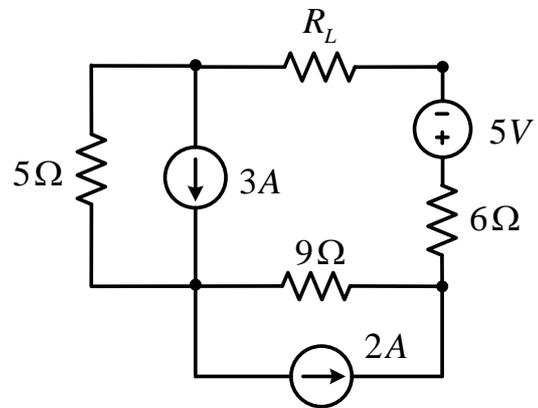

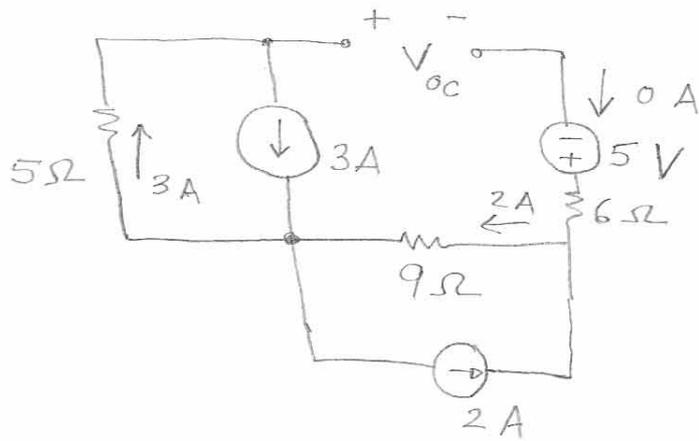

$$V_{oc} = -3(5) - 2(9) + 5 = -28V$$

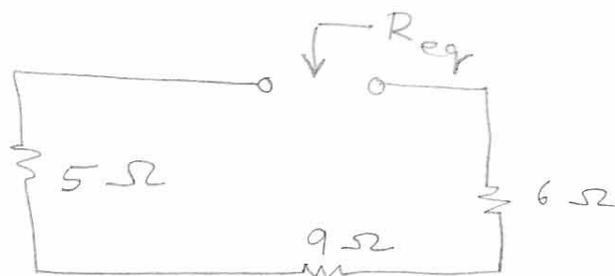


$$R_{eq} = 5 + 9 + 6 = 20 \Omega = R_{th}$$

$$a) R_{th} = R_L = 20 \Omega$$

$$b) P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(28)^2}{4 \times 20} = 9.8 W$$



**Problem 2 (5 Points)**

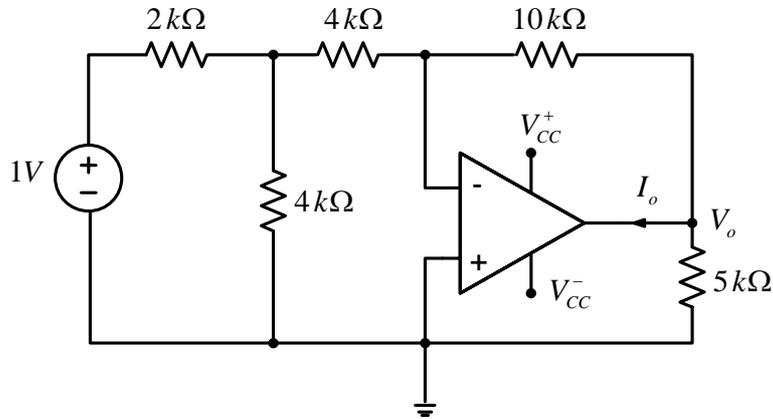a) Determine  $I_o$  and  $V_o$  for the circuit shown below (Assume the Op Amp does not saturate):



$I_o =$	$\frac{3}{8} \text{ mA}$
$V_o =$	$-\frac{5}{4} \text{ V}$

b)

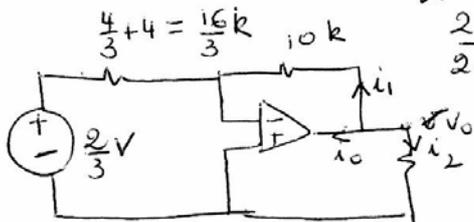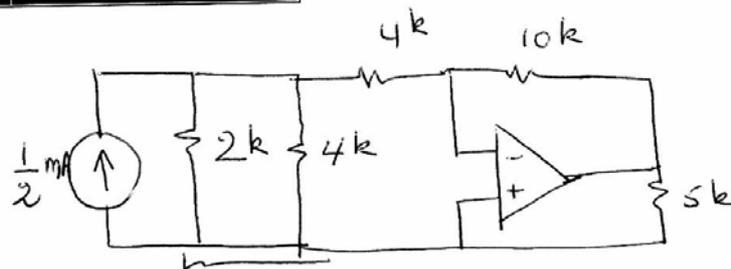

$$V_o = -\frac{10}{16/3} \cdot \frac{2}{3} = -\frac{10}{8} = \boxed{-\frac{5}{4} \text{ V}}$$

$$i_1 = -\frac{5}{40} \text{ mA} \quad i_2 = -\frac{5}{20} \text{ mA}$$


$$i_o = -i_1 - i_2 = \frac{5}{40} + \frac{10}{40} = \frac{15}{40} = \boxed{\frac{3}{8} \text{ mA}}$$

**Problem 3 (5 Points)**

Problem 3


In the circuit shown, the switch remains open for a long time. It is suddenly closed at  $t = 0$ . Find:

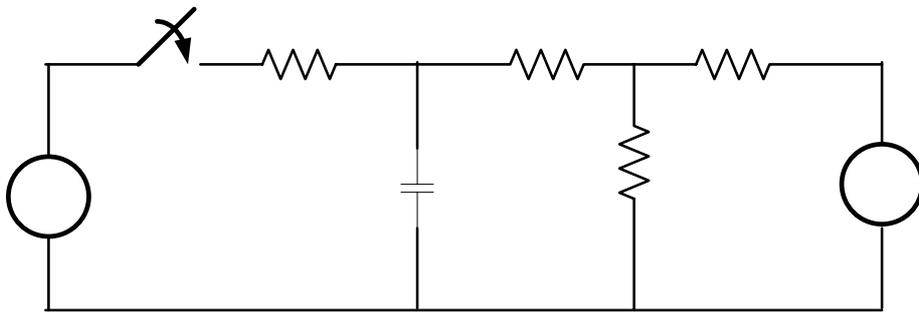- a)  $V_c(t)$  for  $t < 0$ .
- b)  $V_c(t)$  for  $t \geq 0$ .
- c) Calculate the power absorbed by the capacitor at  $t = 20 \text{ ms}$ .





$t = 0$

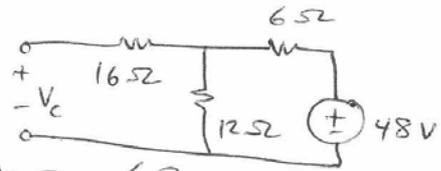a)  $t < 0 \Rightarrow V_c = \frac{12}{18} \times 48 = 32 \text{ V}$




b)  $t > 0$

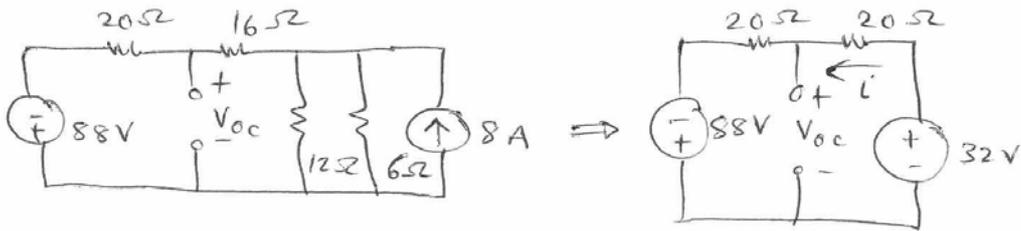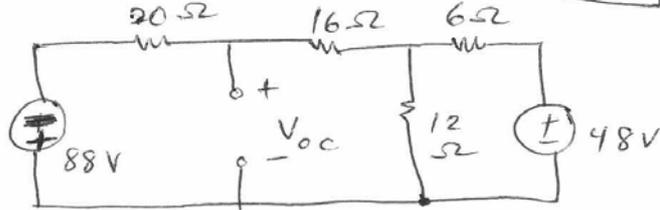

$$i = \frac{32 + 88}{40} = \frac{120}{40} = 3 \text{ A}$$

$$\therefore V_{oc} = -20i + 32 = -60 + 32 = -28 \text{ V}$$

$$R_{eq} = 20 \parallel 20 = 10 \Omega$$

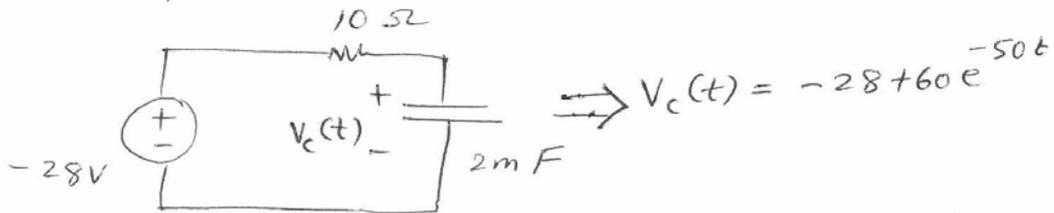

$$c) i_c(t) = 2 \times 10^{-3} (-3000 e^{-50t}) = -6 e^{-50t}$$

$$\therefore P_c(t) = i_c(t) v_c(t) = -6(-28 + 60 e^{-50t}) e^{-50t}$$

$$P_c(0.02) = -6(-28 + 60 e^{-1}) e^{-1}$$

$$= 13.08 \text{ W}$$