

$$\begin{aligned}
 \text{P 9.17 [a]} \quad Y &= \frac{1}{3 + j4} + \frac{1}{16 - j12} + \frac{1}{-j4} \\
 &= 0.12 - j0.16 + 0.04 + j0.03 + j0.25 \\
 &= 0.16 + j0.12 = 200/\underline{36.87^\circ} \text{ mS}
 \end{aligned}$$

$$\text{[b]} \quad G = 160 \text{ mS}$$

$$\text{[c]} \quad B = 120 \text{ mS}$$

$$\text{[d]} \quad \mathbf{I} = 8/\underline{0^\circ} \text{ A}, \quad \mathbf{V} = \frac{\mathbf{I}}{Y} = \frac{8}{0.2/\underline{36.87^\circ}} = 40/\underline{-36.87^\circ} \text{ V}$$

$$\mathbf{I}_C = \frac{\mathbf{V}}{Z_C} = \frac{40/\underline{-36.87^\circ}}{4/\underline{-90^\circ}} = 10/\underline{53.13^\circ} \text{ A}$$

$$i_C = 10 \cos(\omega t + 53.13^\circ) \text{ A}, \quad I_m = 10 \text{ A}$$

P 9.19 [a] $\mathbf{V}_g = 300\angle 78^\circ$; $\mathbf{I}_g = 6\angle 33^\circ$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = \frac{300\angle 78^\circ}{6\angle 33^\circ} = 50\angle 45^\circ \Omega$$


[b] i_g lags v_g by 45° :

$$2\pi f = 5000\pi; \quad f = 2500 \text{ Hz}; \quad T = 1/f = 400 \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{45^\circ}{360^\circ}(400 \mu\text{s}) = 50 \mu\text{s}$$

P 9.29 $j\omega L = j100 \times 10^3(0.6 \times 10^{-3}) = j60 \Omega$
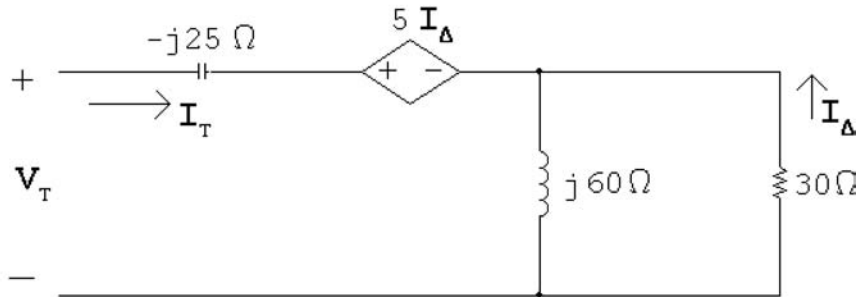
$$\frac{1}{j\omega C} = \frac{-j}{(100 \times 10^3)(0.4 \times 10^{-6})} = -j25 \Omega$$



$$\mathbf{V}_T = -j25\mathbf{I}_T + 5\mathbf{I}_\Delta - 30\mathbf{I}_\Delta$$

$$\mathbf{I}_\Delta = \frac{-j60}{30 + j60}\mathbf{I}_T$$


$$\mathbf{V}_T = -j25\mathbf{I}_T + 25\frac{j60}{30 + j60}\mathbf{I}_T$$

$$\frac{\mathbf{V}_T}{\mathbf{I}_T} = Z_{ab} = 20 - j15 = 25\angle -36.87^\circ \Omega$$

$$\text{P 9.36} \quad \mathbf{V}_o = \mathbf{V}_g \frac{Z_o}{Z_T} = \frac{500 - j1000}{300 + j1600 + 500 - j1000} (100 \angle 0^\circ) = 111.8 \angle -100.3^\circ \text{ V}$$

$$v_o = 111.8 \cos(8000t - 100.3^\circ) \text{ V}$$

P 9.43 Open circuit voltage:

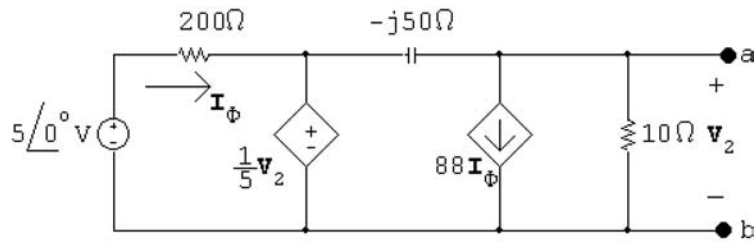


$$\frac{V_2}{10} + 88I_\phi + \frac{V_2 - \frac{1}{5}V_2}{-j50} = 0$$

$$I_\phi = \frac{5 - (V_2/5)}{200}$$

Solving,

$$V_2 = -66 + j88 = 110/126.87^\circ \text{ V} = V_{Th}$$

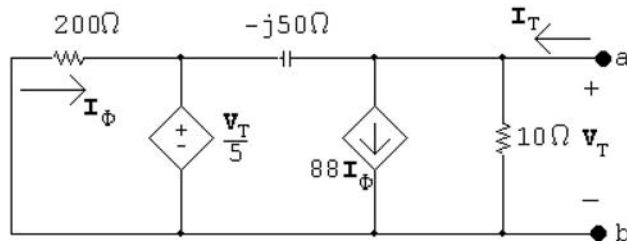Find the Thévenin equivalent impedance using a test source:



$$\mathbf{I}_T = \frac{\mathbf{V}_T}{10} + 88\mathbf{I}_\phi + \frac{0.8\mathbf{V}_t}{-j50}$$

$$\mathbf{I}_\phi = \frac{-\mathbf{V}_T/5}{200}$$

$$\mathbf{I}_T = \mathbf{V}_T \left(\frac{1}{10} - 88\frac{1/5}{200} + \frac{0.8}{-j50} \right)$$

$$\therefore \frac{\mathbf{V}_T}{\mathbf{I}_T} = 30 - j40 = Z_{Th}$$

$$\mathbf{I}_N = \frac{\mathbf{V}_{Th}}{Z_{Th}} = \frac{-66 + j88}{30 - j40} = -2.2 + j0 \text{ A} = 2.2 \angle 180^\circ \text{ A}$$

The Norton equivalent circuit:

