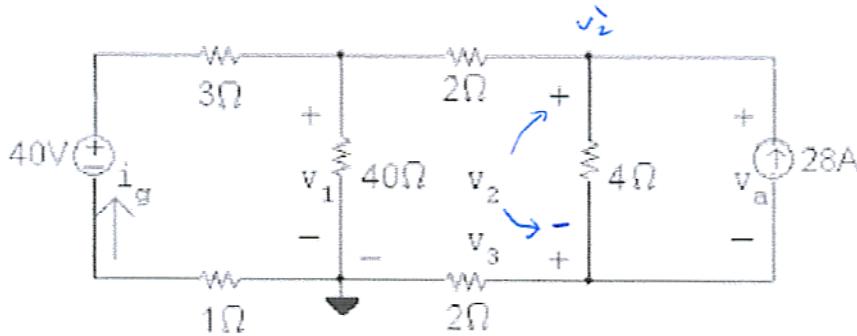


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE-201 ELECTRIC CIRCUITS
Dr. Ibrahim O. Habiballah

Sec: 9 Quiz # 2 Ser. # Name: I.D.#

For the circuit shown below, use nodal analysis to find

- " v_1 ", " v_2 ", and " v_3 "
- the power of the current source (indicating whether it is absorbed or delivered)



Solution:

The three node voltage equations are:

$$\begin{aligned}\frac{v_1 - 40}{4} + \frac{v_1}{40} + \frac{v_1 - v_2}{2} &= 0 \\ \frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{4} - 28 &= 0 \\ \frac{v_3}{2} + \frac{v_3 - v_2}{4} + 28 &= 0\end{aligned}$$

Place these equations in standard form:

$$\begin{aligned}v_1 \left(\frac{1}{4} + \frac{1}{40} + \frac{1}{2} \right) + v_2 \left(-\frac{1}{2} \right) + v_3(0) &= \frac{40}{4} \\ v_1 \left(-\frac{1}{2} \right) + v_2 \left(\frac{1}{2} + \frac{1}{4} \right) + v_3 \left(-\frac{1}{4} \right) &= 28 \\ v_1(0) + v_2 \left(-\frac{1}{4} \right) + v_3 \left(\frac{1}{2} + \frac{1}{4} \right) &= -28\end{aligned}$$

Solving, $v_1 = 60$ V; $v_2 = 73$ V; $v_3 = -13$ V. $\therefore v_2 = v_2 - v_3 = 86$ V

$$p_{28A} = -v_a(28\text{ A}) = -(v_2 - v_3)(28\text{ A}) = -(73 + 13)(28) = -2408 \text{ W}$$

The 28 A source delivers 2408 W.