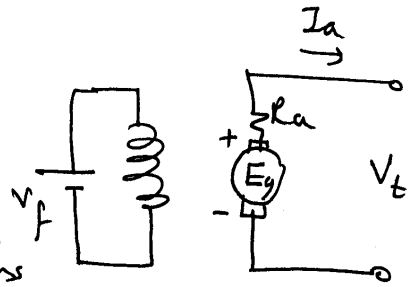


DC Machines

I - Lap Connection:


$P=8, Z=480, E_g=2.2V/Cond.$

$I_{Cond} = 100A$



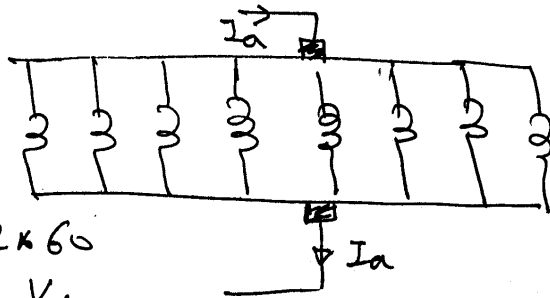(a) $p=a=8 \approx \# \text{ of parallel paths}$

$\# \text{ cond/path} = \frac{Z}{a}$
 $= \frac{480}{8} = 260$



induced emf/path = $2.2 \times 60 = 132V$

$E_g = 132 = \text{no load terminal voltage}$


(b) $I_{a, F.L.} = a \times \text{current/path}$
 $= 8 \times 100 = 800A$

(c) $P_d = E_g \times I_a = 132 \times 800 = \underline{105.6 kW}$

II - Wave Connected

$P=8, a=2$

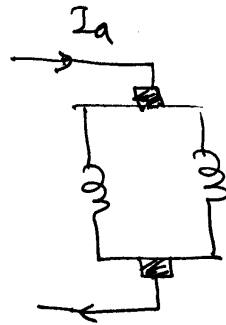$\# \text{ conductor/path} = \frac{480}{2} = 240$



(a) induced emf/path = $2.2 \times 240 = 528$
 $= \text{no load terminal voltage}$

(b) $I_{a, F.L.} = a \times \text{current/path}$
 $= 2 \times 100 = 200A$

(c) $P_d = E_g \times I_a = 528 \times 200 = \underline{105.6 kW}$

Note $P_{d1} = P_{d2}$ & $I_{a1} > I_{a2}$ & $E_{g1} < E_{g2}$


2. 500 V, 450 r.p.m., 750 kW

②

Protational = 12.18 kW

$R_a = 0.007 \Omega$

$R_f = 35 \Omega$.

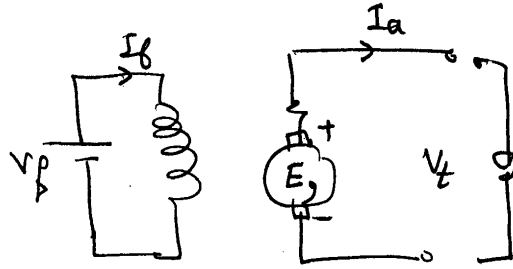

(a) $E_g = V_t + I_a R_a$

$I_{a.f.L} = \frac{750 \times 10^3}{500} = 1500 \text{ A}$

$\rightarrow E_g = 500 + 1500 \times 0.007 = 510.5 \text{ V}$

(b) $P_{iip} = P_o + P_{cu} + \text{Protational}$

$P_{cu} = I_a^2 R_a = (1500)^2 \times 0.007 = 15.75 \text{ kW}$

$\rightarrow P_{iip} = 750 + 15.75 + 12.18 = 777.93 \text{ kW}$
 = mechanical input power

(c) $T_{ip} = \frac{P_{iip}}{\omega_m} = \frac{777.93 \times 10^3}{2\pi \times \frac{450}{60}} = 16.51 \text{ k N.m}$

(d) $\eta = \frac{P_o}{P_{iip}} = \frac{P_o}{P_{iip} + P_{cu \text{ field}}}$

$P_{cu \text{ field}} = I_f^2 R_f = (15)^2 \times 35 = 6.86 \text{ kW}$

$\eta = \frac{750}{777.93 + 6.86} \times 100$

$= 95.57 \%$

(e) $N_2 = \frac{450}{2} = 225 \text{ r.p.m}$

$\frac{E_{g1}}{E_{g2}} = \frac{N_1}{N_2} \quad (\phi = \text{const}) \rightarrow E_{g2} = \frac{E_{g1}}{2} = \frac{510.5}{2}$

$\rightarrow P_{d_{max}} = E_{g2} \times I_{a.f.L} = \frac{510.5}{2} \times 1500 = 382.875$


$P_{o_{max}} = P_{d_{max}} - I_a^2 R_a = 382.875 - 15.75 = 367.125 \text{ kW}$

3. p28, shunt gen, $Z = 778$

wave, 500 r.p.m

5 kW, 250 V load

$R_a = 0.24 \Omega$, $R_f = 250 \Omega$

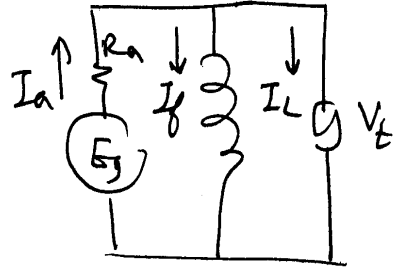

$$(a) I_L = \frac{P_L}{V_t} = \frac{5000}{250} = 20 \text{ A.}$$

$$I_f = \frac{V_t}{R_f} = \frac{250}{250} = 1 \text{ A.}$$

$$I_a = I_L + I_f = 20 + 1 = 21 \text{ A.}$$

$$(b) E_g = V_t + I_a R_a = 250 + 21 \times 0.24 = 255.04$$

$$(c) E_g = \frac{ZN\phi}{60} \left(\frac{P}{a} \right) \quad \text{for wave } a = 2$$

$$255.04 = \frac{778 \times 500 \times \phi}{60} \left(\frac{8}{2} \right)$$

$$\rightarrow \phi = 9.834 \text{ mwb.}$$

$$(d) P_d = E_g I_a = 255.04 \times 21 = 5.3558 \text{ kW.}$$

$$T_d = \frac{P_d}{2\pi \frac{N}{60}} = \frac{5.3558 \times 10^3}{2\pi \times \frac{500}{60}} = 102.29 \text{ N.m}$$

$$(e) \eta = \frac{P_o}{P_{i/p}} = \frac{P_o}{P_o + P_{cu} + P_{rotational}}$$

$$P_{cu} = I_a^2 R_a + I_f^2 R_f = (21)^2 \times 0.24 + (1)^2 \times 250 = 355.84 \text{ W}$$

$$\eta = \frac{5000}{5000 + 355.84 + 645} = 83.32\%$$

$$P_{i/p, mech} = 5000 + 355.84 + 645 = 6000.96 \text{ W.}$$

4.

220 V, shunt motor


$$R_a = 0.2 \Omega, R_f = 110 \Omega$$

$$I_L = 4 A \text{ at no-load}$$

$$I_L = 42 A \text{ at } 1000 \text{ r.p.m.}$$

$$I_f = \frac{220}{110} = 2 A$$

= constant at all conditions.

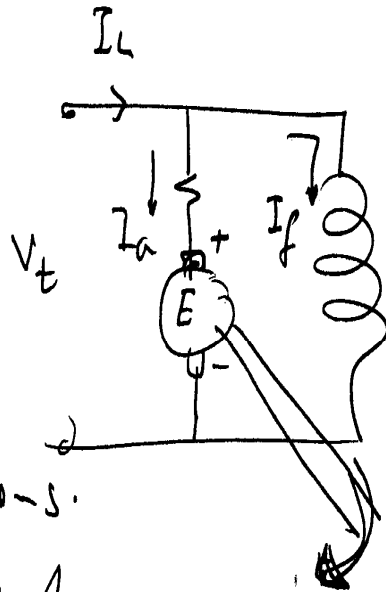

$$\rightarrow I_{a1} = I_{L1} - I_f = 4 - 2 = 2 A.$$

$$I_{a2} = I_{L2} - I_f = 42 - 2 = 40 A.$$

$$E_1 = V_t - I_{a1} R_a \rightarrow E_1 = 220 - 2 \times 0.2 = 219.6 V$$


$$E_2 = V_t - I_{a2} R_a \rightarrow E_2 = 220 - 40 \times 0.2 = 212 V.$$

$$\rightarrow \frac{E_1}{E_2} = \frac{N_1}{N_2} \quad (\phi = \text{const.}, \text{ where } I_f = \text{const.})$$

$$\rightarrow N_1 = \frac{E_1}{E_2} N_2 = \frac{219.6}{212} \times 1000 = 1035.84 \text{ r.p.m.}$$

5. 230V, DC shunt motor
 $R_a = 0.25$, $R_f = 115 \Omega$

At F.L. $I_a = 38 A$, $N = 1050$

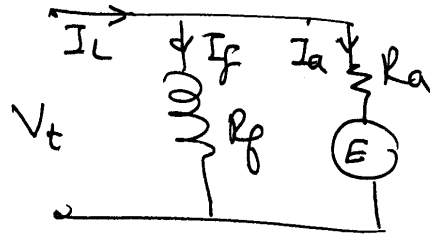

(a) $P_d = E I_a$

$$E_1 = V_t - I_a R_a$$

$$= 230 - 38 \times 0.25$$

$$= 220.5 \text{ V.}$$

$$P_d = 220.5 \times 38 = 8379 \text{ W.}$$

$$T_d = \frac{P_d}{2\pi \frac{N}{60}} = \frac{8379}{2\pi \frac{1050}{60}} = 76.2 \text{ N.m.}$$

(b) $R_f = 144$, Torque = Const, $I_a = \text{const}$

$$T \propto \phi I_a \rightarrow \phi_1 I_{a1} = \phi_2 I_{a2}$$

$$\text{Since } I_{a1} = I_{a2} \rightarrow \phi_1 = \phi_2 \rightarrow I_{f1} = I_{f2}$$

$$I_{f1} = \frac{230}{115} = 2 \text{ A} \rightarrow I_{f2} = 2 = \frac{V_t}{144}$$

$$\rightarrow V_{t2} = 288.$$

$$\rightarrow E_2 = V_{t2} - I_a R_a = 288 - (38)(0.25)$$

$$= 278.5 \text{ V}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \left(\phi_1 = \phi_2 \right)$$

$$N_2 = \frac{E_2}{E_1} N_1 = \frac{278.5}{220.5} \times 1050 = 1326.19 \text{ r.p.m.}$$

(c) $P_o = P_{d2} - \text{Protational} = 278.5 \times 38 - 600 = 9983$

$$\rightarrow \eta = \frac{9983}{288 \times 40}$$

$$= 86.65 \%$$

$$P_{iP} = V_t I_L = 288 \times 40$$

∴ [6.] A series Motor


$$R_a + R_f = 0.1$$

$$220 \text{ V, } 300 \text{ r.p.m} \rightarrow I = 25 \text{ A}$$

$$\text{voltage increased} \rightarrow N_2 = 400 \text{ r.p.m}$$

$$\text{Torque} \propto N^2$$

$$\phi \propto I$$

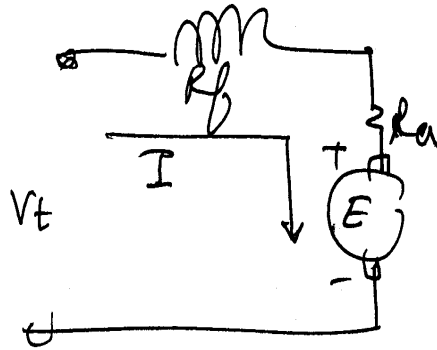

$$E_1 = V_t - I_a R_a$$

$$= 220 - 25 \times 0.1$$

$$= 217.5 \text{ V}$$

$$T = K I^2 \text{ for Series Motor}$$

$$\rightarrow \frac{T_1}{T_2} = \frac{I_1^2}{I_2^2} \text{ also we have } \frac{T_1}{T_2} = \frac{N_1^2}{N_2^2}$$

$$\rightarrow \left(\frac{I_1}{I_2}\right)^2 = \left(\frac{N_1}{N_2}\right)^2 \rightarrow \underline{I_2} = \left(\frac{N_2}{N_1}\right) I_1 = \frac{400}{300} \times 25 = \underline{33.33 \text{ A}}$$

$$\frac{E_1}{E_2} = \frac{\phi_1 I_1}{\phi_2 I_2} = \frac{I_1^2}{I_2^2}$$

$$\rightarrow E_2 = E_1 \frac{I_2^2}{I_1^2} = 217.5 \times \left(\frac{33.33}{25}\right)^2 = 386.66 \text{ V}$$

$$\rightarrow \underline{V_{t2}} = E_2 + I_2 (R_a + R_f)$$

$$= 386.66 + 33.33 (0.1) = \underline{389.99 \text{ V.}}$$

7)

Open circuit voltage = 230 V (from the curve)

Critical field resistance = 37.5 Ω