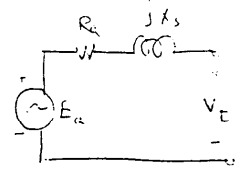


$$1) a) E_n = \frac{5720}{\sqrt{3}} = 4000 \text{ V}$$

$$R_a = \frac{5}{2(10)} = 0.25 \Omega / \text{phase}$$


$$Z = \frac{E_n}{I_{sc}} = \frac{4000}{800} = 5 \Omega / \text{phase}$$

$$X_s = \sqrt{Z^2 - R_a^2} = \sqrt{(5)^2 - (0.25)^2} = \underline{\underline{4.993 \Omega / \text{phase}}}$$



$$b) I_L = \frac{E}{Z_T} = \frac{E}{\sqrt{(12.25)^2 + (4.993)^2}} =$$
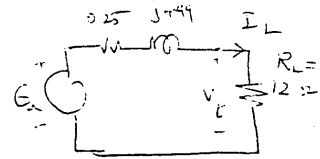
$$= \underline{\underline{302.37 \text{ Amp}}}$$



$$V_L = I_L R_L = 12(302.37) = \underline{\underline{3628.5 \text{ Volt (phase voltage)}}}$$

$$\Rightarrow \text{the line voltage is } 3628.5 \sqrt{3} = \underline{\underline{6284.74 \text{ V}}}$$

$$c) \% VR = \frac{4000 - 3628.5}{3628.5} \times 100 |$$

$$= \underline{\underline{10.2\%}}$$

From the open-circuit + short circuit tests

$$|Z_s| = \frac{E_{oc}(\text{ph})}{I_{sc}(\text{ph})} = \frac{32}{377} = 1.378 \Omega$$

From the Dc-test :

$$R_{dc} = \frac{V_{dc}}{2I_{dc}} = \frac{32}{200} = 0.16 \Omega$$

$$R_a = 1.5 \times R_{dc} = \underline{0.24 \Omega}$$

$$X_s = \sqrt{Z_s^2 - R_a^2} = \sqrt{(1.378)^2 - (0.24)^2} = \underline{1.36 \Omega}$$

$$\% VR = \frac{E_a - V_{tFL}}{V_{tFL}} \times 100\%$$

$$E_a = \sqrt{\left(V_t \cos \theta + \frac{I_a R_a}{FL} \right)^2 + \left(V_t \sin \theta \pm I_a X_s \right)^2} \quad \text{--- (A)}$$


Leading P.f.


$$I_{aFL} = \frac{1500 \times 10^3}{\sqrt{3} \times 2300} = \underline{377 \text{ A}} \quad ; \quad V_t = \frac{2300}{\sqrt{3}} = 1328 \text{ V}$$

at 0.8 p.f lag

$$E_a = \sqrt{\left(1328 \times 0.8 + 377 \times 0.24 \right)^2 + \left(1328 \times 0.6 + 377 \times 1.36 \right)^2} = \underline{1745 \text{ V}}$$
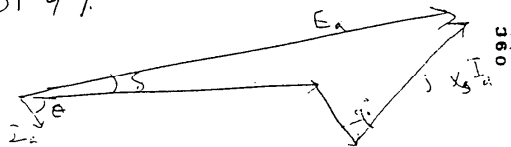
$$\% VR = \frac{1745 - 1328}{1328} \times 100\% = 31.4\%$$



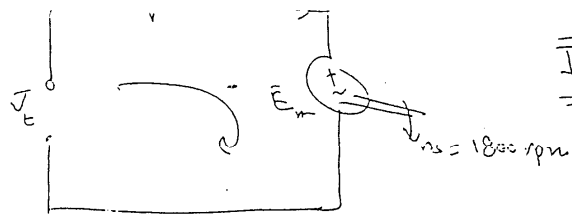


$$\bar{I}_a = 70 \angle 37^\circ \text{ A}$$

$$\bar{E}_m = \bar{V}_t - \bar{I}_a (R_a + jX_s)$$

$$\bar{E}_m = 3810 \angle 0^\circ - 70 \angle 37^\circ (2 + j20)$$

$$\bar{E}_m = 4697 \angle -14.8^\circ \text{ V}$$
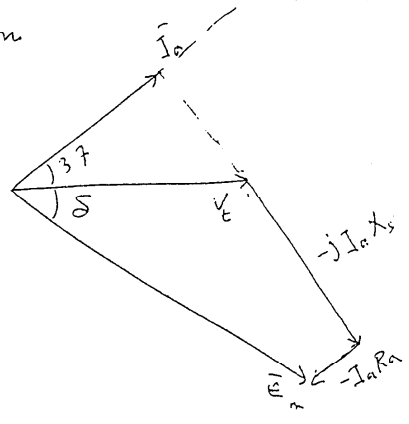
$$\textcircled{b} \quad E_L = \sqrt{3} \times 4697 \Rightarrow E_L = 8136 \text{ V}$$



Overexcited

$$\textcircled{d} \quad \delta = 14.8^\circ \text{ electrical degrees}$$

$$\text{or } \delta = \frac{14.8}{2} = 7.4 \text{ mechanical degrees}$$

$$\textcircled{e} \quad P_d = P_{in} - 3 I_a^2 R_a \Rightarrow P_{in} = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} (6600)(70) \times 0.8$$

$$= 3 V_t I_a \cos \theta = 3 (3810)(70) \times 0.8$$

$$P_{in} = 640.16 \text{ kW}$$

$$P_{copper} = 3 \times (70)^2 \times (2) = 29.4 \text{ kW}$$

$$P_d = 640.16 \text{ kW} - 29.4 \text{ kW} \Rightarrow P_d = 610.76 \text{ kW}$$

$$T_d = \frac{P_d}{\omega_s} = \frac{P_d}{2\pi \frac{n_s}{60}}, \quad n_s = \frac{120 \times f}{p} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$

$$\omega_s = \frac{2\pi \times 1800}{60} = 188.5 \text{ rad/sec}$$

$$\bar{T}_d = \frac{610.76 \times 10^3}{188.5} \Rightarrow \bar{T}_d = 3240.2 \text{ N-m}$$

$$\textcircled{f} \quad \eta = \frac{P_o}{P_{in}} \times 100, \quad P_o = P_d - P_{rot} = 610.76 \text{ kW} - 30 \text{ kW}$$

$$P_o = 580.76 \text{ kW}$$

$$\eta = \frac{580.76}{640.16} \times 100 \Rightarrow \eta = 90.7\%$$

$$\textcircled{g} \quad T_o = \frac{P_o}{\omega_s} = \frac{580.76 \times 10^3}{188.5} \Rightarrow T_o = 3080.9 \text{ N-m}$$

$$\begin{aligned}
 \text{a) } E_a &= V_t - j X_s I_a = \frac{6600}{\sqrt{3}} - j 30 (100 \angle -25.84^\circ) \\
 &= \underline{\underline{5787 \angle -27.8^\circ}} \text{ Volt.}
 \end{aligned}$$

$$\text{b) Rated torque} = \frac{\sqrt{3} \cdot 6600 (100) (0.9)}{2\pi \left(\frac{50}{3}\right)} = \underline{\underline{9827 \text{ Nm}}}$$

c) For maximum torque of 25000 Nm, we have.

$$25000 = 3 \frac{6600}{\sqrt{3}} \frac{E_a}{30} \times \frac{1}{2\pi \left(\frac{50}{3}\right)} \sin -90$$

$$\boxed{E_a = 6870 \text{ V}}$$

d) for the new excitation:

$$9827 = -3 \frac{6600}{\sqrt{3}} \frac{6870}{30} \frac{\sin \delta}{2\pi \left(\frac{50}{3}\right)}$$

$$\Rightarrow \sin \delta = -0.393 \text{ or } \boxed{\delta = -23.1^\circ}$$

$$\begin{aligned}
 I_{a \text{ new}} &= \frac{6600/\sqrt{3} - 6870(0.92 - j 0.393)}{j 30} = 122.9 \angle 42.9^\circ \\
 &\Rightarrow \cos \theta = \underline{\underline{0.732 \text{ lead}}}
 \end{aligned}$$

e) for rated torque at reduced voltage

$$9827 = 3 \frac{V_t}{\sqrt{3}} \frac{6870}{30} \frac{\sin 90}{2\pi \left(\frac{50}{3}\right)}$$