

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**ELECTRICAL ENGINEERING DEPARTMENT**

Dr. Ibrahim O. Habiballah

EE-360

Quiz 1

ser#:

I.D.:

Name:

A balanced three phase, 866-V, 60-Hz, Y-connected source feeds a balanced Δ -connected load via a 100-km long three wire transmission line. The impedance of each wire of the transmission line is $1 + j2 \Omega$. The per phase impedance of the load is $177 - j246 \Omega$. Determine the line and phase currents of the source and the load, the power absorbed by the load, and the power dissipated by transmission line.

Solution:

$$Z_Y = \frac{Z_{\Delta}}{3} = 59 - j82 \Omega$$

$$V_{ph} = \frac{866}{\sqrt{3}} = 500 \text{ V}$$

$$Z_{tot} = 1 + j2 + 59 - j82 = 60 - j80 = 100 \angle -53.13^{\circ} \Omega$$

$$I = \frac{500}{60 - j80} = 5 \angle 53.13^{\circ} \text{ A}$$

$$I_{ph \text{ source}} = I_L = 5 \angle 53.13^{\circ}$$

$$I_{ph \text{ load}} = \frac{I_L}{\sqrt{3} \angle -30^{\circ}} = \frac{5}{\sqrt{3}} \angle 83.13^{\circ} = 2.887 \angle 83.13^{\circ}$$

$$V_{L \text{ load}} = V_{ph \text{ load}} = I_{ph} * (177 - j246) = 874.93 \angle 28.87^{\circ}$$

$$P_{\text{Load}} = 3 I_{ph}^2 R_{ph} = 3 * (2.887)^2 * 177 = 4425.75 \text{ W}$$

$$P_{\text{line}} = 3 * I_L^2 R_{\text{line}} = 3 * (5)^2 * 1 = 75 \text{ W}$$