

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE 306

Solved HW # 1: Three-Phase Circuits

3-19

$S = 500 \text{ MVA}$, $V_L = V_{ph} = 345 \text{ kV}$, Δ -load, $PF = 0.866$ lagging

$$I_{ph} = \frac{(500,000/3)}{345} \angle -\cos^{-1} 0.866 = 483.1 \angle -30^\circ \text{ A}$$

$$\textcircled{1} Z_{2ph} = \frac{345 \angle 0^\circ \text{ kV}}{483.1 \angle -30^\circ \text{ A}} = 714.2 \angle 30^\circ \Omega$$

$$Z_{1ph} = \frac{1}{3} Z_{2ph} = 238 \angle 30^\circ \Omega$$

$$\textcircled{2} I_{ph} = 483.1 \angle -30^\circ \text{ A}$$

$$I_L = \sqrt{3} I_{ph} \angle 0^\circ = \sqrt{3} (483.1 \angle -30^\circ) \angle 0^\circ = 832.4 \angle 0^\circ \text{ A}$$

$$\textcircled{3} P_{ph} = 500 \cos 30^\circ = 433 \text{ MW}$$

$$Q_{ph} = 500 \sin 30^\circ = 250 \text{ MVAR}$$

$$\textcircled{4} P_T = 3 P_{ph} = 1300 \cos 30^\circ = 1119 \text{ MW}$$

$$Q_T = 3 Q_{ph} = 750 \sin 30^\circ = 375 \text{ MVAR}$$

3-22

$$S_M = 40 \text{ kVA}, V_M = 280 \text{ V}, PF_M = 0.65 \text{ lagging}$$

$$P_M = 40(0.65) = 26 \text{ kW}$$

$$\theta_M = \cos^{-1} 0.65 = 49.46^\circ$$

$$\textcircled{a} Q_M = P_M \tan \theta_M = 26 \tan 49.46^\circ = 30.4 \text{ kVAR}$$

$$PF_{\text{new}} = 0.95$$

$$\theta_{\text{new}} = \cos^{-1} 0.95 = 18.19^\circ$$

$$Q_{\text{new}} = P_M \tan \theta_{\text{new}} = 26 \tan 18.19^\circ = 8.54 \text{ kVAR} = Q_M + Q_C$$

$$\therefore Q_C = Q_{\text{new}} - Q_M = 8.54 - 30.4 = -21.86 \text{ kVAR}$$

$$\textcircled{b} I_{\text{before}} = \frac{40,000 \angle -49.46^\circ}{\sqrt{2}(280)} = 100 \angle -49.46^\circ$$

$$I_{\text{after}} = \frac{26,000 \angle -18.19^\circ}{\sqrt{2}(280)(0.95)} = 68.7 \angle -18.19^\circ$$

3-25

$$P_1 = 50 \text{ kW}, V = 400 \text{ V}_{\text{eff}}, \text{PF} = 0.8 \text{ lagging}$$

$$S_2 = 30 \text{ kVA}, V = 400 \text{ V}_{\text{eff}}, \text{PF} = 0.7 \text{ leading}$$

$$Z_{\text{eff}} = 25 + j2.0 \Omega, V_{\text{eff}} = \frac{400}{\sqrt{2}} \angle 0^\circ = 282.8 \angle 0^\circ \text{ V}_{\text{eff}}$$

$$I_1 = \frac{50,000 \angle -36.87^\circ}{282.8 \angle 0^\circ} = 176.8 \angle -36.87^\circ \text{ A}$$

$$I_2 = \frac{30,000 \angle 45^\circ}{282.8 \angle 0^\circ} = 106.1 \angle 45^\circ \text{ A}$$

$$\textcircled{a} Z_1 = \frac{282.8 \angle 0^\circ}{176.8 \angle -36.87^\circ} = 1.58 \angle 36.87^\circ \Omega$$

$$Z_2 = \frac{282.8 \angle 0^\circ}{106.1 \angle 45^\circ} = 2.67 \angle -45^\circ \Omega$$

$$\textcircled{b} I_T = I_1 + I_2 = 176.8 \angle -36.87^\circ + 106.1 \angle 45^\circ = 109.7 \angle -9.1^\circ$$


$$\begin{aligned} \textcircled{c} V_{\text{eff}} &= V_{\text{eff}} + Z_{\text{eff}} I_T = 282.8 \angle 0^\circ + (25 + j2.0)(109.7 \angle -9.1^\circ) \\ &= 402.7 \angle 28.5^\circ \text{ V}_{\text{eff}} \\ &= 282.8 \angle 28.5^\circ \text{ V}_{\text{eff}} \end{aligned}$$

$$\begin{aligned} \textcircled{d} S_{\text{eff}} &= \sqrt{2} V_{\text{eff}} I_T^* = \sqrt{2} (282.8 \angle 28.5^\circ)(109.7 \angle -9.1^\circ)^* \\ &= 126.5 \angle 37.6^\circ \text{ kVA} \\ &= 98.84 + j78.92 \text{ kVA} \end{aligned}$$

$$P_{\text{eff}} = 98.84 \text{ kW}$$

$$Q_{\text{eff}} = 78.92 \text{ kVAR}$$

3-27

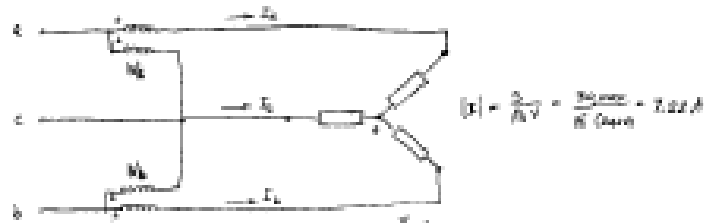

$$|I| = \frac{2000}{\sqrt{2} \times 900} = 2.22 \text{ A}$$

$$P_a = V_{L_a} I_a \cos \phi_a = \frac{V_s}{\sqrt{3}} I_a \cos \phi_a$$

$$P_b = V_{L_b} I_b \cos \phi_b = \frac{V_s}{\sqrt{3}} I_b \cos \phi_b$$

① PF = 1.0, $\phi = \cos^{-1} 1.0 = 0^\circ$

$$P_a = (2000/\sqrt{3})(2.22) \cos 0^\circ = 25 \text{ kW}$$

$$P_b = (2000/\sqrt{3})(2.22) \cos 0^\circ = 25 \text{ kW}$$

② PF = 0.7, $\phi = \cos^{-1} 0.7 = 72.5^\circ$ lagging

$$P_a = (2000/\sqrt{3})(2.22) \cos (90^\circ - 72.5^\circ) = 11.48 \text{ kW}$$

$$P_b = (2000/\sqrt{3})(2.22) \cos (90^\circ + 72.5^\circ) = -8.5 \text{ kW}$$

③ PF = 0.7, $\phi = \cos^{-1} 0.7 = 60^\circ$ leading

$$P_a = (2000/\sqrt{3})(2.22) \cos (90^\circ - 60^\circ) = 0$$

$$P_b = (2000/\sqrt{3})(2.22) \cos (90^\circ + 60^\circ) = 15 \text{ kW}$$

