KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE 306

Solved-HW # 4: DC Machines

6-18
(a)
$$I_{t} = 38 A$$

 $I_{f} = 2 A$
 $I_{R} = I_{t} - \hat{I}_{f} = 38 - 2 = 36 A$
 $I_{R} = V_{t} - R_{A} I_{R} = 230 - (0,15)(36) = 224.6 V$
 $K_{R} = \frac{PZ}{2\pi a} = \frac{(4)(596)}{2\pi (2)} = 189.7$
 $W_{m} = \frac{2\pi n}{40} = \frac{2\pi (1150)}{60} = 120.43 \text{ nad/sec}$
 $\phi_{p} = \frac{E_{R}}{K_{R}} = \frac{224.6}{(189.7)(120.43)} = 9.83 \text{ mWb}$
(b) $T_{e} = \frac{P_{dW}}{W_{m}} = \frac{E_{a}I_{a}}{W_{m}} = \frac{(224.6)(36)}{120.43} = 67.1 \text{ N-m}$

$$\begin{aligned} \mathbf{\hat{6-27}} \\ E_{a_{1}} &= V_{t} - (R_{x} + R_{s}) \overline{J_{a_{1}}} - V_{g_{p}} = 230 - (a_{y} + a_{z}\chi_{s_{1}}) - 2 = 205, g V \\ \end{aligned}$$

$$\begin{aligned} \mathbf{\hat{C}} \quad E_{a_{z}} &= 230 - (a_{y} + a_{s})(2a_{s}) - 2 = 246 V \\ \\ \frac{E_{a_{z}}}{E_{a_{1}}} &= \frac{K_{a} \frac{d_{z}}{d_{z}} (2\pi n_{z}/60)}{K_{a} \frac{d_{1}}{(2\pi n_{1}/60)}} = \frac{K_{x}' \overline{J_{a_{z}}} n_{z}}{K_{y}' \overline{J_{a_{1}}} n_{1}} \\ \\ n_{z} &= \left(\frac{E_{a_{z}}}{E_{a_{1}}}\right) \left(\frac{\overline{J_{a_{1}}}}{\overline{J_{a_{z}}}}\right) n_{1} = \left(\frac{216}{205, g}\right) (1200) = 2330 \text{ rpm} \end{aligned}$$

$$\begin{aligned} \mathbf{\hat{C}} \quad E_{a_{3}} &= 230 - (a_{y} + a_{z}\chi_{z}) - 2 = 227.4 V \\ \\ n_{3} &= \left(\frac{E_{a_{3}}}{E_{a_{1}}}\right) \left(\frac{\overline{J_{a_{1}}}}{\overline{J_{a_{3}}}}\right) n_{1} = \left(\frac{227.4}{205, g}\right) \left(\frac{37}{z}\right) (1200) = 49,060 \text{ rpm} \end{aligned}$$

$$\begin{aligned} \mathbf{\hat{C}} \quad E_{a_{4}} &= 230 - (a_{y} + a_{z}z)(60) - 2 = 192 V \\ \\ \\ n_{4} &= \left(\frac{E_{a_{4}}}{E_{a_{1}}}\right) \left(\frac{d_{1}}{d_{z}}\right) n_{1} = \left(\frac{192}{205, g}\right) \left(\frac{1.25 \frac{d_{1}}{d_{1}}}{d_{1}}\right) (1200) = 1399 \text{ rpm} \end{aligned}$$