

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE 306

Solved-HW # 5: Synchronous Machines

D7-4

$$\textcircled{a} \quad \frac{E_2}{E_1} = \frac{4.44 k_w f_2 N_a \phi_2}{4.44 k_w f_1 N_a \phi_1} = \frac{f_2 \phi_2}{f_1 \phi_1} = \frac{(P n_2 / 120) \phi_2}{(P n_1 / 120) \phi_1} = \frac{n_2 \phi_2}{n_1 \phi_1}$$

$$E_2 = \left(\frac{n_2}{n_1}\right) \left(\frac{\phi_2}{\phi_1}\right) E_1 = \left(\frac{1.1 n_1}{n_1}\right) \left(\frac{0.85 \phi_1}{\phi_1}\right) 620 = 580 \text{ V}$$

\textcircled{b}

$$\frac{P n_2}{P n_1} = \frac{120 f_2}{120 f_1}$$

$$f_2 = \left(\frac{n_2}{n_1}\right) f_1 = \left(\frac{1.1 n_1}{n_1}\right) 60 = 66 \text{ Hz}$$

D7-8

$$V_t = \frac{12000}{\sqrt{3}} \angle 0^\circ = 6928 \angle 0^\circ \text{ V}$$

$$I_a = \frac{750,000}{\sqrt{3} (12000) (0.8)} \angle -\cos^{-1} 0.8 = 45.1 \angle -36.9^\circ \text{ A}$$

$$\begin{aligned} E_a &= V_t + j X_s I_a = 6928 \angle 0^\circ + (j30)(45.1 \angle -36.9^\circ) \\ &= 7815.6 \angle 7.96^\circ \text{ V} \end{aligned}$$

$$\text{V.R.} = \frac{E_a - V_t}{V_t} = \frac{7815.6 - 6928}{6928} 100\% = 12.8\%$$

D7-17

$$V_t = \frac{4160}{\sqrt{3}} = 2401.8 \angle 0^\circ$$

$$E_a = \frac{4600}{\sqrt{3}} = 2655.8 \angle -\delta$$

$$P = \frac{3V_t E_a}{X_s} \sin \delta = \frac{(3)(2401.8)(2655.8)}{10} \sin \delta = 1,914 \sin \delta$$

$$\sin \delta = \frac{1500}{1914}$$

$$\delta = 51.6^\circ$$

$$(a) \quad \bar{I}_a = \frac{V_t - \bar{E}_a}{jX_s} = \frac{2401.8 \angle 0^\circ - 2655.8 \angle -51.6^\circ}{j10} = 221.3 \angle -19.9^\circ$$

$$(b) \quad \text{PF} = \cos 19.9^\circ = 0.94 \text{ lagging}$$

7-9

$$(a) \quad S = 50 + j30 = 58.31 \angle 31^\circ \text{ MVA}$$

$$\bar{I}_a = \frac{S^*}{\sqrt{3}V^*} = \frac{(58.31 \angle 31^\circ)^*}{\sqrt{3}(13.8)} = 2,439.5 \angle -31^\circ \text{ A}$$

$$V_t = \frac{13.8}{\sqrt{3}} \angle 0^\circ = 7967.4 \angle 0^\circ \text{ V}$$

$$E_a = V_t + jX_s \bar{I}_a = 7967.4 \angle 0^\circ + (j7.5)(2439.5 \angle -31^\circ)$$

$$= 23,418 \angle 42^\circ \text{ V}_{LN} = 40,561 \text{ V}_{LL} = 40.56 \text{ kV}_{LL}$$

$$\delta = 42^\circ$$

(b)

