

# KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

## ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-306

### Key Solution

Quiz 1            Sec.: 2            I.D.:            Name:

A three-phase substation bus supplies two wye-connected loads that are connected in parallel. Load 1 draws 50 kW at 0.866 lagging power factor, and load 2 draws 36 kVA at 0.9 leading power factor. The line-to-line voltage at the loads is 460 V.

Total real and reactive power supplied by the substation bus is

- a.  $P = 98.8 \text{ kW}$  ;  $Q = 78.9 \text{ kVAR}$  (inductive)
- b.  $P = 98.8 \text{ kW}$  ;  $Q = 78.9 \text{ kVAR}$  (capacitive)
- c.  $P = 82.2 \text{ kW}$  ;  $Q = 13.17 \text{ kVAR}$  (inductive)
- d.  $P = 82.2 \text{ kW}$  ;  $Q = 13.17 \text{ kVAR}$  (capacitive)

$$P_{\text{total}} = 50 + 36(0.9) = 82.8 \text{ kW}$$

$$Q_{L1} = 50 * (\sin (\cos^{-1}(.866))/0.866) = 28.87 \text{ kVAR (inductive)}$$

$$Q_{L2} = 36 \sin (\cos^{-1}(.9)) = 15.7 \text{ (capacitive)}$$

$$Q_{\text{total}} = 28.87 - 15.7 = 13.17 \text{ kVAR (inductive)}$$