

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-306

Key Solution

Quiz 1

Sec.: 3

I.D.:

Name:

A three-phase substation bus supplies a wye-connected load through a three-phase feeder with impedance of $0.5 + j 2.0$ Ohm per phase. The load draws 36 kVA at 0.9 leading power factor. The line-to-line voltage at the load is 460 V.

The impedance for each phase of the load is

- a. $Z_L = 5.88 \angle 25.8^\circ \Omega$
- b. $Z_L = 5.88 \angle -25.8^\circ \Omega$
- c. $Z_L = 3.4 \angle 25.8^\circ \Omega$
- d. $Z_L = 3.4 \angle -25.8^\circ \Omega$

$$I = 36 / (\sqrt{3} * 460) = 45.18 \angle 25.8^\circ \text{ A}$$

$$Z_L = (460 / \sqrt{3}) / 45.18 \angle 25.8^\circ = 5.88 \angle -25.8^\circ \Omega$$