

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
Dr. Ibrahim O. Habiballah
EE-306

Key Solution

Quiz 1 Sec.: 4 I.D.: Name:

A three-phase substation bus supplies a wye-connected load through a three-phase feeder with impedance of $0.5 + j 2.0$ Ohm per phase. The load draws (absorbs) 50 kW at 0.866 lagging power factor. The line-to-line voltage at the load is 460 V.

The impedance of each phase of the load is

- a. $Z_L = 3.66 \angle 30^\circ \Omega$;
- b. $Z_L = 3.66 \angle -30^\circ \Omega$;
- c. $Z_L = 2.12 \angle 30^\circ \Omega$;
- d. $Z_L = 2.12 \angle -30^\circ \Omega$;

$$I = 50 / (\text{sqrt}(3) * 460 * .866) = 72.47 \angle -30^\circ \text{ A}$$

$$Z_L = (460 / \text{sqrt}(3)) / 72.47 \angle -30^\circ = 3.66 \angle 30^\circ \Omega$$