

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-360

Key Solutions


Quiz # 6 Serial #

Name:

I.D.#

Circle the correct answer.

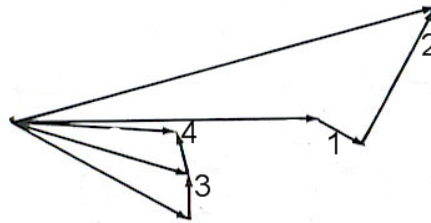1) In the phasor diagram of a Pi-nominal transmission line shown below, number "1" must be (.....), number "2" must be (.....), number "3" must be (.....), and number "4" must be (.....).



- a) $R \cdot I_R$; $j X_L (I_R + I_{CR})$; I_{CR} ; I_{CS} .
- b) $R \cdot I$; $j X_L \cdot I$; I_{CR} ; I_{CS} .**
- c) $0.5 \cdot R \cdot I_R$; $j 0.5 \cdot X_L (I_R + I_{CR})$; I_{CR} ; I_{CS} .
- d) $0.5 \cdot R \cdot I_R$; $j 0.5 \cdot X_L \cdot I_R$; I_C ; I_S .

(5 Marks)

2) A 60 Hz, 200 km, 3-phase, transmission line has a series impedance $(0.08 + j 0.48)$ Ohm/km and a shunt admittance $(j 3.33 \times 10^{-6})$ S/km. The "B" constant of the line using the pi-nominal model is

- a. $0.968 \angle 0.315^\circ$
- b. $97.32 \angle 80.54^\circ$**
- c. $6.553 \times 10^{-4} \angle 90.155^\circ$
- d. $6.66 \times 10^{-4} \angle 90^\circ$

(5 Marks)