

EE 460
Solution of Home Work #2a

5.1 (a) $\bar{A} = \bar{D} = 1.0 \angle 0^\circ \text{ pu}; \bar{C} = 0. \text{ S}$

$$\bar{B} = \bar{Z} = (0.19 + j0.34)25 = 9.737 \angle 60.8^\circ \Omega$$

(b) $\bar{V}_R = \frac{33}{\sqrt{3}} \angle 0^\circ = 19.05 \angle 0^\circ \text{ kV}_{\text{LN}}$

$$\bar{I}_R = \frac{S_R \angle -\cos^{-1}(pf)}{\sqrt{3} V_{R-L-L}} = \frac{10}{\sqrt{3}(33)} \angle -\cos^{-1}(0.9)$$

$$= 0.175 \angle -25.84^\circ \text{ kA}$$

$$\bar{V}_S = \bar{A}\bar{V}_R + \bar{B}\bar{I}_R = (1.0)(19.05) + (9.737 \angle 60.8^\circ)(0.175 \angle -25.84^\circ)$$

$$= 20.45 + j0.976 = 20.47 \angle 2.732^\circ \text{ kV}_{\text{L-N}}$$

$$V_{S_{L-L}} = 20.47\sqrt{3} = 35.45 \text{ kV}$$

(c) $\bar{I}_R = 0.175 \angle 25.84^\circ$

$$\bar{V}_S = \bar{A}\bar{V}_R + \bar{B}\bar{I}_R = (1.0)(19.05) + (9.737 \angle 60.8^\circ)(0.175 \angle 25.84^\circ)$$

$$= 19.15 + j1.701 = 19.23 \angle 5.076^\circ \text{ kV}_{\text{L-N}}$$

$$V_{S_{L-L}} = 19.23\sqrt{3} = 33.3 \text{ kV}$$

$$5.7 \quad V_s = \frac{3300}{\sqrt{3}} = 1905.3 \text{ V (Line-to-neutral)}$$

$$0.5 \angle 53.13^\circ = 0.5(0.6 + j0.8) = 0.3 + j0.4$$

$$I = \frac{(900/3)10^3}{0.8 \times V_R} = \frac{375 \times 10^3}{V_R} \text{ A}$$

From the phasor diagram drawn below with \bar{I} as reference,

$$V_s^2 = (V_R \cos \phi_R + IR)^2 + (V_R \sin \phi_R + IX)^2 \quad (1)$$


$$(1905.3)^2 = \left(0.8V_R + \frac{375 \times 10^3 \times 0.3}{V_R} \right)^2 + \left(0.6V_R + \frac{375 \times 10^3 \times 0.4}{V_R} \right)^2$$

From which one gets $V_R = 1805 \text{ V}$

(a) Line-to-line voltage at receiving end = $1805\sqrt{3}$
 $= 3126 \text{ V} \leftarrow$
 $= 3.126 \text{ kV}$

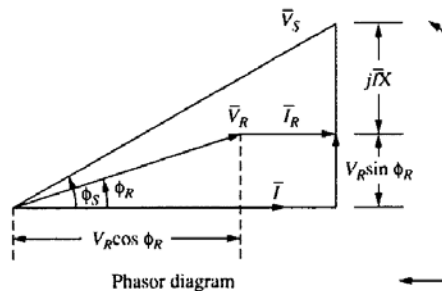(b) Line current is given by

$$I = \frac{375 \times 10^3}{1805} = 207.76 \text{ A} \leftarrow$$



$$5.14 \quad (a) \quad \bar{Z}_c = \sqrt{\frac{\bar{z}}{\bar{y}}} = \sqrt{\frac{0.03 + j0.35}{4.4 \times 10^{-6} \angle 90^\circ}} = 282.6 \angle -2.45^\circ \Omega$$

$$(b) \quad \bar{\gamma}l = \sqrt{\bar{z}\bar{y}(l)} = \sqrt{(0.35128 \angle 85.101^\circ)(4.4 \times 10^{-6} \angle 90^\circ)}(400) \\ = 0.4973 \angle 87.55^\circ = 0.02126 + j0.4968 \text{ pu}$$

$$(c) \quad \bar{A} = \bar{D} = \cosh \bar{\gamma}l = \cosh(0.02126 + j0.4968) \\ = (\cosh 0.02126)(\cos 0.4968 \text{ radians}) + j(\sinh 0.02126)(\sin 0.4968 \text{ radians}) \\ = (1.00023)(0.87911) + j(0.02126)(0.47661) \\ = 0.87931 + j0.01013 = 0.8794 \angle 0.66^\circ \text{ pu} \\ \sinh \bar{\gamma}l = \sinh(0.02126 + j0.4968) \\ = \sinh(0.02126)\cos(0.4968 \text{ radians}) + j(\cosh 0.02126)(\sin 0.4968 \text{ radians}) \\ = (0.02126)(0.87911) + j(1.00023)(0.47661) \\ = 0.01869 + j0.4767 = 0.4771 \angle 87.75^\circ \\ \bar{B} = \bar{Z}_c \sinh(\bar{\gamma}l) = (282.6 \angle -2.45^\circ)(0.4771 \angle 87.75^\circ) \\ = 134.8 \angle 85.3^\circ \Omega \\ \bar{C} = \frac{1}{\bar{Z}_c} \sinh(\bar{\gamma}l) = \frac{0.4771 \angle 87.75^\circ}{282.6 \angle -2.45^\circ} = 1.688 \times 10^{-3} \angle 90.2^\circ \text{ S}$$