

Q 2.1

SOLUTION

(a) The turns ratio of this transformer is $a = 8000/277 = 28.88$. Therefore, the primary impedances referred to the low voltage (secondary) side are

$$R_p' = \frac{R_p}{a^2} = \frac{5 \Omega}{(28.88)^2} = 0.006 \Omega$$


$$X_p' = \frac{X_p}{a^2} = \frac{6 \Omega}{(28.88)^2} = 0.0072 \Omega$$

and the excitation branch elements referred to the secondary side are


$$R_c' = \frac{R_c}{a^2} = \frac{50 \text{ k}\Omega}{(28.88)^2} = 60 \Omega$$

$$X_M' = \frac{X_M}{a^2} = \frac{10 \text{ k}\Omega}{(28.88)^2} = 12 \Omega$$

The resulting equivalent circuit is

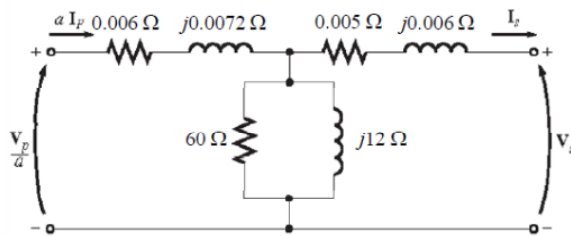

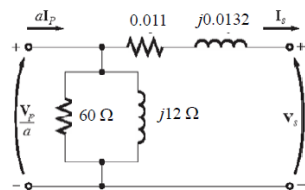(c) To simplify the calculations, use the simplified equivalent circuit referred to the secondary side of the transformer:



The secondary current in this transformer is

$$I_s = \frac{100 \text{ kVA}}{277 \text{ V}} \angle -31.8^\circ \text{ A} = 361 \angle -31.8^\circ \text{ A}$$

Therefore, the primary voltage on this transformer (referred to the secondary side) is

$$V_p' = V_s + (R_{\text{RQ}} + jX_{\text{RQ}}) I_s$$

$$V_p' = 277 \angle 0^\circ \text{ V} + (0.011 + j0.0132)(361 \angle -31.8^\circ \text{ A}) = 283 \angle 0.4^\circ \text{ V}$$

The voltage regulation of the transformer under these conditions is

$$\text{VR} = \frac{283 - 277}{277} \times 100\% = 2.2\%$$

(d) Under the conditions of part (c), the transformer's output power copper losses and core losses are:

$$P_{\text{OUT}} = S \cos \theta = (100 \text{ kVA})(0.85) = 85 \text{ kW}$$

$$P_{\text{CU}} = (I_s)^2 R_{\text{RQ}} = (361)^2 (0.11) = 1430 \text{ W}$$

$$P_{\text{core}} = \frac{V_p'^2}{R_c} = \frac{283^2}{50} = 1602 \text{ W}$$

(e) The efficiency of this transformer is

$$\eta = \frac{P_{\text{OUT}}}{P_{\text{OUT}} + P_{\text{CU}} + P_{\text{core}}} \times 100\% = \frac{85,000}{85,000 + 1430 + 1602} \times 100\% = 96.6\%$$

Q2.6

SOLUTION

(a) **OPEN CIRCUIT TEST** (referred to the low-voltage or secondary side):

$$|Y_{EX}| = |G_C - jB_M| = \frac{0.11 \text{ A}}{115 \text{ V}} = 0.0009565 \text{ S}$$

$$\theta = \cos^{-1} \frac{P_{OC}}{V_{OC} I_{OC}} = \cos^{-1} \frac{3.9 \text{ W}}{(115 \text{ V})(0.11 \text{ A})} = 72.0^\circ$$

$$Y_{EX} = G_C - jB_M = 0.0009565 \angle -72^\circ \text{ S} = 0.0002956 - j0.0009096 \text{ S}$$

$$R_C = \frac{1}{G_C} = 3383 \ \Omega$$

$$X_M = \frac{1}{B_M} = 1099 \ \Omega$$

SHORT CIRCUIT TEST (referred to the high-voltage or primary side):

$$|Z_{EQ}| = |R_{EQ} + jX_{EQ}| = \frac{17.1 \text{ V}}{8.7 \text{ A}} = 1.97 \ \Omega$$


$$\theta = \cos^{-1} \frac{P_{SC}}{V_{SC} I_{SC}} = \cos^{-1} \frac{38.1 \text{ W}}{(17.1 \text{ V})(8.7 \text{ A})} = 75.2^\circ$$

$$Z_{EQ} = R_{EQ} + jX_{EQ} = 1.97 \angle 75.2^\circ \ \Omega = 0.503 + j1.905 \ \Omega$$

$$R_{EQ} = 0.503 \ \Omega$$

$$X_{EQ} = j1.905 \ \Omega$$

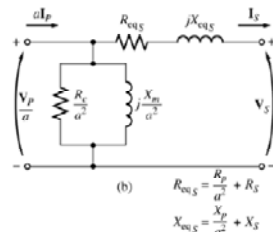To convert the equivalent circuit to the secondary side, divide each series impedance by the square of the turns ratio ($a = 230/115 = 2$). Note that the excitation branch elements are already on the secondary side. The resulting equivalent circuit is shown below:



$$R_{EQ,S} = 0.126 \ \Omega$$

$$X_{EQ,S} = j0.476 \ \Omega$$

$$R_{C,S} = 3383 \ \Omega$$

$$X_{M,S} = 1099 \ \Omega$$

(b) To find the required voltage regulation, we will use the equivalent circuit of the transformer referred to the secondary side. The rated secondary current is

$$I_s = \frac{1000 \text{ VA}}{115 \text{ V}} = 8.70 \text{ A}$$

We will now calculate the primary voltage referred to the secondary side and use the voltage regulation equation for each power factor.

(1) **0.8 PF Lagging:**

$$V_p' = V_s + Z_{EQ} I_s = 115 \angle 0^\circ \text{ V} + (0.126 + j0.476 \ \Omega)(8.7 \angle -36.87^\circ \text{ A})$$

$$V_p' = 118.4 \angle 1.3^\circ \text{ V}$$

$$\text{VR} = \frac{118.4 - 115}{115} \times 100\% = 2.96\%$$

(2) **1.0 PF:**

$$V_p' = V_s + Z_{EQ} I_s = 115 \angle 0^\circ \text{ V} + (0.126 + j0.476 \ \Omega)(8.7 \angle 0.0^\circ \text{ A})$$

$$V_p' = 116.2 \angle 2.04^\circ \text{ V}$$

$$\text{VR} = \frac{116.2-115}{115} \times 100\% = 1.04\%$$

(3) **0.8 PF Leading:**

$$\mathbf{V}_p' = \mathbf{V}_s + \mathbf{Z}_{\text{EQ}} \mathbf{I}_s = 115 \angle 0^\circ \text{ V} + (0.126 + j0.476 \Omega)(8.7 \angle 36.87^\circ \text{ A})$$

$$\mathbf{V}_p' = 113.5 \angle 2.0^\circ \text{ V}$$

$$\text{VR} = \frac{113.5-115}{115} \times 100\% = -1.3\%$$

(c) At rated conditions and 0.8 PF lagging, the output power of this transformer is

$$P_{\text{OUT}} = V_s I_s \cos \phi = (115 \text{ V})(8.7 \text{ A})(0.8) = 800 \text{ W}$$

The copper and core losses of this transformer are

$$P_{\text{CU}} = I_s^2 R_{\text{EQ},s} = (8.7 \text{ A})^2 (0.126 \Omega) = 9.5 \text{ W}$$

$$P_{\text{core}} = \frac{(V_p')^2}{R_c} = \frac{(118.4 \text{ V})^2}{3383 \Omega} = 4.1 \text{ W}$$

Therefore the efficiency of this transformer at these conditions is

$$\eta = \frac{P_{\text{OUT}}}{P_{\text{OUT}} + P_{\text{CU}} + P_{\text{core}}} \times 100\% = \frac{800 \text{ W}}{800 \text{ W} + 9.5 \text{ W} + 4.1 \text{ W}} = 98.3\%$$

Q2.7

SOLUTION

(a) The easiest way to solve this problem is to refer all components to the *primary* side of the transformer. The turns ratio is $a = 8000/230 = 34.78$. Thus the load impedance referred to the primary side is

$$\mathbf{Z}_L' = (34.78)^2 (2.0 + j0.7 \Omega) = 2419 + j847 \Omega$$

The referred secondary current is

$$\mathbf{I}_s' = \frac{7967 \angle 0^\circ \text{ V}}{(20 + j100 \Omega) + (2419 + j847 \Omega)} = \frac{7967 \angle 0^\circ \text{ V}}{2616 \angle 21.2^\circ \Omega} = 3.045 \angle -21.2^\circ \text{ A}$$

and the referred secondary voltage is

$$\mathbf{V}_s' = \mathbf{I}_s' \mathbf{Z}_L' = (3.045 \angle -21.2^\circ \text{ A})(2419 + j847 \Omega) = 7804 \angle -1.9^\circ \text{ V}$$

The actual secondary voltage is thus

$$\mathbf{V}_s = \frac{\mathbf{V}_s'}{a} = \frac{7804 \angle -1.9^\circ \text{ V}}{34.78} = 224.4 \angle -1.9^\circ \text{ V}$$

The voltage regulation is

$$\text{VR} = \frac{7967-7804}{7804} \times 100\% = 2.09\%$$

(b) The easiest way to solve this problem is to refer all components to the *primary* side of the transformer. The turns ratio is again $a = 34.78$. Thus the load impedance referred to the primary side is

$$\mathbf{Z}_L' = (34.78)^2 (-j3.0 \Omega) = -j3629 \Omega$$

The referred secondary current is

$$\mathbf{I}_s' = \frac{7967 \angle 0^\circ \text{ V}}{(20 + j100 \Omega) + (-j3629 \Omega)} = \frac{7967 \angle 0^\circ \text{ V}}{3529 \angle -89.7^\circ \Omega} = 2.258 \angle 89.7^\circ \text{ A}$$

and the referred secondary voltage is

$$\mathbf{V}_s' = \mathbf{I}_s' \mathbf{Z}_L' = (2.258 \angle 89.7^\circ \text{ A})(-j3629 \Omega) = 8194 \angle -0.3^\circ \text{ V}$$

The actual secondary voltage is thus

$$\mathbf{V}_s = \frac{\mathbf{V}_s'}{a} = \frac{8194 \angle -0.3^\circ \text{ V}}{34.78} = 235.6 \angle -0.3^\circ \text{ V}$$

The voltage regulation is


$$\text{VR} = \frac{7967 - 8194}{8194} \times 100\% = -10.6\%$$

P1)

$$a = \frac{2400}{240} = 10$$

$$R'_2 = 0.0075(10)^2 = 0.75 \Omega$$

$$X'_2 = 0.01(10)^2 = 1 \Omega$$

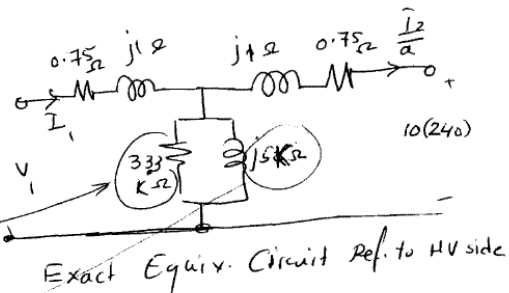

a)

Note
 $R_C = 33.3 \text{ k}\Omega$
 $X_M = 5 \text{ k}\Omega$

b)

$$\vec{I}_2 = \frac{50 \times 10^3}{10(2400)} \angle -\cos^{-1} 0.8$$



$$\vec{I}_2 = 20.8 \angle -36.9^\circ \text{ A}$$

$$\vec{V}_2 = 2400 \angle 0 + (20.8 \angle -36.9^\circ) Z_{eq}$$

$$Z_{eq} = (0.75 + 0.75 + 0.5) + j(1 + 1 + 2)$$

$$\vec{V}_2 = 2400 \angle 0 + (20.8 \angle -36.9^\circ)(2 + j4)$$
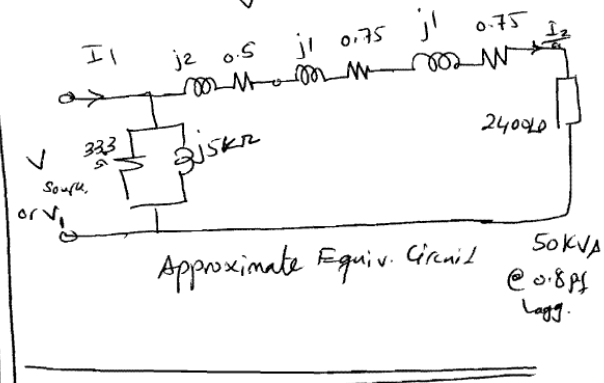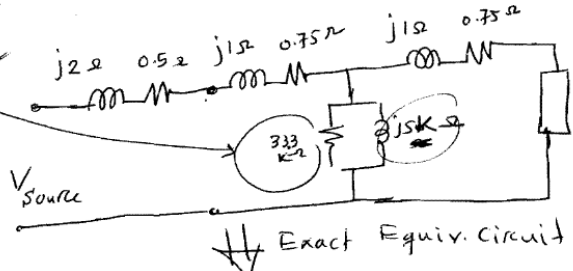
$$\vec{V}_2 = 2483.5 \angle 0.96^\circ \text{ V}$$



$$\% \text{ VR} = \frac{|V_1| - |V_2|}{|V_2|} \times 100\%$$

$$= \frac{2483.5 - 2400}{2400} \times 100\%$$

$$\% \text{ VR} = 3.48\%$$

$$\% \text{ efficiency} = \frac{P_{out}}{P_{out} + P_{loss}} = 97.4\%$$

$$P_{out} = 50 \times 10^3 (0.8) = 40 \text{ kW}$$

$$P_{loss} = (0.75 + 0.75 + 0.5) \left(\frac{I_2}{a}\right)^2 + \frac{|V_1|^2}{R_C}$$

$$= (2.0) (20.8)^2 + \frac{(2483.5)^2}{333 \times 10^3}$$

$$P_{loss} = 1050.5 \text{ W}$$

$$\Rightarrow \% \text{ eff} = \frac{40 \times 10^3}{40 \times 10^3 + 1050.5} \times 100\% = 97.4\%$$