

King Fahd University of Petroleum & Minerals
Department of Electrical Engineering
EE 360: Home Work # 2
Due Date (3rd March)

Key Solutions

Q1) Problem 2-1 (a, c, d, e)

SOLUTION

(a) The turns ratio of this transformer is $a = 8000/277 = 28.88$. Therefore, the primary impedances referred to the low voltage (secondary) side are

$$R_p' = \frac{R_p}{a^2} = \frac{5 \Omega}{(28.88)^2} = 0.006 \Omega$$


$$X_p' = \frac{X_p}{a^2} = \frac{6 \Omega}{(28.88)^2} = 0.0072 \Omega$$

and the excitation branch elements referred to the secondary side are


$$R_c' = \frac{R_c}{a^2} = \frac{50 \text{ k}\Omega}{(28.88)^2} = 60 \Omega$$

$$X_M' = \frac{X_M}{a^2} = \frac{10 \text{ k}\Omega}{(28.88)^2} = 12 \Omega$$

The resulting equivalent circuit is

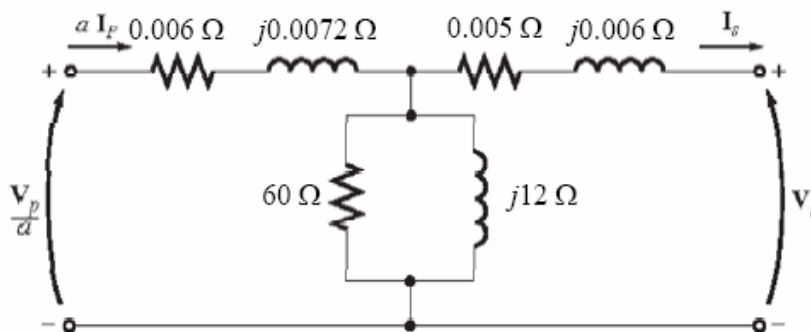

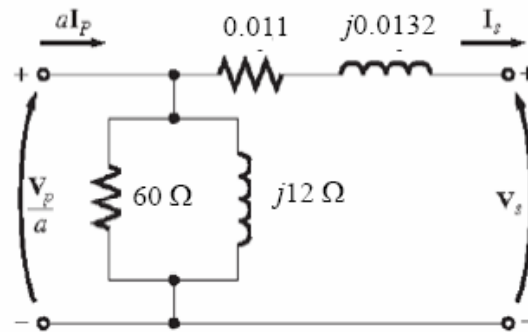(c) To simplify the calculations, use the simplified equivalent circuit referred to the secondary side of the transformer:



The secondary current in this transformer is

$$I_s = \frac{100 \text{ kVA}}{277 \text{ V}} \angle -31.8^\circ \text{ A} = 361 \angle -31.8^\circ \text{ A}$$

Therefore, the primary voltage on this transformer (referred to the secondary side) is

$$\begin{aligned} V_p' &= V_s + (R_{EQ} + jX_{EQ}) I_s \\ V_p' &= 277 \angle 0^\circ \text{ V} + (0.011 + j0.0132)(361 \angle -31.8^\circ \text{ A}) = 283 \angle 0.4^\circ \text{ V} \end{aligned}$$

The voltage regulation of the transformer under these conditions is

$$\text{VR} = \frac{283 - 277}{277} \times 100\% = 2.2\%$$

(d) Under the conditions of part (c), the transformer's output power copper losses and core losses are:

$$\begin{aligned} P_{\text{OUT}} &= S \cos \theta = (100 \text{ kVA})(0.85) = 85 \text{ kW} \\ P_{\text{CU}} &= (I_s)^2 R_{EQ} = (361)^2 (0.11) = 1430 \text{ W} \\ P_{\text{core}} &= \frac{V_p'^2}{R_c} = \frac{283^2}{50} = 1602 \text{ W} \end{aligned}$$

(e) The efficiency of this transformer is

$$\eta = \frac{P_{\text{OUT}}}{P_{\text{OUT}} + P_{\text{CU}} + P_{\text{core}}} \times 100\% = \frac{85,000}{85,000 + 1430 + 1602} \times 100\% = 96.6\%$$

Q2) Problem 2-2

SOLUTION

To solve this problem, we will refer the circuit to the secondary (low-voltage) side. The feeder's impedance referred to the secondary side is

$$Z_{\text{line}}' = \left(\frac{2.4 \text{ kV}}{14 \text{ kV}} \right)^2 (38.2 \Omega + j140 \Omega) = 1.12 + j4.11 \Omega$$

The secondary current I_S is given by

$$I_S = \frac{90 \text{ kW}}{(2400 \text{ V})(0.8)} = 46.88 \text{ A}$$

The power factor is 0.80 lagging, so the impedance angle $\theta = \cos^{-1}(0.8) = 36.87^\circ$, and the phasor current is

$$I_S = 46.88 \angle -36.87^\circ \text{ A}$$

(a) The voltage at the power source of this system (referred to the secondary side) is

$$V_{\text{source}}' = V_S + I_S Z_{\text{line}}' + I_S Z_{\text{EQ}}$$

$$V_{\text{source}}' = 2400 \angle 0^\circ \text{ V} + (46.88 \angle -36.87^\circ \text{ A})(1.12 + j4.11 \Omega) + (46.88 \angle -36.87^\circ \text{ A})(0.10 + j0.40 \Omega)$$

$$V_{\text{source}}' = 2576 \angle 3.0^\circ \text{ V}$$

Therefore, the voltage at the power source is

$$V_{\text{source}} = (2576 \angle 3.0^\circ \text{ V}) \frac{14 \text{ kV}}{2.4 \text{ kV}} = 15.5 \angle 3.0^\circ \text{ kV}$$

(b) To find the voltage regulation of the transformer, we must find the voltage at the primary side of the transformer (referred to the secondary side) under these conditions:

$$V_P' = V_S + I_S Z_{\text{EQ}}$$

$$V_P' = 2400 \angle 0^\circ \text{ V} + (46.88 \angle -36.87^\circ \text{ A})(0.10 + j0.40 \Omega) = 2415 \angle 0.3^\circ \text{ V}$$

There is a voltage drop of 15 V under these load conditions. Therefore the voltage regulation of the transformer is

$$\text{VR} = \frac{2415 - 2400}{2400} \times 100\% = 0.63\%$$

(c) The overall efficiency of the power system will be the ratio of the output power to the input power. The output power supplied to the load is $P_{\text{OUT}} = 90 \text{ kW}$. The input power supplied by the source is

$$P_{\text{IN}} = P_{\text{OUT}} + P_{\text{LOSS}} = P_{\text{OUT}} + I^2 R = (90 \text{ kW}) + (46.88 \text{ A})^2 (1.22 \Omega) = 92.68 \text{ kW}$$

$$P_{\text{IN}} = V_{\text{source}}' I_S \cos \theta = (2415 \text{ V})(46.88 \text{ A}) \cos 36.57^\circ = 90.93 \text{ kW}$$

Therefore, the efficiency of the power system is

$$\eta = \frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100\% = \frac{90 \text{ kW}}{92.68 \text{ kW}} \times 100\% = 97.1\%$$

Extra Problems:

Q3) A 2.2-kVA, 440/220-V, step down transformer has the following equivalent parameters as referred to the primary side:

$$\begin{aligned} R_{eqp} &= 3\text{-}\Omega, & R_{cp} &= 2.5\text{-k}\Omega \\ X_{eqp} &= 4\text{-}\Omega, & X_{mp} &= 2\text{-k}\Omega \end{aligned}$$

The transformer is operating at full load with a power factor of 0.707 lagging. Determine the efficiency and the voltage regulation of the transformer

Solution:

For lagging power of 0.707

$$\theta = -45^\circ$$

Secondary current referred to primary

$$I'_s = \frac{I_s}{a} = \frac{2200 \text{ kVA} / 220 \text{ V}}{440 \text{ V} / 220 \text{ V}} = 5 \angle -45^\circ \text{ A}$$

Secondary voltage referred to primary

$$V'_s = aV_s = 2 \times 220 \text{ V} = 440 \angle 0^\circ \text{ V}$$

Thus,

$$\begin{aligned} V_p &= V'_s + I'_s (R_{eqp} + jX_{eqp}) = 440 + (5 \angle -45^\circ)(3 + j4) \\ &= 464.76 \angle 0.44^\circ \text{ V} \end{aligned}$$

The core-loss and magnetizing currents are,

$$I_{cp} = \frac{464.76 \angle 0.44^\circ \text{ V}}{2500} = 0.186 \angle 0.44^\circ \text{ A}$$

$$I_{mp} = \frac{464.76 \angle 0.44^\circ \text{ V}}{j 2000} = 0.232 \angle -89.56^\circ \text{ A}$$

Total primary current,

$$\begin{aligned} I_p &= I_s' + I_{cp} + I_{mp} = 5\angle -45^\circ + 0.186\angle 0.44^\circ + 0.232\angle -89.56^\circ \\ &= 5.296\angle -45.33^\circ \text{ A} \end{aligned}$$

The output power, input power and the efficiency are,

$$P_o = \text{Re}[(440)(5\angle -45^\circ)] = 1555.63 \text{ W}$$

$$P_{in} = \text{Re}[(464.72\angle 0.44^\circ)(5.296\angle -45.33^\circ)] = 1716.91 \text{ W}$$

$$\eta = \frac{1555.63}{1716.91} \times 100 = 90.6 \%$$

The voltage regulation is,

$$VR = \frac{464.76 - 440}{440} \times 100 = 5.63 \%$$

Q4) A 120-kVA, 2400/240-V, step down transformer has the following parameters:

$$\begin{aligned} R_1 &= 0.75\text{-}\Omega, & R_2 &= 0.01\text{-}\Omega \\ X_1 &= 0.8\text{-}\Omega, & X_2 &= 0.02\ \Omega \end{aligned}$$

The transformer is designed to operate at maximum efficiency at 70% of its rated load with 0.8 power factor lagging. Determine:

- the kVA rating of the transformer, copper loss and core loss at maximum efficiency
- the maximum efficiency
- the efficiency at full load and 0.8 power factor is lagging and the equivalent core-loss resistance

Solution:

The rated load current

$$I_{s_rated} = \frac{kVA_{rated}}{V_{s_rated}} = \frac{120\ kVA}{240\ V} = 500\ A$$

The load current at maximum efficiency

$$I_{s\eta} = 0.7 \times I_{s_rated} = 0.7 \times 500 = 350\ A$$

- The kVA rating of the transformer at maximum efficiency:

$$kVA \Big|_{\max\text{-eff}} = I_{s\eta} \times V_{s_rated} = 350\ A \times 240\ V = 84\ kVA$$

the copper loss at maximum efficiency:

$$P_{Cu\eta} = I_{s\eta}^2 \left(\frac{R_1}{a^2} + R_2 \right) = 350^2 \left(\frac{0.75}{10^2} + 0.01 \right) = 2.14\ kW$$

the core loss at maximum efficiency:

$$P_{core\eta} = P_{Cu\eta} = 2.14\ kW$$

b) The output power, input power and efficiency when the transformer delivers load at maximum efficiency:

$$P_o = V_{s_rated} \times I_{s\eta} \times PF = 240 \text{ V} \times 350 \text{ A} \times 0.8 = 67.2 \text{ kW}$$

$$P_{in} = P_o + P_{core\eta} + P_{Cu\eta} = 67.2 + 2.14 + 2.14 = 71.48 \text{ kW}$$

$$\eta = \frac{P_o}{P_{in}} \times 100 = \frac{67.2}{71.48} \times 100 = 94 \%$$

c) The output power, input power and efficiency at full load:

$$P_o = V_{s_rated} \times I_{s_rated} \times PF = 240 \text{ V} \times 500 \text{ A} \times 0.8 = 96 \text{ kW}$$

$$P_{Cu} = I_{s_rated}^2 \left(\frac{R_1}{a^2} + R_2 \right) = 500^2 \left(\frac{0.75}{10^2} + 0.01 \right) = 4.375 \text{ kW}$$

$$\eta = \frac{P_o}{P_o + P_{Cu} + P_{core}} \times 100 = \frac{96}{96 + 4.375 + 2.14} \times 100 = 93.64 \%$$

d) The equivalent core loss resistance at no load is:

$$R_C = \frac{V_p^2}{P_{core}} = \frac{2400^2 \text{ V}}{2.14 \text{ kW}} = 2691 \ \Omega$$