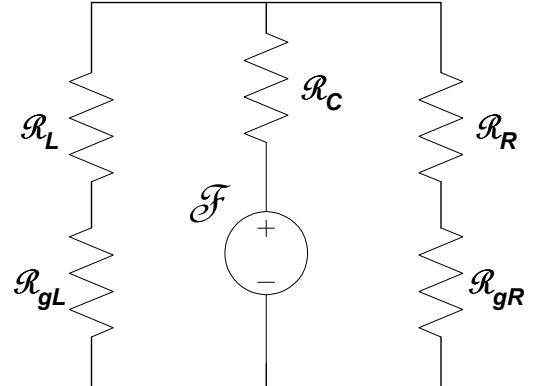


King Fahd University of Petroleum & Minerals
 Electrical Engineering Department

EE-360 Problem Session Solution #1, 2014, 132

Solution 1:

$$\mathcal{R}_{tot} = \mathcal{R}_c + \frac{(\mathcal{R}_L + \mathcal{R}_{gL})(\mathcal{R}_R + \mathcal{R}_{gR})}{\mathcal{R}_L + \mathcal{R}_{gL} + \mathcal{R}_R + \mathcal{R}_{gR}}$$



$$\mathcal{R}_L = \frac{l_L}{\mu A_L} = \frac{l_L}{\mu_0 \mu_r A_L} = \frac{1.2m}{2000 \times 4\pi 10^{-7} (0.07m)(0.1m)} = 68.2 kA \cdot t / wb$$

$$\mathcal{R}_{gL} = \frac{l_{gL}}{\mu A_{gL}} = \frac{l_{gL}}{\mu_0 A_{gL}} = \frac{0.0005m}{4\pi 10^{-7} (0.07m)(0.1m)(1.05)} = 54.1 kA \cdot t / wb$$

$$\mathcal{R}_R = \frac{l_R}{\mu A_R} = \frac{l_R}{\mu_0 \mu_r A_R} = \frac{1.2m}{2000 \times 4\pi 10^{-7} (0.07m)(0.1m)} = 68.2 kA \cdot t / wb$$

$$\mathcal{R}_{gR} = \frac{l_{gR}}{\mu A_{gR}} = \frac{l_{gR}}{\mu_0 A_{gR}} = \frac{0.0007m}{4\pi 10^{-7} (0.07m)(0.1m)(1.05)} = 75.8 kA \cdot t / wb$$

$$\mathcal{R}_c = \frac{l_c}{\mu A_c} = \frac{l_c}{\mu_0 \mu_r A_c} = \frac{0.4m}{2000 \times 4\pi 10^{-7} (0.07m)(0.1m)} = 22.7 kA \cdot t / wb$$

$$\mathcal{R}_{tot} = 22.7 + \frac{(68.2 + 54.1)(68.2 + 75.8)}{68.2 + 54.1 + 68.2 + 75.8} = 88.8 kA \cdot t / wb$$

$$\phi_{total} = \phi_c = \frac{\mathcal{F}}{\mathcal{R}_{tot}} = \frac{Ni}{\mathcal{R}_{tot}} = \frac{300t \times 1A}{88.8kA \cdot t / wb} = 0.0034 \text{ wb}$$

$$\phi_L = \phi_{tot} \times \frac{\mathcal{R}_R + \mathcal{R}_{gR}}{\mathcal{R}_L + \mathcal{R}_{gL} + \mathcal{R}_R + \mathcal{R}_{gR}} = 0.0018 \text{ wb}$$

$$\phi_R = \phi_{tot} \times \frac{\mathcal{R}_L + \mathcal{R}_{gL}}{\mathcal{R}_L + \mathcal{R}_{gL} + \mathcal{R}_R + \mathcal{R}_{gR}} = 0.0016 \text{ wb}$$

$$B_{gL} = \frac{\phi_L}{A_{gL}} = \frac{0.0018}{0.07 \times 0.1 \times 1.05} = 0.245 \text{ T}$$

$$B_{gR} = \frac{\phi_R}{A_{gR}} = \frac{0.0016}{0.07 \times 0.1 \times 1.05} = 0.22 \text{ T}$$

Solution 2:


$$\phi_c = 0.02 \text{ wb}$$

$$N = 1200 \text{ t}$$

$$A = 200 \text{ cm}^2$$

$$B_C = B_g = \frac{\phi_c}{A} = \frac{0.02 \text{ wb}}{200 \times 10^{-4} \text{ mm}^2} = 1 \text{ T}$$
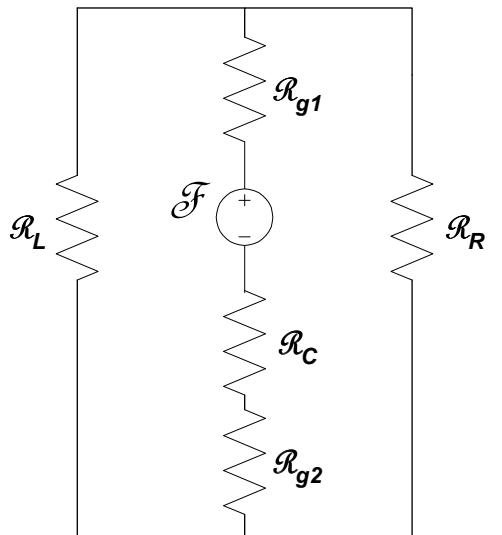
$$B_L = B_R = \frac{\phi_c / 2}{A} = \frac{0.01 \text{ wb}}{200 \times 10^{-4} \text{ mm}^2} = 0.5 \text{ T}$$



Using the cast steel curve to find H from the values of B above:

$$H_C = 800 \text{ } A \cdot t / m$$

$$H_L = H_R = 280 \text{ } A \cdot t / m$$

$$H_g = \frac{B_g}{\mu_0} = \frac{1 \text{ T}}{4\pi \times 10^{-7}} = 795.77 \times 10^3 \text{ } A \cdot t / m$$

$$\mathcal{F}_{g_1} = \mathcal{F}_{g_2} = H_g l_g = 795.77 \times 10^3 \times 0.001 = 795.77 \text{ } A \cdot t$$


$$\mathcal{F}_C = H_C l_C = 800 \times 0.1 = 80 \text{ } A \cdot t$$

$$\mathcal{F}_L = \mathcal{F}_R = H_L l_L = 280 \times 0.2 = 56 \text{ } A \cdot t$$

$$\mathcal{F}_{tot} = 2 \times \mathcal{F}_g + \mathcal{F}_C + \mathcal{F}_L = 1727.54 \text{ } A \cdot t$$

$$I = \frac{\mathcal{F}_{tot}}{N} = \frac{1727.54 \text{ } A \cdot t}{1200 \text{ } t} = 1.44 \text{ } A$$

Solution 3:

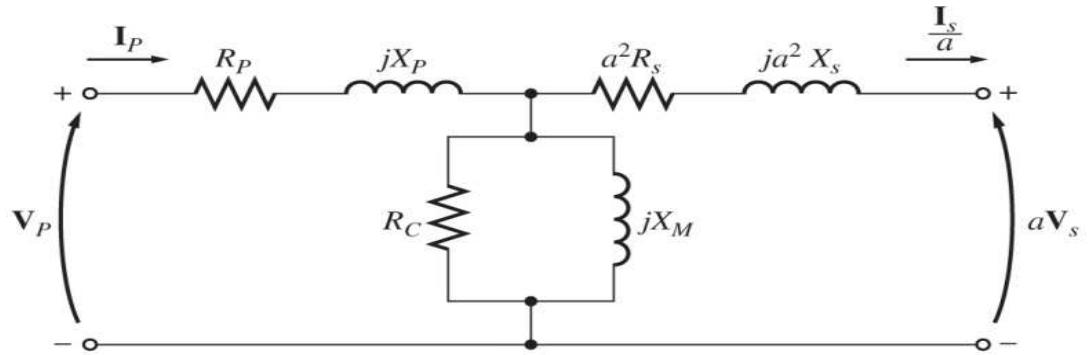

$$I_s = \frac{S}{V_s} = \frac{150 \text{ kVA}}{240 \text{ V}} = 625 \angle -36.8^\circ \text{ A}$$

$$\frac{I_s}{a} = \frac{625 \angle -36.8^\circ \text{ A}}{10} = 62.5 \angle -36.8^\circ \text{ A} = 50 - j 37.5 \text{ A}$$

$$aV_s = 2400 \angle 0^\circ \text{ V} = 2400 + j 0 \text{ V}$$

$$a^2R_2 = 0.2 \Omega \text{ and } a^2X_2 = 0.45 \Omega$$

Therefore,

$$\begin{aligned} E_1 &= (2400 + j 0 \text{ V}) + (50 - j 37.5 \text{ A})(0.2 + j 0.45) \\ &= 2427 + j 15 = 2427 \angle 0.35^\circ \text{ V} \end{aligned}$$

$$I_m = \frac{E_1}{X_m} = \frac{2427 \angle 0.35^\circ}{1550 \angle 90^\circ} = 1.56 \angle -89.65^\circ = 0.0095 - j 1.56 \text{ A}$$

$$I_c = \frac{E_1}{R_c} = \frac{2427 \angle 0.35^\circ}{10000} = 0.2427 - j 0 \text{ A}$$

$$I_o = I_m + I_c = 0.25 - j 1.56 \text{ A}$$

$$I_p = I_o + \frac{I_s}{a} = 50.25 - j 39.06 = 63.65 \angle -37.850^\circ \text{ A}$$

Therefore, the primary voltage is

$$\begin{aligned}
 V_P &= E_1 + I_P \times (R_1 + jX_1) \\
 &= (2427 + j15) + (50.25 - j39.06)(0.2 + j0.45) \\
 &= 2455 + J30 = 2455\angle0.7^\circ \text{ V}
 \end{aligned}$$

$$VR = \frac{V_P / a - V_{S,fL}}{V_{S,fL}} \times 100\% = \frac{2455 / 10 - 240}{240} \times 100\% = 2.3\%$$

$$P_i = I_c^2 R_c = 0.2427^2 \times 10000 = 589 \text{ W}$$

$$P_{cu} = I_P^2 R_1 + I_S^2 R_2 = 63.65^2 \times 0.2 + 62.5^2 \times 0.2 = 1592 \text{ W}$$

$$P_{loss} = P_i + P_{cu} = 589 + 1592 = 2181 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\% = \frac{150kVA \times 0.8}{150kVA \times 0.8 + 2.181kW} \times 100\% = 98.2\%$$

Solution 4:

(a) From O/C test result:

$$\begin{aligned}
 R_{cs} &= \frac{V_{o/c}^2}{P_{o/c}} = \frac{120^2}{80} = 180 \Omega \\
 R_{cp} &= a^2 R_c = (450 / 120)^2 \times 180 \Omega = 2530 \Omega
 \end{aligned}$$

$$I_{cs} = \frac{V_{o/c}}{R_c} = \frac{120 \text{ V}}{180 \Omega} = 0.667 \text{ A}$$

$$I_{ms} = \sqrt{I_o^2 - I_{cs}^2} = \sqrt{4.2^2 - 0.667^2} = 4.15 \text{ A}$$

$$X_{ms} = \frac{V_{o/c}}{I_m} = \frac{120}{4.15} = 28.92 \Omega$$

$$X_{mp} = a^2 X_m = (450/120)^2 \times 28.92 \Omega = 406.7 \Omega$$

From S/C test result:

$$Z_{eq} = \frac{V_{s/c}}{I_{s/c}} = \frac{9.65 \text{ V}}{22.2 \text{ A}} = 0.435 \Omega$$

$$R_{eq} = \frac{P_{s/c}}{I_{s/c}^2} = \frac{120 \text{ W}}{22.2^2 \text{ A}} = 0.243 \Omega$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2} = \sqrt{0.435^2 - 0.243^2} = 0.361 \Omega$$

$$\theta_{sc} = \tan^{-1} \left(\frac{X_{eq}}{R_{eq}} \right) = \tan^{-1} \left(\frac{0.361}{0.234} \right) = 57^\circ$$

(b) At full load:

$$I_{S_FL} = \frac{S}{V_{S_rated}} = \frac{10 \text{ kVA}}{120 \text{ V}} = 83.33 \text{ A}$$

At power factor PF = 0.8 leading,

$$I_S = 83.33 \angle 36.9^\circ \text{ A}$$

$$\begin{aligned}
\frac{V_p}{a} &= V_s + I_s \times (R_{eq} + jX_{eq}) \\
&= 120\angle 0^\circ + (83.33\angle 36.9^\circ)(0.243) + (83.33\angle 36.9^\circ)(j 0.361) \\
&= 120 + 20.25\angle 36.9^\circ + 30.08\angle 126.9^\circ \\
&= 120 + 16.2 + j 12.16 - 18.06 + j 24.05 \\
&= 118.14 + j 36.21 = 123.56\angle 17^\circ \text{ V}
\end{aligned}$$

$$VR = \frac{V_p/a - V_{s,fL}}{V_{s,fL}} \times 100\% = \frac{123.56 - 120}{120} \times 100\% = 2.96\%$$

(C) Efficiency at half load:

$$\begin{aligned}
P_{core} &= \frac{(V_p/a)^2}{R_{cs}} = \frac{123.56^2}{180} = 84.8 \text{ W} \\
P_{cu} &= (0.5I_s)^2 R_{eq} = 41.66^2 \times 0.243 = 421.84 \text{ W}
\end{aligned}$$

$$\begin{aligned}
\eta &= \frac{0.5P_{out}}{0.5P_{out} + P_{core} + 0.5P_{cu}} \times 100\% \\
&= \frac{0.5 \times 10kVA \times 0.8}{0.5 \times 10kVA \times 0.8 + 84.8 + 421.84} \times 100\% = 88.75\%
\end{aligned}$$