

King Fahd University of Petroleum & Minerals
Electrical Engineering Department

EE-360 Problem Session # 2, 2014, 132

Problem 1:

A 24-kVA, 60-Hz, 2400/240-V distribution transformer is to be reconnected for use as an autotransformer. Determine the following for step-up and step-down connections:

- a) The primary winding voltage
- b) The secondary winding voltage
- c) The ratio of transformation
- d) The nominal rating of the autotransformer

Problem 2:

A 150-kVA wye-delta connected step down transformer has an input line-voltage of 4160-V and an output line voltage of 240-V

- a) Draw the winding arrangements and its equivalent wye-wye representation
- b) Determine the transformer ratio
- c) Determine the rated line and phase currents for the high side
- d) Determine the rated line and phase currents for the low side

Problem 3:

A 20 hp, 240 V shunt DC motor has an armature resistance of 0.1 Ω . The motor's field resistance is 240 Ω . At no load, the motor draws 5 A from the source and produces a no-load speed of 1800 rpm. When delivering the rated horse power, the motor draws 69.1 A from the source.

- a) Calculate the motor speed regulation.
- b) Calculate the converted power and the corresponding induced torque.
- c) Find the rotational losses and the motor efficiency

Problem 4:

A 25-kVA, 230-V, three-phase, 60-Hz, four-pole, Y-connected synchronous generator has a synchronous reactance of 1.5 Ω per phase and negligible armature resistance

- a) Draw the single phase equivalent circuit and determine the synchronous speed
- b) Find the excitation voltage (E_A) and the power angle (δ) if the generator is delivering rated kVA at 0.8 PF lagging
- c) The field current is increased by 20 % without changing the input power from the prime mover. Find the armature current, the power factor, and the reactive power supplied by the machine