

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-360

Key Solutions


Quize # 6 Serial #

Name:

I.D.#

Circle the correct answer.

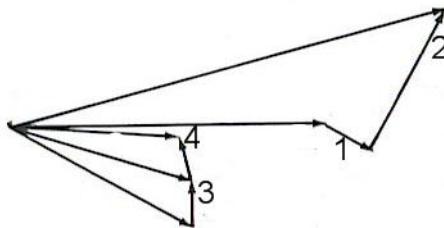- 1) In the phasor diagram of a Pi-nominal transmission line shown below, number "1" must be (....), number "2" must be (....), number "3" must be (....), and number "4" must be (....).



- a) $R^*I_R ; j X_L^*I_R ; I_C ; I_S$
- b) $R^*I_R ; j X_L(I_R + I_{CR}) ; I_{CR} ; I_{CS}$.**
- c) $0.5^*R^*I_R ; j 0.5^*X_L(I_R + I_{CR}) ; I_{CR} ; I_{CS}$.
- d) $0.5^*R^*I_R ; j 0.5^*X_L^*I_R ; I_C ; I_S$.

- 2) A 60 Hz, 3-phase, transmission line is 40 miles long with a total series impedance of $(35 + j 140)$ Ohm. It delivers 40 MW at 220 kV and 0.9 power factor lagging. The line voltage at the sending end is

- a. $239.7 \angle 5.4^\circ$ kV.
- b. $239.7 \angle 35.4^\circ$ kV.**
- c. $231. \angle 3.2^\circ$ kV.
- d. $231. \angle 33.2^\circ$ kV.