

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim Omar Habiballah

EE-306

Key Solutions

Quiz 1

Sec.: 2

I.D.:

Name:

Q.1 Three identical impedances of $4 + j3$ Ohm are delta-connected and tied to a three-phase 208-V power line. The phase and line currents absorbed by the load are

- a. $I_{ph} = 41.6 \angle -36.87^\circ \text{ A}$; $I_{Line} = 72.05 \angle -66.87^\circ \text{ A}$
- b. $I_{ph} = 24.02 \angle -36.87^\circ \text{ A}$; $I_{Line} = 24.02 \angle -36.87^\circ \text{ A}$
- c. $I_{ph} = 41.6 \angle -36.87^\circ \text{ A}$; $I_{Line} = 72.05 \angle -6.87^\circ \text{ A}$
- d. $I_{ph} = 24.06 \angle -36.87^\circ \text{ A}$; $I_{Line} = 41.6 \angle -6.87^\circ \text{ A}$

Q.2 Three identical impedances of $4 + j3$ Ohm are Y-connected and tied to a three-phase 208-V power line. The phase and line currents absorbed by the load are

- a. $I_{ph} = 41.6 \angle -36.87^\circ \text{ A}$; $I_{Line} = 72.05 \angle -66.87^\circ \text{ A}$
- b. $I_{ph} = 24.02 \angle -36.87^\circ \text{ A}$; $I_{Line} = 24.02 \angle -36.87^\circ \text{ A}$
- c. $I_{ph} = 41.6 \angle -36.87^\circ \text{ A}$; $I_{Line} = 72.05 \angle -6.87^\circ \text{ A}$
- d. $I_{ph} = 24.06 \angle -36.87^\circ \text{ A}$; $I_{Line} = 41.6 \angle -6.87^\circ \text{ A}$