

EE306

Problem session # 2

Solution

2014/2015

141

P1)

$$I_2 = \frac{150 \times 10^3}{240} = 625 \text{ A}$$

$$\frac{I_2}{a} = 62.5 \angle -36.8^\circ = 50 - j37.5 \text{ A}$$

$$aV_2 = 2400 \angle 0^\circ = 2400 + j0 \text{ V}$$

$$a^2R_2 = 0.2 \Omega \quad \text{and} \quad a^2X_2 = 0.45 \Omega$$

Hence

$$E_1 = (2400 + j0) + (50 - j37.5)(0.2 + j0.45) \\ = 2427 + j15 = 2427 \angle 0.35^\circ \text{ V}$$

$$I_m = \frac{2427 \angle 0.35^\circ}{1550 \angle 90^\circ} = 1.56 \angle -89.65 = 0.0095 - j1.56 \text{ A}$$

$$I_c = \frac{2427 + j15}{10,000} \approx 0.2427 + j0 \text{ A}$$

$$I_0 = I_c + I_m = 0.25 - j1.56 \text{ A}$$

$$I_1 = I_0 + \frac{I_2}{a} = 50.25 - j39.06 = 63.65 \angle -37.850^\circ \text{ A}$$

Thus, the primary voltage is

$$V_1 = (2427 + j15) + (50.25 - j39.06)(0.2 + j0.45) \\ = 2455 + j30 = 2455 \angle 0.7^\circ \text{ V}$$

$$\text{VR} = \frac{2455 - 2400}{2400} * 100 = 2.3\%$$

$$P_i = I_c^2 R_c, \quad P_{Cu} = I_1^2 R_1 + I_2^2 R_2$$

$$P_i + P_{Cu} = 2.18 \text{ kW}, \quad P_o/P = 150 * 0.8 = 120 \text{ kW}$$

$$\gamma = \frac{120}{120 + 2.18} * 100 = 98.2\%$$

P2

$$\frac{O.C}{R_C} = \frac{(120)^2}{80} = 180 \Omega , a = \frac{450}{120} = 3.75$$

$$R_C = a^2 R_C = \underline{\underline{2530 \Omega}}$$

$$I_C' = \frac{120}{R_C} = 0.667 A \quad I_m' = \sqrt{I_0^2 - I_C'} = 4.15 A$$

$$X_m' = \frac{120}{I_m'} = 28.94 \Omega$$

$$X_m = a^2 X_m' = \underline{\underline{407}} \Omega$$

$$\underline{S.C} \quad Z_{e_1} = \frac{9.65}{22.2} = 0.435 \Omega$$

$$R_{e_1} = \frac{120}{(22.2)^2} = \underline{\underline{0.243 \Omega}}$$

$$X_{e_1} = \sqrt{Z_{e_1}^2 - R_{e_1}^2} = \underline{\underline{0.361 \Omega}}$$

$$I_{IFL} = \frac{10000}{450} = 22.2 A$$

$$\text{Voltage Drop} \approx I_1 (R_{e_1} \cos \phi + X_{e_1} \sin \phi) \approx 9.2 V$$

$$VR = \frac{9.2}{450} * 100 = 2.04 \%$$

$$\gamma_{FL} = \frac{10000 * 0.8}{10000 * 0.8 + 80 + 120} * 100 = 97.57 \%$$

at half load

$$\gamma = \frac{\frac{1}{2} * 10000 * 0.8}{\frac{1}{2} * 10000 * 0.8 + 80 + (\frac{1}{2})^2 * 120} * 100 = 97.34 \%$$

$$\textcircled{a} \quad I_t = \frac{P_{\text{load}}}{V_t} = \frac{10,000}{250} = 40 \text{ A}$$

$$I_f = \frac{V_t}{R_f} = \frac{250}{12.5} = 2 \text{ A}$$

$$I_a = I_t + I_f = 40 + 2 = 42 \text{ A}$$

$$E_a = V_t + R_a I_a = 250 + (0.2)(42) = 258.4 \text{ V}$$

$$\textcircled{b} \quad \omega_m = \frac{2\pi n}{60} = \frac{2\pi(1750)}{60} = 183.26 \text{ rad/sec}$$

$$P_{\text{loss}} = E_a I_a = (258.4)(42) = 10,852.8 \text{ W}$$

$$T_e = \frac{P_{\text{load}}}{\omega_m} = \frac{10,000}{183.26} = 54.2 \text{ N-m}$$

$$\textcircled{c} \quad VR = \frac{E_a - V_t}{V_t} \times 100 = \frac{258.4 - 250}{250} \times 100 = 3.36\%$$

$$\textcircled{d} \quad P_m = I_a^2 R_a + \sum_f R_f = (42)^2(0.2) + (2)^2(12) = 852.8 \text{ W}$$

$$P_{\text{out}} = 10,000 \text{ W}$$

$$P_{\text{in}} = P_{\text{out}} + P_{\text{loss}} + P_{\text{rotational}} = 10,000 + 852.8 + 450 = 11,303.8 \text{ W}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{10,000}{11,303.8} / 100 \% = 88.5 \%$$

P4

 The no load Saturation curve for a speed of 1500 rpm

a) $\frac{E_1}{E} = \frac{K_a \phi_{P_1} w_{m_1}}{K_a \phi_P w_m} \Rightarrow E = E_1 \frac{w_m}{w_{m_1}}$

$E = E_1 \frac{1500}{1800}$ (for a given field current the speed affects E proportionally $E \propto \text{Speed}$)

| | | | | | | | | | | | |
|-----|-------|------|-------|-------|-------|-------|-------|-----|-------|-------|-------|
| (V) | E | 6.67 | 33.33 | 61.67 | 94.17 | 126.7 | 177.5 | 195 | 206.7 | 221.7 | 231.7 |
| (A) | I_f | 0 | 0.5 | 1.0 | 1.5 | 2.0 | 3.0 | 3.5 | 4.0 | 5.0 | 6.0 |

Both Plots are attached


b) when $I_f = 4.6 A$, $E = 215 V$ at 1500 rpm.
taken from the graph

$$E \text{ at } 1000 \text{ rpm is } 215 \times \frac{1000 \text{ rpm}}{1500} = 143.33 \checkmark$$

c) For a given field current, $E = 120 V$ at 900 rpm,
this is equivalent to $E = 120 \times \frac{1500}{900} = 200 V$ at
1500 rpm. From the graph the corresponding
field current is 3.75 Amp.

OCC

Series1
Series2

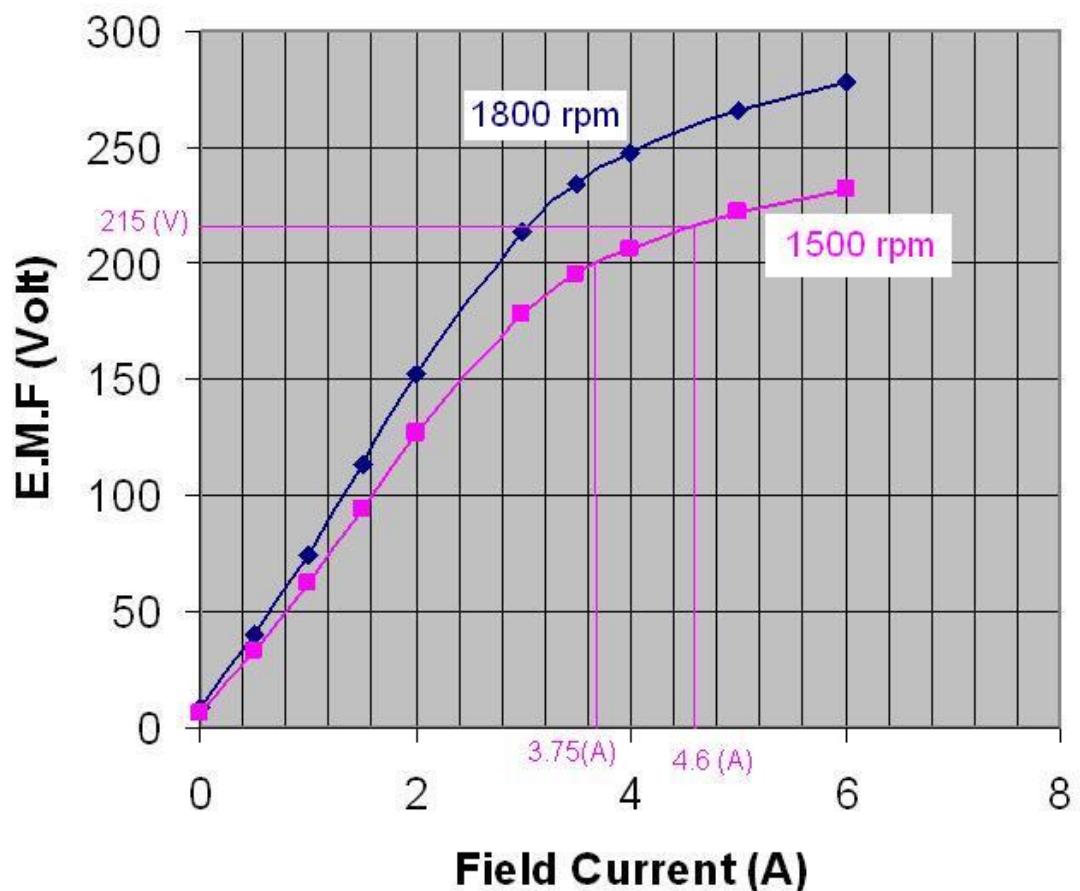

P5:

$$\textcircled{a} \quad I_f = \frac{V_t}{R_f} = \frac{220}{110} = 2 A$$

$$I_{a,NL} = I_{t,NL} - I_f = 5 - 2 = 3 A$$

$$E_{a,NL} = V_t - R_a I_{a,NL} = 220 - (0.15)(3) = 219.55 V$$

$$I_{t,L} = \frac{P}{V_t} = \frac{12,000}{220} = 54.54 A$$

$$I_{a,L} = 54.54 - 2 = 52.54 A$$

$$E_{a,L} = 220 - (0.15)(52.54) = 211.82 V$$

$$\frac{E_{a,L}}{E_{a,NL}} = \frac{k_a \phi w_{m,L}}{k_a \phi w_{a,NL}} = \frac{k_a \phi (2\pi n_L / 60)}{k_a \phi (2\pi n_{NL} / 60)} = \frac{n_L}{n_{NL}}$$

$$n_L = \left(\frac{E_{a,L}}{E_{a,NL}} \right) n_{NL} = \left(\frac{211.82}{219.55} \right) (1200) = 1158 \text{ rpm}$$

$$\textcircled{b} \quad P_{dew,L} = E_{a,L} I_{a,L} = (211.82)(52.54) = 11,129 W$$

$$w_{m,L} = \frac{2\pi n_L}{60} = \frac{2\pi (1158)}{60} = 121.26 \text{ rad/sec}$$

$$T_e = \frac{P_{dew}}{w_{m,L}} = \frac{11,129}{121.26} = 91.8 N\cdot m$$

$$\textcircled{c} \quad P_{rotational} = P_{dew,NL} = E_{a,NL} I_{a,NL} = (219.55)(3) = 658.65 W$$

$$P_{out,L} = P_{dew,L} - P_{rotational} = E_{a,L} I_{a,L} - P_{rotational}$$

$$= (211.82)(52.54) - 658.65 = 10,470 W$$

$$\eta = \frac{P_{out,L}}{P_{in}} = \frac{10,470}{12,000} 100\% = 87.25\%$$

P6:

$$\textcircled{a} \quad E_a = V_t - (R_a + R_z) I_a = 230 - (0.25 + 0.10)(40) = 216 \text{ V}$$

$$P_{deu} = E_a I_a = (216)(40) = 8640 \text{ W}$$

$$\omega_m = \frac{2\pi n}{60} = \frac{2\pi(1200)}{60} = 125.66 \text{ rad/sec}$$

$$T_e = \frac{P_{deu}}{\omega_m} = \frac{8640}{125.66} = 68.8 \text{ N-m}$$

$$\textcircled{b} \quad E'_a = 230 - (0.25 + 0.10)(20) = 223 \text{ V}$$

$$\frac{E'_a}{E_a} = \frac{K_a \phi' \omega_m'}{K_a \phi \omega_m} = \frac{K'_a I'_a (2\pi n'/60)}{K_a I_a (2\pi n/60)} = \frac{I'_a n'}{I_a n}$$

$$n' = \left(\frac{E'_a}{E_a}\right) \left(\frac{I_a}{I'_a}\right) n = \left(\frac{223}{216}\right) \left(\frac{40}{20}\right) (1200) = 2478 \text{ rpm} \left(\frac{2\pi}{60}\right) = 259.5 \text{ rad/s}$$

$$P'_{deu} = E'_a I'_a = (223)(20) = 4460 \text{ W}$$

$$T'_e = \frac{P'_{deu}}{\omega_m} = \frac{4460}{259.5} = 17.2 \text{ N-m}$$