

**Q1) Textbook Problem 2.2**

**Q2) Textbook Problem 2.11**

**Q3) Textbook Problem 2.13**

**Q4) Textbook Problem 2.20**

**Q5) Textbook Problem 2.27**

**Q6)** A 3-phase  $\Delta/Y$  transformer is assembled by connecting three 830-VA, 240/120-V single phase transformers. Each transformer parameters are as follow:

$$R_P = 15.5 \Omega, X_P = 18.2 \Omega, R_{CP} = 6.54 \text{ k}\Omega, X_{MP} = 4.64 \text{ k}\Omega$$
$$R_S = 2.4 \Omega, X_S = 2.8 \Omega$$

- a) Determine the 3-phase transformer bank's ratings (voltages and power).
- b) Draw the winding arrangements, equivalent Y/Y connections, and per-phase equivalent circuit.