

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**  
**ELECTRICAL ENGINEERING DEPARTMENT**

**Dr. Ibrahim O. Habiballah**  
**EE-360 (142)**

**Key Solution**


Quiz # 2    Sec. 1 – 2 – 3    Serial #    Name:    I.D.#

**Circle the correct answer.**

1) A 12 kVA, 4800/240 V, transformer has an equivalent impedance referred to the primary side as  $Z_{eqp} = 120 + j300\Omega$ . If the secondary side of the transformer supplies a resistive load at rated current, the primary current will be (4 Marks)

- a- 50 A.
- b-  $2.5\sqrt{3}$  A.
- c- 2.5 A.**
- d-  $2.5/\sqrt{3}$  A.

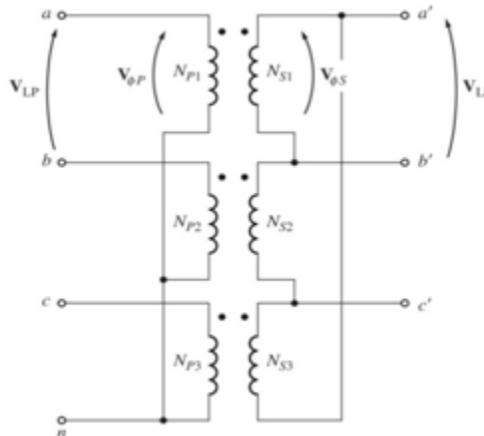2) The ratings of the 3-phase transformer shown below are 69 kV (on primary) / 4.16 kV (on secondary), 1000 kVA. (3 Marks)



The rated phase voltage on the primary side is (.....) kV, and the rated phase voltage on the secondary side is (.....) kV

- a- 69 ; 2.4
- b- 69 ; 4.16
- c- 39.84 ; 2.4
- d- 39.84 ; 4.16**

3) A 10 kVA, 480/120 V transformer is connected as a step-down autotransformer feeding a load at 480 V. The amount of kVA transferred by conduction is (3 Marks)

- a- 4
- b- 5
- c- 10
- d- 40**