

①

Problem-1:-

Given :- 25 kVA 1-phase transformer

$$\alpha = \frac{2400}{240} = 10$$

Measurement of open-circuit test are taken at the Secondary side.

$$V_{ocs} = 240V \quad I_{ocs} = 3.2A \quad P_{ocs} = 165W$$

$$PF = \frac{P_{ocs}}{V_{ocs} I_{ocs}} = \frac{165}{240 \times 3.2} = 0.2148$$

$$\Rightarrow \theta_{oc} = \cos^{-1}(0.2148) = 77.59^\circ$$

Shunt excitation admittance

$$|Y_{ocs}| = \frac{I_{ocs}}{V_{ocs}}$$

$$= \frac{3.2}{240} = 0.01333 \text{ S}$$

$$\therefore Y_{ocs} = 0.01333 \angle -77.59^\circ \text{ S}$$

$$\Rightarrow Y_{ocs} = 0.002865 - j0.0130021$$

$$\Rightarrow R_{cs} = \frac{1}{0.002865} = 349.65 \Omega$$

$$X_{ms} = \frac{1}{-j0.0130021} = 76.796 \Omega$$

(2)

The excitation elements are now referred to the primary side as

$$R_{cp} = a^2 R_{cs} = (10)^2 (349.65) = 3496.5 \text{ k}\Omega$$

$$X_{mp} = a^2 X_{ms} = (10)^2 (76.796) = 767.96 \text{ k}\Omega$$

The measurement of short-circuit test are taken on the primary side.

$$P_{SCP} = 375 \text{ W} \quad V_{SCP} = 55 \text{ V} \quad I_{SCP} = 10.4 \text{ A}$$

Compute I_p^{rated}

$$I_{\text{rated}} = \frac{S_{\text{rated}}}{V_p} = \frac{25 \times 10^3}{2400} = 10.4 \text{ A}$$

Hence the short-circuit test is carried on full-load primary current.

$$\text{Now } PF = \frac{P_{SCP}}{V_{SCP} \cdot I_{SCP}} = \frac{375}{55 \times 10.4} = 0.65559$$


$$\Rightarrow \theta = \cos^{-1}(0.65559) = 49.035^\circ$$

$$Z_{SCP} = \frac{V_{SCP} \angle \theta}{I_{SCP}} = \frac{55 \angle 49.035^\circ}{10.4}$$

$$Z_{SCP} = 3.467 + j3993 \Omega$$

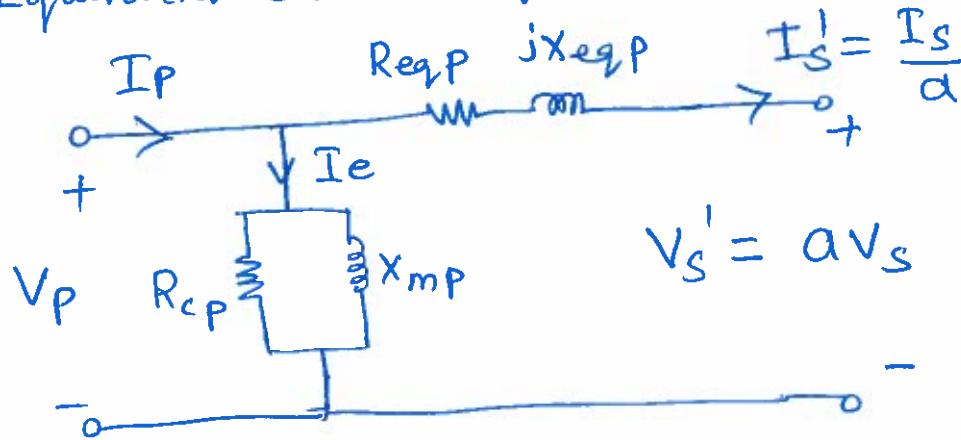(3)

Equivalent circuit referred to the primary side



(b) $\cos\theta = 0.85$ lagging

$$P_{out} = 25 \times 0.85 = 21.25 \text{ kW}$$

$$\theta_s = \cos^{-1}(0.85) = 31.788^\circ$$

$$\begin{aligned} \text{Now } I_s &= \frac{P_{out} (= P_s)}{V_s \cos \theta_s} \\ &= \frac{21.25 \times 10^3}{240 \times 0.85} \end{aligned}$$

$$I_s = 104.166 \text{ A}$$

$$\therefore \bar{I}_s = 104.166 L - 31.788^\circ \text{ A}$$

$$\text{Now, } \bar{V}_p = \bar{V}_s' + \bar{I}_s (R_{eqp} + jX_{eqp})$$

(4)

$$= aV_s + \frac{Ps}{a} (R_{eqP} + jX_{eqP})$$

$$= (10)(240\angle 0^\circ) + \frac{104.166}{10} \angle -31.788^\circ (3.467 + j3.993)$$

$$V_p = 2452.66 \angle 0.38^\circ V$$

$$\therefore V_{regulation} = \frac{|V_p| - |V_s'|}{|V_s'|} \times 100$$

$$= \frac{2452 - (10)(2400)}{(10)(2400)} \times 100$$

$$= 2.194 \%$$

Efficiency :

$$\eta = \frac{P_{out}}{P_{in}} \times 100 \%$$

$$= \frac{P_{out}}{P_{out} + P_{cu} + P_{core}} \times 100 \%$$

$$P_{core} = \frac{|V_P|^2}{R_{CP}} = \frac{(2452.66)^2}{34 \cdot 904 \times 10^3} = 172.345 \text{ W}$$

$$P_{cu} = I_s^{12} \cdot R_{eqP}$$

$$= \left(\frac{104}{10} \cdot 166 \right)^2 \cdot 3.47$$

$$P_{cu} = 376.188 \text{ W}$$

$$P_{in} = 376.188 + 172.343 + 21250$$

$$= 21798.53 \text{ W}$$

$$\eta = \frac{21250}{21798.53} \times 100$$

$$\eta = 97.48\%$$

C. condition for max. efficiency, $P_{core} = P_{cu} \Delta PF = 1$

$$P_{core} = P_{cu} = 165 \text{ W} = I_s^2 R_{effs}, \quad R_{effs} = \frac{3.467}{100} = 0.03467$$

$$I_s = \sqrt{\frac{165}{0.03467}} = 68.98 \text{ A}$$

Power output at η_{max}

$$P_{out} = V_s I_s \cos \theta_s$$
$$= 240 * 68.98 = 16.556 \text{ kW}$$


$$\eta_{max} = \frac{P_{out}}{P_{out} + 2P_c} = \left(\frac{16.556 \text{ kW}}{16.556 \text{ kW} + 2(165)} \right) * 100\%$$

$$= 98.04 \%$$


(1)

Problem-2 :-

Single-phase distribution system

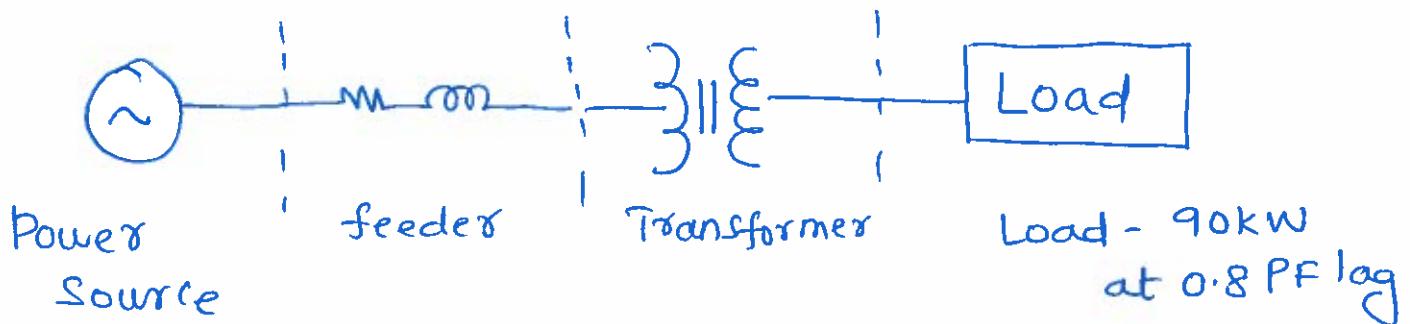

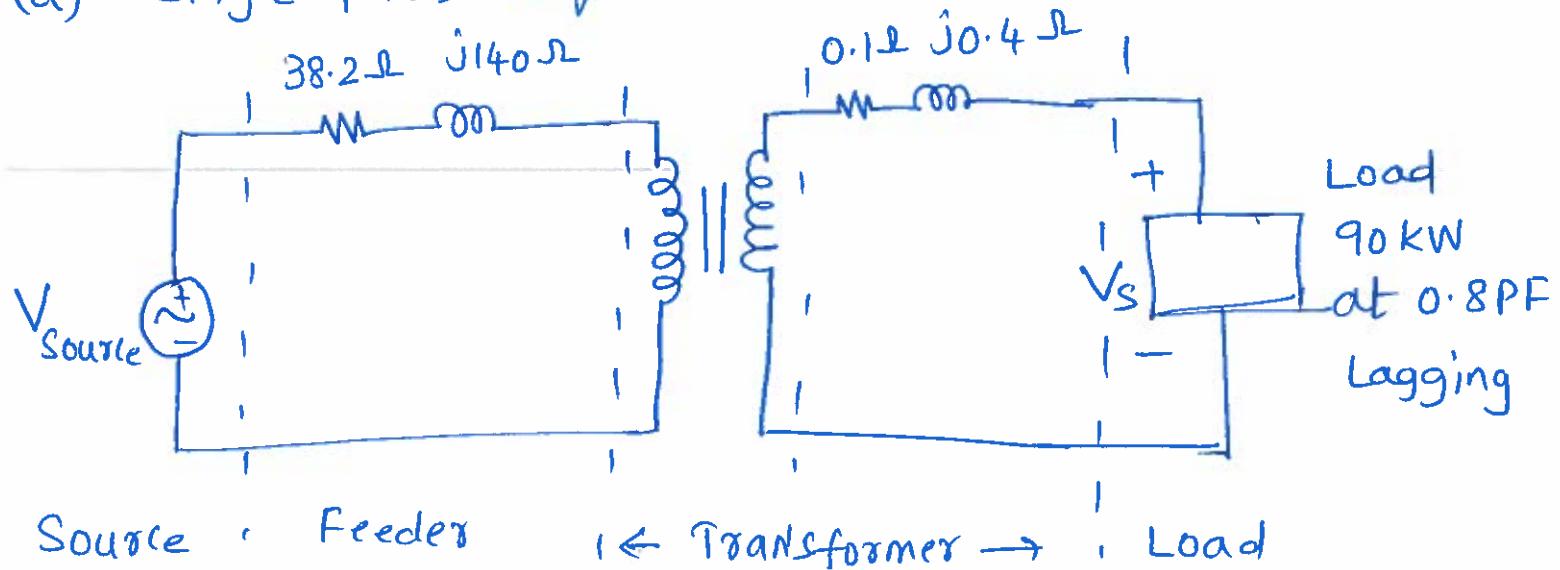(a) Single-phase equivalent circuit of the power-system



(b) To solve this problem, we will refer the circuit to the secondary (low-voltage) side.

The feeder impedance referred to the secondary side is

$$Z_{line} = (38.2 + j140) \Omega$$

$$a = \frac{14 \text{ kV}}{2.4 \text{ kV}}$$

(2)

$$Z_{\text{line}}^1 = \frac{(38.2 + j140) \Omega}{a^2}$$

$$Z_{\text{line}}^1 = (1.12 + j4.11) \Omega$$

To compute the Secondary Current I_s

$$P_s = V_s I_s \cos \theta_s$$

$$I_s = \frac{P_s}{V_s \cos \theta_s}$$

$$= \frac{90 \times 10^3}{(2400)(0.8)} = 46.88 \text{ A}$$

$$\therefore \bar{I}_s = 46.88 \angle -\cos^{-1}(\text{PF})$$


$$\bar{I}_s = 46.88 \angle -36.87^\circ \text{ A}$$

The voltage at the power source of this system
(referred to the secondary side) is

$$V_{\text{source}}^1 = V_s + I_s Z_{\text{line}}^1 + I_s Z_{\text{eqs}}$$

Taking $V_s = 2400 \angle 0^\circ \text{ V}$ as reference

(3)

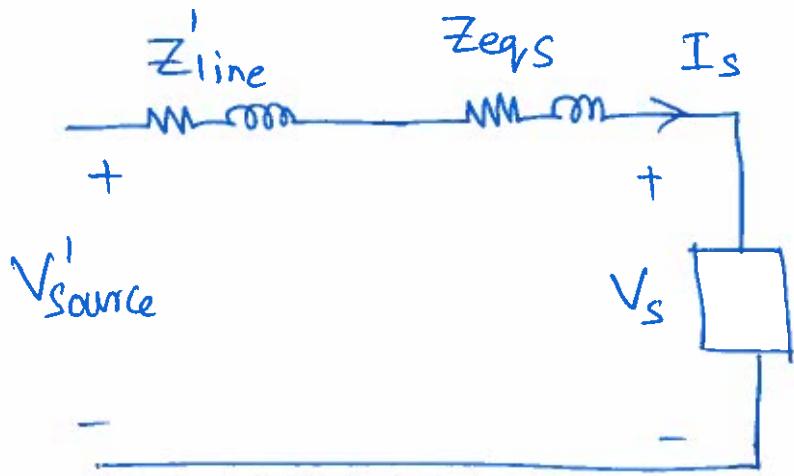

$$V'_{\text{Source}} = V_s + I_s (Z_{\text{line}} + Z_{\text{eqs}})$$

$$= 2400 \angle 0^\circ + 46.88 \angle -36.87^\circ (1.12 + j4.11 + 0.1 + j0.4)$$

$$V'_{\text{Source}} = 2576 \angle 3.0^\circ \text{ V}$$

\therefore The voltage at the power source is

$$\begin{aligned} V_{\text{source}} &= V'_{\text{source}} : a \\ &= (2576 \angle 3.0^\circ) \left(\frac{14 \text{ kV}}{2.4 \text{ kV}} \right) \end{aligned}$$

$$V_{\text{source}} = 15.5 \angle 3.0^\circ \text{ kV}$$

(c) To find the voltage regulation of the transformer we must find the voltage at the primary side of the transformer (referred to the secondary side).

(4)

$$V_p' = V_s + I_s Z_{eq,s}$$

$$= 2400 \angle 0^\circ + (46.88 \angle -36.87^\circ) (0.1 + j0.4)$$

$$V_p' = 2415 \angle 0.3^\circ V$$

\therefore Voltage regulation is

$$VR = \frac{|V_p'| - |V_s|}{|V_s|} \times 100$$

$$= \frac{2415 - 2400}{2400} \times 100$$

$$VR = 0.63\%$$

(d) The overall efficiency of the power system will be the ratio of the output power to the input power.

The output power = power supplied to the load

$$= 90 \text{ kW}$$

$$\text{Input power } P_{in} = P_{out} + P_{loss}$$

(5)

$$P_{in} = P_{out} + P_{loss}$$

$$= P_{out} + I^2 R$$

$$= (90 \times 10^3) + (46.88)^2 (1.22)$$

$$P_{in} = 92.68 \text{ kW}$$

Therefore the efficiency of the power system is

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$= \frac{90 \times 10^3}{92.68 \times 10^3} \times 100\%$$

$$\eta = 97.1\%$$


Problem - 3 :-

$$\text{Turns ratio } a = \frac{8000}{230} = 34.78$$


$$Z_{eqP} = (20 + j100) \Omega$$

$$R_{CP} = 100 \text{ k}\Omega \quad X_{MP} = 20 \text{ k}\Omega$$

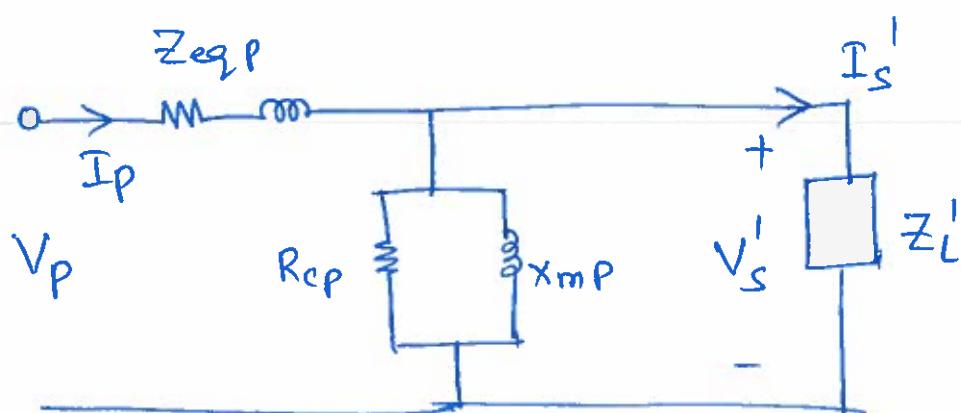(a) Equivalent circuit referred to the Primary side



Approximate equivalent circuit,

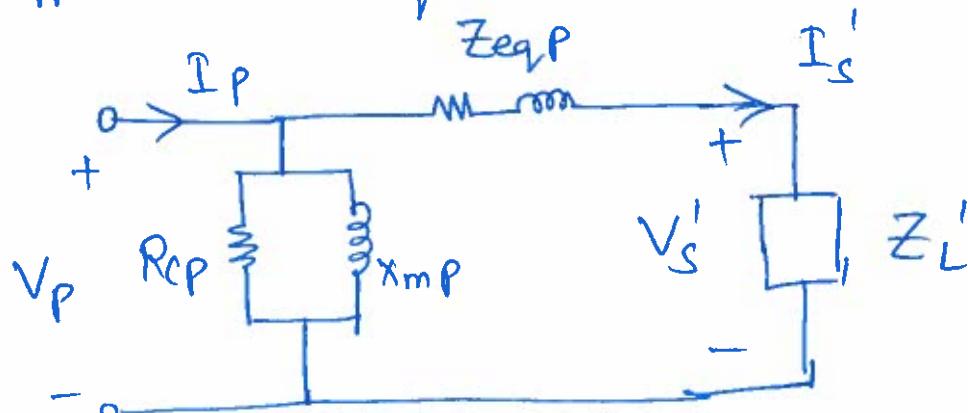

(2)

The load impedance referred to the primary side,

$$Z_L' = a^2 Z_L$$

$$Z_L' = (34.78)^2 (2.0 + j0.7) = 2419 + j847 \Omega$$

The referred Secondary Current,

$$I_s' = \frac{V_p}{Z_{eqp} + Z_L'}$$

$$= \frac{7967 \angle 0^\circ}{(20 + j100) + (2419 + j847)}$$

$$I_s' = 3.045 \angle -21.2^\circ A$$

The referred Secondary voltage is,

$$V_s' = I_s' Z_L' = (3.045 \angle -21.2^\circ) (2419 + j847)$$

$$V_s' = 7804 \angle -1.9^\circ V$$

The actual Secondary voltage is

$$V_s = \frac{V_s'}{d} = \frac{7804 \angle -1.9^\circ}{34.78} = 224.4 \angle -1.9^\circ V$$

(3)

The voltage regulation is

$$VR = \frac{|V_p| - |V_s'|}{|V_s'|} \times 100 \text{ %}$$

$$= \frac{7967 - 7804}{7804} \times 100 \text{ %}$$

$$VR = 2.09\%$$

(b) Now the load is disconnected. Connect a capacitor with $Z_L = -j3.0 \Omega$ as load.

The load impedance referred to the primary side is

$$Z_L' = a^2 Z_L = (34.78)^2 (-j3.0) = -j3629 \Omega$$

The referred secondary current is

$$I_s' = \frac{V_p}{Z_L' + Z_{eqp}}$$

$$= \frac{7967 L^0}{(-j3629) + (20 + j100)}$$

$$I_s' = 2.258 \angle 89.7^\circ A$$

(4)

The referred Secondary voltage is

$$V_s' = I_s' Z_i = (2.258 \angle 89.7^\circ) (-j3629)$$

$$V_s' = 8194 \angle -0.3^\circ V$$

The actual Secondary voltage is

$$V_s = \frac{V_s'}{a} = \frac{8194 \angle -0.3^\circ}{34.78} = 235.6 \angle -0.3^\circ V$$

The voltage regulation is

$$\begin{aligned} VR &= \frac{|V_p| - |V_s'|}{|V_s'|} \times 100\% \\ &= \frac{7967 - 8194}{8194} \times 100\% \end{aligned}$$

$$VR = -10.6\%$$

problem 4

$$\text{Turns ratio: } a = \frac{2200}{220} = 10$$

$$a - R_{sp} = R_p + a^2 R_S = 4 + 10^2 \times 0.04 = 8 \Omega$$


$$x_{esp} = x_p + a^2 x_S = 5 + 10^2 \times 0.05 = 10 \Omega$$

$Z_{esp} = (8 + j10) \Omega$ - Total series impedance referred
to HV side

$Z_{ess} = (0.08 + j0.1) \Omega$ - Total series impedance referred
to LV side

$$b - I_S = \frac{10,000}{220} = 45.45, Q = -\cos 0.8 = -36.87^\circ$$

$$I_S = 45.45 \angle -36.87^\circ$$

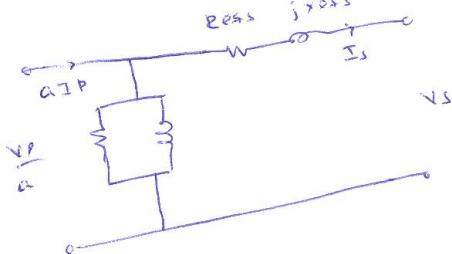

$$\frac{V_p}{a} = V_S + I_S (R_{ess}, jx_{ess})$$

$$= 220 \angle 0^\circ + 45.45 \angle -36.87^\circ [0.08 + j0.1] = 225.64 \angle 0.36^\circ$$

$$\text{Voltage Regulation VR} = \frac{\frac{V_p}{a} - V_S}{V_S} \times 100\% =$$

$$= \frac{225.64 - 220}{220} \times 100\% = 2.56\%$$

$$c - \frac{V_p}{a} = 220 \angle 0^\circ + 45.45 \angle -36.87^\circ [0.08 + j0.1] = 220.258 \angle 1.81^\circ$$

$$\text{NR} = \frac{220.258 - 220}{220} \times 100\% = 0.1173\%$$

$$d - P_C = 80 \text{ W}$$

$$P_{CU} = I_s^2 R_{REFS} = 45.45 \times 0.08$$

$$= 165.25 \text{ W}$$

$$P_{OUT} = 10 \times 0.8 = 8 \text{ kW}$$

$$\eta = \frac{P_{OUT}}{P_{OUT} + P_{CU} + P_C} = \frac{8000 \text{ W}}{8000 \text{ W} + 80 \text{ W} + 165.25 \text{ W}} \times 100\%$$
$$= 97.025\%$$

It will be the same, because the magnitude of

the load current is the same.