

EE 306: Electromechanical Devices - Semester 161

Homework #4

Problem 1

A separately excited DC generator has six poles and is running at 1150 rpm. The armature has 120 slots with 8 conductors per slot and is connected as lap winding. The generated voltage in each conductor is 1.5 V and each conductor can carry a full load current of 4 A. Determine:

- The terminal voltage on no load,
- The output current on full load,
- The required flux per pole,
- The power developed by the armature on full load.

Repeat the calculations for wave-connected armature.

Problem 2

An 8-pole DC shunt generator running at 500 rpm is supplying a load of 5 kW at 250 V. The armature resistance $R_a = 0.24 \Omega$ and the field resistance $R_f = 250 \Omega$. Find:

- The load, field, and armature currents,
- The generated EMF,
- The developed power and torque,
- The input mechanical power (rotational losses are 645 W)

Problem 3

A DC Shunt motor of 250 V as input voltage has an armature resistance of 0.2Ω and a field resistance of 110Ω . While running at no load the motor consumes 1000 W at a speed of 1100 rpm. The full load input power is 14 kW at 250 V. (Armature reaction is neglected)

- Find the motor rotational losses
- Estimate the full load motor speed

- c. Calculate the motor speed regulation
- d. What will be the motor converted power and induced torque
- e. Find the motor efficiency

Problem 4

A 240 V, short shunt cumulative compound generator is rated at 100 A. The shunt field current is 3 A. It has an armature resistance of 50 m Ω , a series field resistance of 10 m Ω and a rotational loss of 2 kW. When the generator is supplying the full load at the rated voltage, determine:

- a. The generated voltage
- b. The magnitude of the shunt field resistance
- c. The developed power
- d. Efficiency