

# KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

## ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-306

### Key Solution

Quiz 1a          Ser. #:          I.D.:          Name:

Q.1 Three identical impedances of  $4 - j3$  Ohm are delta-connected and supplied from a three-phase source of 208-V line-line. The phase and line currents absorbed by the load are

- a.  $I_{ph} = 41.6 \angle -36.87^\circ$  A          ;           $I_{Line} = 72.05 \angle -66.87^\circ$  A
- b.  $I_{ph} = 41.6 \angle +36.87^\circ$  A          ;           $I_{Line} = 72.05 \angle +6.87^\circ$  A
- c.  $I_{ph} = 24.02 \angle -36.87^\circ$  A          ;           $I_{Line} = 41.6 \angle -36.87^\circ$  A
- d.  $I_{ph} = 24.06 \angle +36.87^\circ$  A          ;           $I_{Line} = 41.6 \angle +6.87^\circ$  A

Q.2 A three-phase substation bus supplies two wye-connected loads that are connected in parallel. Load 1 draws 50 kW at 0.866 leading power factor, and load 2 draws 36 kVA at 0.9 lagging power factor. The line-to-line voltage at the loads is 460 V.

Total real and reactive power supplied by the substation bus is

- a.  $P = 98.4$  kW          ;           $Q = 78.9$  kVAR (inductive)
- b.  $P = 98.4$  kW          ;           $Q = 13.17$  kVAR (capacitive)
- c.  $P = 82.4$  kW          ;           $Q = 78.9$  kVAR (inductive)
- d.  $P = 82.4$  kW          ;           $Q = 13.17$  kVAR (capacitive)