

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-463 -161

Key Solutions

Quiz 1 ser#: I.D.: Name:

Q.1 A 40-MVA, 400-kV/20-kV, single-phase transformer has the following series impedances: $0.9 + j1.8$ Ohm (referred to the low-voltage side) and $40 + j80$ Ohm (referred to the high-voltage side). Using the transformer rating as base, determine the per unit equivalent impedance of the transformer referred to the low-voltage side.

- a. $400 + j 800$
- b. $4.0 + j 8.0$
- c. $1.0 + j 2.0$
- d. $0.10 + j 0.20$**

Q.2 A 40-MVA, 400-kV/20-kV, single-phase transformer has the following series impedances: $0.9 + j1.8$ Ohm (referred to the low-voltage side) and $40 + j80$ Ohm (referred to the high-voltage side). Using the transformer rating as base, determine the per unit equivalent impedance of the transformer referred to the high-voltage side.

- a. $400 + j 800$
- b. $4.0 + j 8.0$
- c. $1.0 + j 2.0$
- d. $0.10 + j 0.20$**


Q.3 A 40-MVA, 400-kV/20-kV, single-phase transformer has the following series impedances: $0.9 + j1.8$ Ohm (referred to the low-voltage side) and $40 + j80$ Ohm (referred to the high-voltage side). Using the transformer voltage ratio as the voltage base, and 400-MVA as the MVA base; determine the per unit equivalent impedance of the transformer referred to the low-voltage side.

- a. $400 + j 800$
- b. $4.0 + j 8.0$
- c. $1.0 + j 2.0$**
- d. $0.10 + j 0.20$

Q.4 A 40-MVA, 400-kV/20-kV, single-phase transformer has the following series impedances: $0.9 + j1.8$ Ohm (referred to the low-voltage side) and $40 + j80$ Ohm (referred to the high-voltage side). Using the transformer voltage ratio as the voltage base, and 400-MVA as the MVA base; determine the per unit equivalent impedance of the transformer referred to the high-voltage side.

- a. $400 + j 800$
- b. $4.0 + j 8.0$
- c. $1.0 + j 2.0$**
- d. $0.10 + j 0.20$

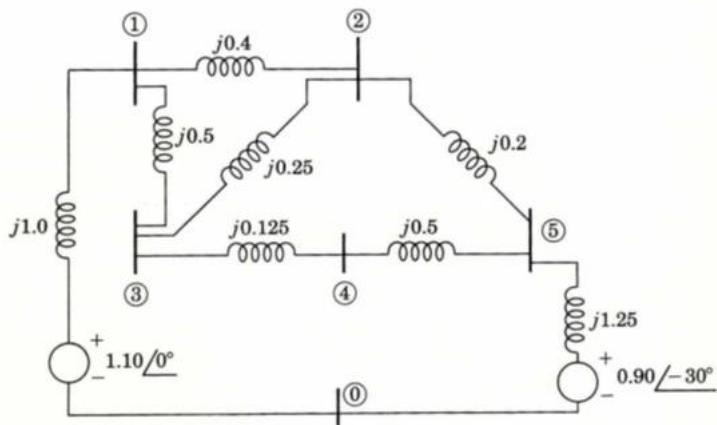Q5. The Y_{bus} for the following network is



a. $Y_{bus} = j$

$$\begin{vmatrix} -5.5 & 2.5 & 2.0 & 0.0 & 0.0 \\ 2.5 & -11.5 & 4.0 & 0.0 & 5.0 \\ 2.0 & 4.0 & -14.0 & 8.0 & 0.0 \\ 0.0 & 0.0 & 8.0 & -10.0 & 2.0 \\ 0.0 & 5.0 & 0.0 & 2.0 & -7.8 \end{vmatrix}$$

b. $Y_{bus} = -j$

$$\begin{vmatrix} -5.5 & 2.5 & 2.0 & 0.0 & 0.0 \\ 2.5 & -11.5 & 4.0 & 0.0 & 5.0 \\ 2.0 & 4.0 & -14.0 & 8.0 & 0.0 \\ 0.0 & 0.0 & 8.0 & -10.0 & 2.0 \\ 0.0 & 5.0 & 0.0 & 2.0 & -7.8 \end{vmatrix}$$

c. $Y_{bus} = j$

$$\begin{vmatrix} -1.900 & 0.400 & 0.500 & 0.000 & 0.000 \\ 2.500 & -0.850 & 0.250 & 0.000 & 0.200 \\ 0.500 & 0.250 & -0.875 & 0.125 & 0.000 \\ 0.000 & 0.000 & 0.125 & -0.625 & 0.500 \\ 0.000 & 0.200 & | & 0.000 & 0.500 & -1.950 \end{vmatrix}$$

d. $Y_{bus} = -j$

$$\begin{vmatrix} -1.900 & 0.400 & 0.500 & 0.000 & 0.000 \\ 2.500 & -0.850 & 0.250 & 0.000 & 0.200 \\ 0.500 & 0.250 & -0.875 & 0.125 & 0.000 \\ 0.000 & 0.000 & 0.125 & -0.625 & 0.500 \\ 0.000 & 0.200 & | & 0.000 & 0.500 & -1.950 \end{vmatrix}$$