

Homework 4

EE-306 – Electromechanical Devices - Semester 162

Submission Deadline: 20 Apr 2017

Note: You must submit this cover page along with your solution

Student Name	ID	Sr. #	Section

Total Marks Obtained /

Problem 1

A four-pole DC machine has a wave winding of 300 turns. The flux per pole is 0.025 Wb. The DC machine rotates at 1000 rpm.

- Determine the machine constant,
- Determine the generated voltage,
- Determine the kW rating if the rated current through the turn is 25 A.

Problem 2

A separately excited DC generator has six poles and is running at 1150 rpm. The armature has 120 slots with 8 conductors per slot and is connected as **wave winding**. The generated voltage in each conductor is 1.5 V and each conductor can carry a full load current of 4 A. Determine the following:

- The terminal voltage at no load,
- The output current at full load,
- The required flux per pole,
- The power developed by the armature on full load.

Problem 3

Part (a)

A self excited DC shunt generator (20 kW, 200 V, 1800 rpm) has $R_a = 0.1 \Omega$, $R_{fw} = 150 \Omega$. Assume that $E_a = V_t$ at no load. Data for the magnetization curve at 1800 rpm are:

I_f (A)	0.0	0.125	0.25	0.5	0.625	0.75	0.857	1.0	1.25	1.5
E_a (V)	5	33.5	67	134	160	175	190	200	214	223

- Determine the maximum generated voltage,
- At full-load condition, $V_t = V_t(\text{rated})$, $I_a = I_a(\text{rated})$, If $I_f = 1.25$ A. Determine the value of the field control resistance R_{fc} ,
- Determine the electromagnetic power and torque developed at full-load condition.

Part (b)

Suppose that the shunt generator is now connected as a long-shunt compound generator. If the full-load terminal voltage, $V_t = 200V$, and resistance of the series field windings is 0.04Ω .

- Determine the generated voltage,
- Draw the long-shunt generator circuit diagram and label it.

Problem 4

A 240 V DC shunt motor has an armature resistance of 0.05Ω . When the motor is connected to its supply, the armature current is 20 A, the field current is 12 A, and the speed is 1200 rpm. Now, a load is applied to the shaft, and the armature current increases to 300 A and the speed drops to 1150 rpm. Determine the following for the loaded condition,

- (a) Rotational loss,
- (b) Field circuit loss,
- (c) Efficiency at the loaded condition.

Problem 5

A DC series motor (230 V, 12 hp, 1200 rpm) is connected to a 230 V supply, draws a current of 40 amperes, and rotates at 1200 rpm. $R_a = 0.25 \Omega$ and $R_{sr} = 0.1 \Omega$. Assume magnetic linearity.

- (a) Determine the power and torque developed by the motor,
- (b) Determine the speed, torque, and power if the motor draws 20 amperes.

Problem 6

A 220 V shunt DC motor has an armature resistance of 0.2Ω and a field resistance of 110Ω . At no-load, the motor runs at 1000 rpm and it draws a current of 7 A. At full-load, the input to the motor is 11 kW.

- (a) Determine the speed regulation of the motor at full-load conditions.

!End of Homework Problems!