

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE 306 – Term 171

HW # 1: Three-Phase Circuits

Due Date: October 2nd, 2017

Problem # 1:

Three impedances of $4 + j3 \Omega$ are Δ -connected and tied to a three-phase 208-V power line. Find I_ϕ , I_L , P , Q , S , and the power factor of this load.

Problem # 2:

Prove that the line voltage of a Y-connected generator with an acb phase sequence lags the corresponding phase voltage by 30° . Draw a phasor diagram showing the phase and line voltages for this generator.

Problem # 3:

A balanced 3-phase, 173-V, 60-Hz source supplies the two following loads:

- ❖ A Δ -connected load with a phase impedance of $(18+j24) \Omega$,
- ❖ A Y-connected load with a phase impedance of $10\angle 53.13^\circ \Omega$.

Find:

- a. The power factor of the entire load.
- b. The total line current supplied.
- c. The total real, reactive, and apparent powers.

