

# KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

## ELECTRICAL ENGINEERING DEPARTMENT

### EE 306 – Term 172

#### HW # 1: Three-Phase Circuits

ST Classes Due: February 4<sup>th</sup> ; MW Classes February 5<sup>th</sup> , 2018

#### Key Solution

##### Problem # 1: (1-point)

Given the number  $A_1 = 5\angle 30^\circ$  (in polar form) and  $A_2 = -3 + j4$  (in rectangular form). Calculate the following, given the answers in both rectangular and polar forms:

- $A_1 + A_2$
- $A_1 * A_2$
- $A_1 / (A_2)^*$

##### Solution:

$$A_1 = 5 \angle 30^\circ = 4.33 + j2.50$$

$$A_2 = -3 + j4 = 5 \angle 126.9^\circ$$

$$\textcircled{a} A_1 + A_2 = 1.33 + j6.5 = 6.63 \angle 78.4^\circ$$

$$\textcircled{b} A_1 A_2 = 25 \angle 156.9^\circ = -23 + j9.8$$

$$\textcircled{c} A_1 / A_2^* = 1 \angle 156.9^\circ = -0.92 + j0.39$$

**Problem # 2: (1-point)**

A load with an impedance of  $Z = 25\angle 53.1^\circ \Omega$  is fed from a single-phase source of 220V.

- Find the resistance and reactance of the load.
- Find the real (active) and imaginary (reactive) power of the load.
- Find the power factor of the load, and state whether it is lagging or leading.

**Solution:**

$$\textcircled{a} \quad Z = 15 + j20$$

$$R = 15 \, \Omega$$

$$X = 20 \, \Omega$$

$$\textcircled{b} \quad I = \frac{V}{Z} = \frac{220 \angle 0^\circ}{25 \angle 53.1^\circ} = 8.8 \angle -53.1^\circ$$

$$\textcircled{c} \quad S = \mathbf{VI}^* = (220 \angle 0^\circ)(8.8 \angle -53.1^\circ)^* = 1936 \angle 53.1^\circ = 1162 + j1549 \text{ VA}$$

$$P = 1162 \text{ W}$$

$$Q = 1549 \text{ VAR}$$

$$\textcircled{c} \quad \text{PF} = \cos 53.1^\circ = 0.6 \text{ lagging}$$

**Problem # 3: (2-points)**

A delta connected load has per-phase impedance of  $45\angle 60^\circ \Omega$  is fed a 208-V 3-phase substation through a 3-phase feeder. The per-phase impedance of the feeder is  $(1.2 + j 1.6) \Omega$ . Calculate the line to line voltage at the load terminals.

**Solution:**

$$Z_{\Delta} = 45 \angle 60^\circ \Omega ; Z_{\text{fdr}} = 1.2 + j1.6 \Omega$$

$$Z_Y = \frac{1}{3} Z_{\Delta} = 15 \angle 60^\circ = 7.5 + j13 \Omega$$

$$Z_T = Z_{\text{fdr}} + Z_Y = 7.5 + j13 + 1.2 + j1.6 = 8.7 + j14.6 \Omega$$

$$\mathbf{I} = \frac{V_{\text{ph}}}{Z_T} = \frac{(208/\sqrt{3}) \angle 0^\circ}{8.7 + j14.6} = 7.06 \angle -59.2^\circ \text{ A}$$

$$\begin{aligned} V_{\text{LOAD}} &= V_{\text{ph}} - Z_{\text{fdr}} \mathbf{I} = 120 \angle 0^\circ - (1.2 + j1.6)(7.06 \angle -59.2^\circ) \\ &= 120 + j0 - (14.04 - j1.493) = 106 \angle 0.81^\circ \text{ V}_{\text{LN}} \\ &= 183.6 \angle 30.81^\circ \text{ V}_{\text{LL}} \end{aligned}$$

**Problem # 4: (2-points)**

A 345-kV, 3-phase transmission line delivers 500 MVA, 0.866 power factor lagging, to a 3-phase star-connected load.

- Find the line and phase currents drawn by the load.
- Find the per-phase impedance of the load in polar form.
- Find the total active and reactive power of the load.

**Solution:**

$$\textcircled{a} \quad I_{ph} = \frac{500,000}{\sqrt{3} (345)} \frac{1}{\cos^{-1} 0.866} = 836.74 \angle -30^\circ \text{ A}$$

$$V_{ph} = \frac{345}{\sqrt{3}} \angle 0^\circ = 199.2 \angle 0^\circ \text{ V}$$

$$I_L = I_{ph} = 836.74 \angle -30^\circ \text{ A}$$

$$\textcircled{b} \quad Z_{Y,ph} = \frac{199.2 \angle 0^\circ}{836.74 \angle -30^\circ} = 238 \angle 30^\circ \Omega$$

$$\textcircled{c} \quad P_T = 433 \text{ MW} ; Q_T = 250 \text{ MVAR}$$

**Problem # 5: (2-points)**

A 3-phase motor draws 40 kVA at 0.65 power factor lagging from a 230-V source. A capacitor bank (i.e., 3-phase capacitors) is connected across (i.e., in parallel) the motor terminals to make the compined power factor 0.95 lagging.

- Find the required KVAR rating of the capacitor bank.
- Find the line current before and after the capacitors are added.

**Solution:**

$$S_M = 40 \text{ kVA}, V_M = 230 \text{ V}, PF_M = 0.65 \text{ lagging}$$

$$P_M = 40 (0.65) = 26 \text{ kW}$$

$$\theta_M = \cos^{-1} 0.65 = 49.46^\circ$$

$$\textcircled{a} \quad Q_M = P_M \tan \theta_M = 26 \tan 49.46^\circ = 30.4 \text{ kVAR}$$

$$PF_{\text{new}} = 0.95$$

$$\theta_{\text{new}} = \cos^{-1} 0.95 = 18.19^\circ$$

$$Q_{\text{new}} = P_M \tan \theta_{\text{new}} = 8.54 \text{ kVAR} = Q_M + Q_C$$

$$\therefore Q_C = Q_{\text{new}} - Q_M = 8.54 - 30.4 = -21.86 \text{ kVAR}$$

$$\textcircled{b} \quad I_{\text{before}} = \frac{40,000}{\sqrt{3} (230)} \angle -\cos^{-1} 0.65 = 100 \angle -49.46^\circ$$

$$I_{\text{after}} = \frac{26,000}{\sqrt{3} (230)(0.95)} \angle -\cos^{-1} 0.95 = 68.7 \angle -18.19^\circ$$

**Problem # 6: (2-points)**

A balanced 3-phase, 173-V, 60-Hz source supplies the two following loads:

- ❖ A  $\Delta$ -connected load with a phase impedance of  $(18+j24) \Omega$ ,
- ❖ A Y-connected load with a phase impedance of  $10\angle 53.13^\circ \Omega$ .

Find:

- a. The power factor of the entire load.
- b. The total line current supplied.
- c. The total real, reactive, and apparent powers.

**Solution:**

Convert  $\Delta$  to Y 
$$Z_y = \frac{18 + j24}{3} = 6 + j8$$

Parallel combination of the 2 loads (per phase)

$$Z_T = \frac{(6 + j8)(10\angle 53.1^\circ)}{6 + j8 + 10\angle 53.1^\circ} = 5\angle 53.1^\circ$$

- a. Power factor =  $\cos(53.1^\circ) = 0.6$  lag
- b.  $I_L = I_{ph} = \frac{173/\sqrt{3}\angle 0^\circ}{5\angle 53.1^\circ} = 20\angle -53.1^\circ \text{ A}$
- c.

$$P_T = \sqrt{3} \times 173 \times 20 \times 0.6 = 3.596 \text{ kW}$$

$$Q_T = \sqrt{3} \times 173 \times 20 \times 0.8 = 4.794 \text{ kVAR}$$

$$|S_T| = \sqrt{3} \times 173 \times 20 = 5.993 \text{ kVA}$$