

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

Electrical Engineering Department

EE 306 – Term 172

HW # 3: Single Phase Transformers

(Solution)

Solution P1:

(a)

$$V_{H(\text{rated})} = 1000\text{V}, I_{H(\text{rated})} = \frac{100 \times 10^3}{1000} = 100\text{A}.$$

$$V_{L(\text{rated})} = 100\text{V}, I_{L(\text{rated})} = \frac{100 \times 10^3}{100} = 1000\text{A}$$

From open circuit test,

$$R_{CL} = \frac{100^2}{400} = 25\ \Omega.$$

$$I_{CL} = \frac{100}{25} = 4\text{A}.$$

$$I_{mL} = \sqrt{6^2 - 4^2} = 4.47\text{A}$$

$$X_{mL} = \frac{100}{4.47} = 22.37\ \Omega$$

$$\text{Turns ratio } a = \frac{1000}{100} = 10$$

Refer to high voltage side,

$$R_{CH} = 25 \times 10^2 = 2500\ \Omega, X_{mH} = 2237\ \Omega$$

From short circuit test,


$$R_{eqH} = \frac{1800}{100^2} = 0.18\ \Omega.$$

$$Z_{eqH} = \frac{50}{100} = 0.5\ \Omega$$

$$X_{eqH} = \sqrt{0.5^2 - 0.18^2} = 0.4665\ \Omega$$

(b)

Equivalent circuit referred to H.V. side

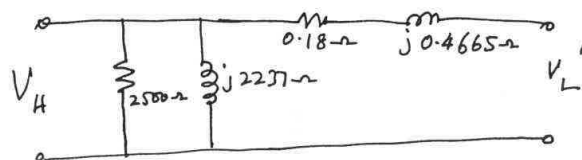


(c)

$$V_1 = V_2' + I_2' Z_{eqH}$$

$$= 1000 \angle 0^\circ + 100 \angle 53^\circ (0.18 + j0.4665)$$


$$= 974.4 \angle 2.5^\circ$$
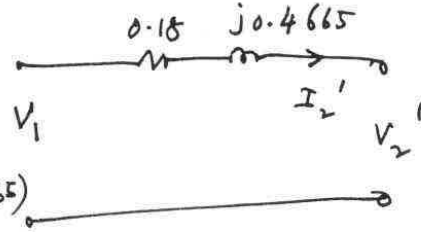
$$V.R = \frac{974.4 - 1000}{1000} \times 100 \% = -2.56 \%$$



(d)

Phaser Diagram

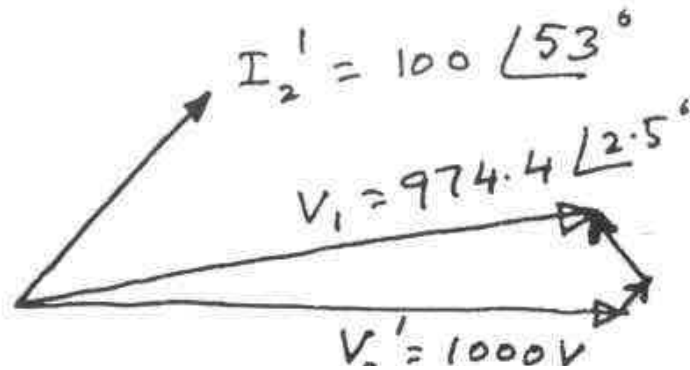

Solution P2:

$$\text{Turn's Ratio } a = \frac{2400}{240} = 10$$


Take the secondary voltage as reference phasor.

$$\bar{V}_s = 240 \angle 0^\circ \text{ V}$$

The Secondary current is

$$\bar{I}_s = \frac{150,000}{240} \angle -\cos^{-1} 0.85$$

$$= 625 \angle -31.8^\circ \text{ A}$$

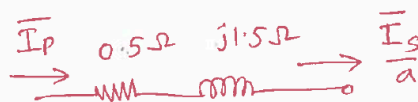

$$\bar{V}_p \qquad \qquad \qquad a \bar{V}_s$$



$$P_{\text{output}} = \frac{150,000 \times 0.85}{0.85} = 127,500 \text{ W}$$

$$P_{cu} = I_p^2 R_{eqp} = \left(\frac{625}{10}\right)^2 \cdot (0.5) = 1953 \text{ W}$$

$$P_{\text{core}} = 600 \text{ W}$$

The efficiency is,

$$\eta = \frac{P_{\text{output}}}{P_{\text{output}} + P_{\text{core}} + P_{cu}} \times 100$$

$$= \frac{127,500}{127,500 + 600 + 1953} \times 100$$

$$\eta = 98\%$$

Solution P3:**(a)**

$$P_{out} = V_S I_S \cos \theta_S = 0.7 \times 30,000 \times 0.7 = 14,700 \text{ W}$$

$$P_{core} = 400 \text{ W}$$

$$P_{cu} = I_S^2 R_{eqs} \Rightarrow R_{eqs} = \frac{P_{cu}}{I_S^2} = \frac{1200}{\left(\frac{30,000}{240}\right)^2} = 0.0768 \Omega$$

$$P_{cu} @ 0.7 \text{ load} \Rightarrow P_{cu} = 0.7^2 * 1200 = 588 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{out} + P_{core} + P_{cu}} \times 100$$

$$= \frac{14,700}{14,700 + 400 + 588} \times 100 = 93.7 \%$$

(b) I_S at man. efficiency

$$I_S = \left(\frac{P_{cu}}{R_{eqs}} \right)^{1/2} = \sqrt{\frac{400}{0.0768}}$$

Page 5 of 10

$$I_S = 72.168 \text{ A}$$

$$P_{out} |_{\eta_{max}} = V_S I_S \cos \theta_S$$

$$= 240 \times 72.168 \times 1$$

$$P_{out} |_{\eta_{max}} = 17320.5 \text{ W}$$

(c)

$$\eta_{\max} = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{core}} + P_{\text{ly}}} \times 100$$
$$= \frac{17320.5}{17320.5 + 400 + 400} \times 100$$

$$\eta_{\max} = 95.58\%$$

(d)

Output kVA at $\eta_{\max} = 17.320$

Rated kVA = 30

η_{\max} occurs at $\frac{17.320}{30} = 57.7\%$ of full load.