

# KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

## ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-306

### Key Solution

Quiz 3

Sec.: 3

I.D.:

Ser#:

Name:

Q1. For a non-ideal transformer connected to a resistive load, which sentence is absolutely correct? (4 points)

- a. The primary-current lags the primary-voltage.
- b. The primary-current is in-phase with the primary-voltage.
- c. The primary-current leads the primary-voltage.

Q2. The equation below is for calculating the primary current of non-idea transformers when using (4 points)

$$I_p = I_s / a + [(1/R_c) + (1/jX_m)] * V_p$$

- a. the approximate equivalent-circuit with magnetization-branch referred to the primary side.
- b. the approximate equivalent-circuit with magnetization-branch referred to the secondary side.
- c. the approximate equivalent-circuit without magnetization-branch referred to the primary side.
- d. the approximate equivalent-circuit without magnetization-branch referred to the secondary side.

Q3. The magnetization reactance in the excitation-branch of non-ideal transformers can be obtained from the open-circuit test. (2 points)

- a. True.
- b. False.