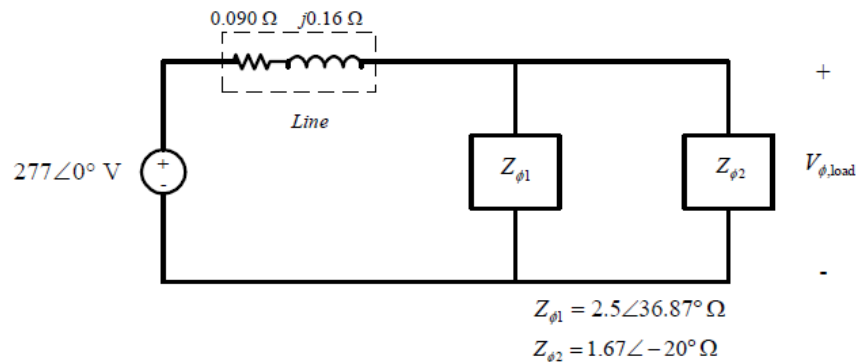


EE 306: Solution of Home Work #1

Problem 1 Solution:

SOLUTION To solve this problem, first convert the delta-connected load 2 to an equivalent wye (by dividing the impedance by 3), and get the per-phase equivalent circuit.



(a) The phase voltage of the equivalent Y-loads can be found by nodal analysis.

$$\frac{V_{\phi, \text{load}} - 277 \angle 0^\circ \text{ V}}{0.09 + j0.16 \Omega} + \frac{V_{\phi, \text{load}}}{2.5 \angle 36.87^\circ \Omega} + \frac{V_{\phi, \text{load}}}{1.67 \angle -20^\circ \Omega} = 0$$

$$(5.443 \angle -60.6^\circ) (V_{\phi, \text{load}} - 277 \angle 0^\circ \text{ V}) + (0.4 \angle -36.87^\circ) V_{\phi, \text{load}} + (0.6 \angle 20^\circ) V_{\phi, \text{load}} = 0$$

$$(5.955 \angle -53.34^\circ) V_{\phi, \text{load}} = 1508 \angle -60.6^\circ$$

$$V_{\phi, \text{load}} = 253.2 \angle -7.3^\circ \text{ V}$$

Therefore, the line voltage at the loads is $V_L \sqrt{3} V_\phi = 439 \text{ V}$.

(b) The voltage drop in the transmission lines is

$$\Delta V_{\text{line}} = V_{\phi, \text{gen}} - V_{\phi, \text{load}} = 277 \angle 0^\circ \text{ V} - 253.2 \angle -7.3^\circ = 41.3 \angle 52^\circ \text{ V}$$

(c) The real and reactive power of each load is

$$P_1 = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(253.2 \text{ V})^2}{2.5 \Omega} \cos 36.87^\circ = 61.6 \text{ kW}$$

$$Q_1 = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(253.2 \text{ V})^2}{2.5 \Omega} \sin 36.87^\circ = 46.2 \text{ kvar}$$

$$P_2 = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(253.2 \text{ V})^2}{1.67 \Omega} \cos (-20^\circ) = 108.4 \text{ kW}$$

$$Q_2 = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(253.2 \text{ V})^2}{1.67 \Omega} \sin (-20^\circ) = -39.5 \text{ kvar}$$

(d) The line current is

$$I_{\text{line}} = \frac{\Delta V_{\text{line}}}{Z_{\text{line}}} = \frac{41.3 \angle 52^\circ \text{ V}}{0.09 + j0.16 \Omega} = 225 \angle -8.6^\circ \text{ A}$$

Therefore, the losses in the transmission line are

$$P_{\text{line}} = 3 I_{\text{line}}^2 R_{\text{line}} = 3 (225 \text{ A})^2 (0.09 \Omega) = 13.7 \text{ kW}$$

$$Q_{\text{line}} = 3 I_{\text{line}}^2 X_{\text{line}} = 3 (225 \text{ A})^2 (0.16 \Omega) = 24.3 \text{ kvar}$$

(e) The real and reactive power supplied by the generator is

$$P_{\text{gen}} = P_{\text{line}} + P_1 + P_2 = 13.7 \text{ kW} + 61.6 \text{ kW} + 108.4 \text{ kW} = 183.7 \text{ kW}$$

$$Q_{\text{gen}} = Q_{\text{line}} + Q_1 + Q_2 = 24.3 \text{ kvar} + 46.2 \text{ kvar} - 39.5 \text{ kvar} = 31 \text{ kvar}$$

The power factor of the generator is

$$\text{PF} = \cos \left[\tan^{-1} \frac{Q_{\text{gen}}}{P_{\text{gen}}} \right] = \cos \left[\tan^{-1} \frac{31 \text{ kvar}}{183.7 \text{ kW}} \right] = 0.986 \text{ lagging}$$

Problem 2 Solution:

The per-phase equivalent circuit is first constructed. For load 1, a Y-connected balanced load, the per-phase impedance is $150 + j50 \Omega$. For load 2, a Δ -connected balanced load, the per-phase impedance is the equivalent Y-connected load which is $Z_{\Delta}/3 = 300 + j200 \Omega$. We will represent load 3 in terms of the complex power it absorbs per-phase. This is given by

$$\begin{aligned} S_{3/\phi} &= \frac{95040}{3} (0.6 - j0.8) \\ &= 19,008 - j25,344 \text{ VA} \end{aligned}$$

The voltage across the per-phase equivalents of these loads has been specified as 4800 V, which is the line-to-neutral voltage at the load end.

The per-phase equivalent circuit is shown below in Figure 3

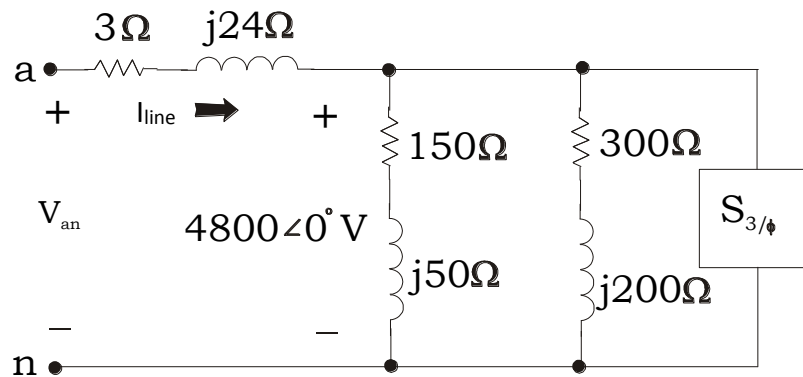


Figure 3 Per-Phase Equivalent Circuit

$$\begin{aligned} \mathbf{I}_\ell &= \frac{4800}{150 + j50} + \frac{4800}{300 + j200} + \frac{19,008 + j25,344}{4800} \\ &= 28.8 - j9.6 + 11.0769 - j7.3846 + 3.96 + j5.28 \\ &= 43.8369 - j11.7046 \text{ A}(rms) \\ &= 45.3725 \angle -14.949^\circ \text{ A}(rms) \end{aligned}$$

In the above step, the total current is obtained by summing the individual currents through the three loads. For loads 1&2, we

use the expression $\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}}$, and for load 3 the current is determined using $\mathbf{I} = \left(\frac{S}{\mathbf{V}} \right)^*$.

In the distribution line,

$$P_{loss} = 3 |I_{eff}|^2 R = 3(45.3725)^2 (3) = 18,528.04 W$$

$$Q_{loss} = 3 |I_{eff}|^2 X = 3(45.3725)^2 (24) = 148,224.34 VAR$$

In each load,

$$P_1 = 3 |28.8 - j9.6|^2 (150) = 414,720 W$$

$$Q_1 = 3 |28.8 - j9.6|^2 (50) = 138,240 VAR (abs)$$

$$P_2 = 3 |11.0769 - j7.3846|^2 (300) = 159,507.02 W$$

$$Q_2 = 3 |11.0769 - j7.3846|^2 (200) = 106,338.02 VAR (abs)$$

$$P_3 = 95,040 (0.6) = 57,024 W$$

$$Q_3 = -95,040 (0.8) = -76,032 VAR$$

$$S_{total} = 636,251 + j168,546 VA (load end)$$


Check :

$$S_{total} = 3(4800)(43.8369 + j11.74046) = 631,251 + j168,546 VA$$

$$\begin{aligned} S_{sending} &= 631,251 + j168,546 + 18,528.04 + j148,224.34 VA \\ &= 649,779.04 + j316,770.34 VA \end{aligned}$$

$$\%P = \frac{631,251}{649,779.04} \times 100 = 97.148$$

Problem 3 Solution:

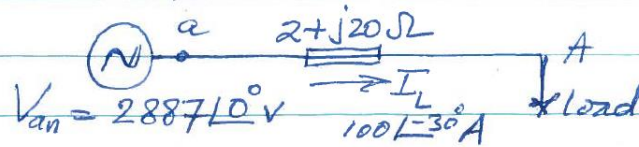

$$1. \text{PF}_{\text{source}} = \cos(\theta_v - \theta_i) = \cos(0 + 30^\circ) = 0.866 \text{ lagging}$$

$$2. V_{AN} = V_{an} - Z_L I_L = 2887\angle 0^\circ - (2 + j20)100\angle -30^\circ$$

$$V_{AN} = 2887 - (2 + j20)(86.6 - j50)$$

$$V_{AN} = 2887 - (1173.2 + j1632) = 1713.8 - j1632$$

$$V_{AN} = 2366.54 \angle -43.6^\circ \text{ V}$$

$$3. \text{PF}_{\text{load}} = \cos(\theta_v - \theta_i) = \cos(-43.6 + 30) = 0.972 \text{ leading}$$

a. leading

b. Capacitive

$$4. P = 3 \frac{|V_{AN}| |I_L|}{1000} \cos \theta_{\text{load}} = 3 \times 2366.54 \times 100 \times 0.972$$

$$Q = 3 \frac{|V_{AN}| |I_L|}{1000} \sin \theta_{\text{load}} = 3 \times 2366.54 \times 100 \times -0.235$$

$$P = 690083.064 \text{ W}$$

$$Q = -166942 \text{ VAR}$$

Problem 4 Solution:

(a) Assume $\vec{V}_{an} = \frac{480}{\sqrt{3}} \angle 0^\circ \text{ V}$ $\vec{V}_{ab} = 480 \angle 30^\circ \text{ V}$
 $Z_Y = 4 \angle 36.87^\circ \Omega$ $Z_\Delta = 10 \angle 30^\circ \Omega$

$$S_Y = 3 \frac{V_\phi^2}{Z_Y^*} = \frac{V_L^2}{Z_Y^*} = \frac{(480)^2}{4 \angle -36.87^\circ} = 57600 \angle 36.87^\circ$$

$$S_Y = 46080 + j 34560 \text{ VA}$$

$$S_\Delta = 3 \frac{V_L^2}{Z_\Delta^*} = 3 \frac{480^2}{10 \angle -30^\circ} = 69120 \angle 30^\circ = 59859.7 + j 34560 \text{ VA}$$

$$\therefore S_T = P_T + j Q_T = 105939.7 + j 69120 \text{ VA}$$

$$= 126494.25 \angle 33.12^\circ \text{ VA}$$

$$I_T = \frac{S}{\sqrt{3} V_L} = \frac{126494.25}{\sqrt{3} 480} = 152.14 \text{ A}$$

(b) $S_{\text{cap}} = -j \frac{(480)^2}{5} = Q_c = -j 46080 \text{ VAR}$

$$S_{T_{\text{new}}} = 105939.7 + j 23040 = 108416.15 \angle 12.27^\circ \text{ VA}$$

(c) $I = \frac{S_{T_{\text{new}}}}{\sqrt{3} V_L} = \frac{108416.15}{\sqrt{3} 480} = 130.4 \text{ A}$

The current is reduced since part of the reactive power is compensated by the capacitor bank.