

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-306

Key Solution

Quiz 1 Sec.: 7 I.D.: Ser#: Name:

Q.1 In a Y-connected abc-sequence system (going counter clockwise), the line voltage V_{ba} leads the phase voltage V_{an} by 150° (4-points)

- a. TRUE.
- b. FALSE.

Q.2 A three-phase substation delivers 120-MW to a three-phase load, at 0.8 power factor lagging. The load is (---), and has (---) apparent power. (3-points)

- a. inductive, 96 MVA
- b. capacitive, 96 MVA
- c. inductive, 150 MVA
- d. capacitive, 150 MVA

Q.3 In a Wye-connected source feeding directly a Delta-connected resistive-load, (3-points)

- a. phase current phase-angle of the load is the source line-current phase-angle.
- b. phase-current phase-angle of the load is the source phase-current phase-angle.
- c. phase-current phase-angle of the load is the source line-current phase-angle minus 30° .
- d. phase-current phase-angle of the load is the source line-current phase-angle plus 30° .