

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-463 - 131

Key Solutions


Quiz 3

ser#:

I.D.:

Name:

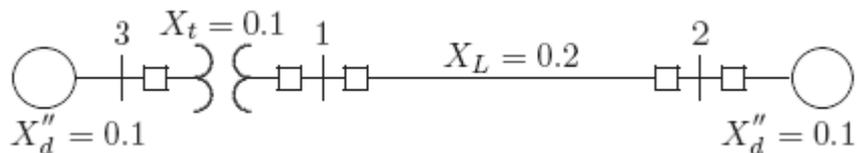The one-line diagram of a simple power system is shown below. All impedances are expressed in per unit on a common MVA base. The generators are operating on no load at their rated voltage with their emfs in phase. A three-phase fault occurs at bus 1 through a fault impedance of $Z_f = j0.08$ per unit.



1) Using Thevenin's theorem, the impedance to the point of fault is

- a) $j 0.3$ pu
- b) $j 0.2$ pu
- c) $j 0.12$ pu**
- d) $j 0.08$ pu

2) The voltage on bus 2 due to the fault at bus 1 is

- a) 0.0 pu
- b) 0.4 pu
- c) 0.7 pu
- d) 0.8 pu**