

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
Department of Electrical Engineering

EE200 Digital Logic Circuit Design	Quiz #4 (19/10/2005)	Section: 03
Student's Name :		I.D.# :

Determine the Boolean functions for outputs F and G as a function of inputs A , B , C , and D . Show the output functions in a sum of products form and sum of minterms.

